An exciting hobby....for everyone

everyday MAY 74 20p 40 electronics

Australia 40c New Zealand 45c



24 PAGE South Africa 40c Malaysia \$1.80 Sweden Kr.3.50 Malta 22c5

Dictionary of Electronic Terms





COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT.

BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER.



★ 4 Transistor Earpiece Radio ★ Signal Tracer ★ Signal Injector ★ Transistor Tester NPN-PNP ★ 4 Transistor Push Pull Amplifier ★ 5 Transistor Push Pull Amplifier ★ 7 Transistor Loudspeaker Radio MWLW ★ 5 Transistor Short Wave Radio ★ Electronic Metronome ★ Electronic Noise Generator ★ Batteryless Crystal Radio ★ One Transistor Radio ★ 2 Transistor Regenerative Radio ★ 2 Transistor Regenerative Radio ★ 3 Transistor Regenerative Radio ★ 4 Multible Continuity Tester ★ Sensitive Pre-Amplifier.

★ 24 Resistors ★ 21 Capacitors ★ 10 Transistors
★ 31 loudspeaker ★ Earpiece ★ Mica Baseboard ★ 3 12way connectors ★ 2 Volume controls ★ 2 Slider Switches
★ 1 Tuning Condenser ★ 3 Knobs ★ Ready Wound
MW/LW/SW Colls ★ Ferrite Rod ★ 61 yards of wire ★ 1
yard of sleeving, etc. ★ Parts price list and plans 50p (FREE with parts).

Total Building Costs P P & Ins. 44p. (Overseas P & P £7·23 £1.85p.) (+ 10% VAT 72p)

ROAMER TEN

with
VHF including aircraft. 10 Transistors.
Latest 4" 2 watt Ferrite Magnet Loudspeakers, 9 Tunable




speakers, 9 Tunable
Wavebands, MW1, SW2, SW3, Trawler Band, VHF
MW2, LW, SW1, SW2, SW3, Trawler Band, VHF
and Local Stations also Aircraft Band, Built in
Ferrite Rod Aerial for MWI/LW. Retractable, chrome
plated 7 section Telescopic Aerial, can be angled and
rotated for peak short wave and VHF listening. Push
Pull output using 600 mw Transistors. Car Aerial and
Tape Recording Sockets. 10 Transistors plus 3 Diodes.
Ganged Tuning Condenser with VHF section.
Separate coil for Aircraft Band, Volume
Separate coil for Aircraft Band, Attractrotated and pull of the pull of the pull output using 600 mw Tape Recording Sockets. 10 Transistors puls and to ganged Tuning Condenser with VHF section. Separate coil for Aircraft Band. Volume on/off. Wave Change and tone Control. Attractive Case in black with silver blocking. Size 9" × 7" × 4". Easy to follow instructions and diagrams. 9" × 7" × 4". Easy to follow instructions and diagrams. The pulse of on/off. Wave Change and tive Case in black with silver block by "x 7" x 4". Easy to follow instructions and Parts price list and plans 30p (FREE with Total building costs (Overseas P. & P. £1.85) (+ 10% VAT 85p)

POCKET FIVE

3 Tunable wavebands.
M.W./L.W. and Trawler
Band. 7 stages, 5 transistors and 2 diodes.
supersensitive ferrite rod aerial, moving coll loud-speaker, attractive Black and Gold Case. Size
51 × 11 × 34" approx.
Plans and parts price list
159, (Free with parts).

Total Building Costs £2.28 PP& Ins. 26p (Overseas P &P 1.25p)

(+ 10% VAT 22p)

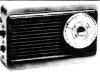


TRANSONA

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial.

Total Building Costs £2.50 PP& Ins. 26p (+ 10% VAT 25p) (Overseas P & P 1.25p)

NEW **EVERYDAY** SERIES

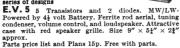Build this exciting New series of designs



Total Building Costs £2.73 PP& Ins. 30p (Overseas P & P £1 25p) (+ 10% VAT 27p)

E.V. 6 Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc., MW/LW coverage. Push Pull output. Parts price list and Plans 15p. Free with parts.

Total Building Costs £3.60 P&P Ins. 30p (Overseas P & P £1.25p) (+ 10% VAT 36p)

E.V. 7 Case and looks as above. 7 Transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" loud-speaker. Parts price list and easy build plans 20p. Free with parts.

Total Building Costs £4.08 PP& Ins. 31p (+ 10% VAT 40p)

ROAMER **EIGHT Mk 1 NOW WITH** VARIABLE TONE CONTROL



Total Building Costs £6.98 PP& Ins. 47p

NEW ROAMER NINE

WITH V.H.F INCLUD-ING AIRCRAFT

Nine Transistors. Tunable wave bands as Roam



(+ 10% VAT 69p)



Components include:
Tuning Condenser: 2 Volume Controls: 2 Slider
Switches: Fine 3" Tone Moving Coil Speaker: Terminal
Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards:
10 Transistors: 4 Diodes: Resistors: Capacitors:
Three f" Knobs. Units once constructed are detachable
from Master Unit servicing them to be befored the Three f" Knobs. Units once constructed are usual from Master Unit, enabling them to be stored for future use, Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

Total Building Costs

£5.50 PP& & Ins. 33p (+ 10% VAT 55p)

ROAMER SIX Case and looks as Trans-Eight

6 Tunable Wavebands: MW, LW, SW1, SW2, SW3, Trawler band plus an Extra Medium waveband for easier tuning of Luxembourg etc. Sensitive ferrite rod aerial and telescopic aerial for Short Waves. 3in. Speaker. 8 stages—6 transistors and 2 diodes. Attactive black case with red grille, dial and black knobs with polished metal inserts. Size 9 × 6‡ × 2‡in. approx. Plans and parts price list 25p (FREE with

(Overseas P. & P. £1.85)

Total Building Costs £3.98 PP& Ins. 31p + 10% VAT 39p)

TRANS EIGHT

8 TRANSISTORS and 3 DIODES

6 Tunable Wavebands; MW, LW, SW1, SW2, SW3 and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 3in. Speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size $9 \times 5\frac{1}{5} \times 2\frac{1}{5}$ in. approx. Push pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

Total Building Costs £4.48 PP& Ins. 33p


(+ 10% V.A.T. 44p)

Callers side entrance "Lavells" Shop Open 10-1, 2.30-4.30 Mon.-Fri.-9-12 Sat.

RADIO EXCHANGE CO

61a HIGH STREET, BEDFORD, MK40 1SA Reg. no. 788372	7	'el. 0234 52367
I enclose £ for	٠.	
Name	• •	
Address	• •	
	• •	(Dept. E.E.5.)

The Catalogue you MUST have!

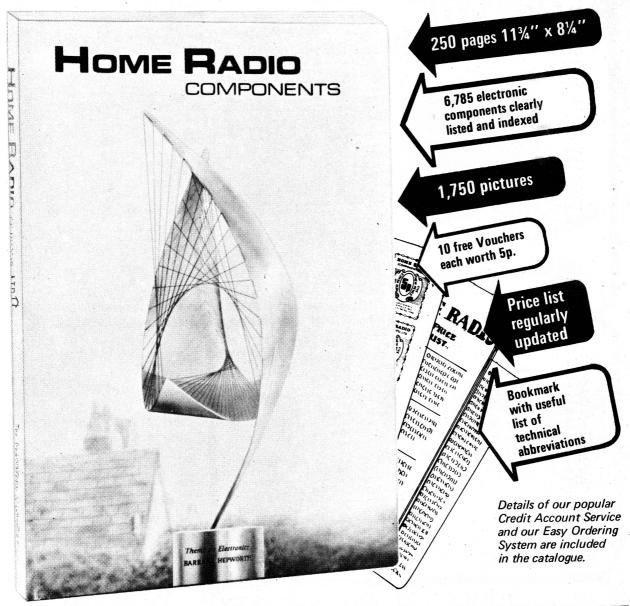

Only 55p. plus 22p POST AND PACKING

POST THIS COUPON with cheque or P.O. for 77p.

The price of 77p applies only to customers in the U.K. and to BFPO addresses

ne			
dress		: . N -	



COMPLETE* REO SYSTEM



40 Watt Amplifier.

Viscount III - R102 now 20 watts per channel. System I includes,

Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/ stereo on/off function and bass and treble filters. Plus headphone socket.

Specification

20 watts per channel into 8 ohms. Total distortion@ 10W@ 1kHz 0·1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K. equalised within ± 1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. Tone controls and filter characteristics. Bass: +12dB to -17dB@ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble + 12dB to -12dB@ 15kHz. Treble filter: 12dB per octave. Signal to noise ratio: (all controls at max.) -58dB. Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all

inputs. Size approx. $13\frac{3}{4}" \times 9" \times 3\frac{3}{4}"$. Garrard SP25 deck, with magnetic cartridge, de luxe plinth and hinged cover.

Two Duo Type II matched speakers -Enclosure size approx. $17\frac{1}{2}$ " \times $10\frac{1}{2}$ " \times 6" in simulated teak. Drive unit 13"×8" with parasitic Complete System £51.00

£69·00

Viscount III amplifier (As System I) Garrard SP. 25 (As System I) Two Duo Type IIIA matched speakers-

Enclosure size approx. $31'' \times 13'' \times 171\frac{1}{2}''$. Finished in teak veneer. Drive units approx. $13\frac{1}{2}$ " $\times 8\frac{1}{4}$ " with $3\frac{1}{4}$ " HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz.

Complete System £69.00

PRICES · SYSTEM 1

Viscount III R 102 amplifier £24.20 + £1 p & p £14.00 + £2.20 p & p 2 Duo Type II speakers Garrard SP25 with

MAG. cartridge de luxe plinth

and hinged cover £21.00 + £1.75 p & p.

total £59.20

Available complete for only £51.00 +£3.50 p. & p.

PRICES: SYSTEM 2

Viscount R 102 amplifier £24.20 +£1 p & p 2 Duo Type III A speakers £39.00 +£4.00 p & p

Garrard SP25 with

MAG. cartridge de luxe plinth £21.00 + £1.75 p & p. and hinged cover

total £84.20

Available complete for only £69.00+£4 p & p.

Stereo 21 easy to assemble audio system kit, - no soldering required. Includes:

BSR 3 speed deck, automatic, manual facilities together with ceramic cartridge.

Two 8" × 5" speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

For the technically minded :-

Specifications:

Input sensitivity 600mV:Aux. input sensitivity 120mV: Power output 2.7 watts per channel: Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. Overall Dimensions. Speakers approx. $15\frac{1}{2}''\times8''\times4''$. Complete deck and cover in closed position approx. $15\frac{1}{2}''\times12''\times6''$. Complete only $\bf £18.95+£1.00$

Extras if required. p & p

Optional Diamond Styli £1.37

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance, £3.85.



Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Outputs 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).

Inputs *5 Electrically Mixed Inputs. *3 Individual Mixing controls. *Separate bass and treble controls common to all 5 inputs. *Mixer employing F.E.T. (Field Effect Transistors), *Solid State Circuitry, *Attractive Styling,

INPUT SENSITIVITIES

1) Crystal Mic or Guitar 9mV. 2) Moving coil Mic or Guitar 8mV. 3), 4), 5) Medium output equipment (Gram. Tuner, Monitor, Organ, etc.) all 250mV sensitivity.

AC Mains 240V. operation,

Size approx. $12\frac{1}{2}$ ins \times 6 ins \times $3\frac{1}{2}$ ins £13.50 + 60p.

postage & packing.



Elegant self selector push button player for use with your own stereo system. Compatible with Viscount III system, the Stereo 21 and the Unisound module. Technical specification.

Mains input, 240V, Output sensitivity 125mV Comparable unit sold elsewhere at £24.00 approx.

Yours for only £10.95 + 90p. p& p




For the man who wants to design his own stereo -here's your chance to start, with Unisoundpre-amp, power amplifier and control panel. No soldering-just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only. £7.64 + 55p. p&p

PETAPE LINK



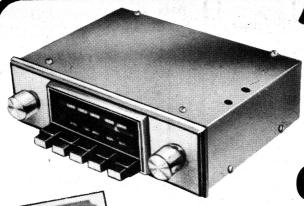A suitable 3 speed tape deck, less heads. Caters up to $5\frac{3}{4}$ ins. spools. 240V AC mains. Unused but store soiled hence no warranty: £4.00 + £1.00 p & p



Remember! one of the Top Ten Accessory
Awards from Motor magazine
PUSH BUTTON*
CAR RADIOKIT

BUILD YOUR OWN TOURIST PUSH BUTTON CAR RADIO

Technical specification:

- 1.) Output 2.5 watts R.M.S. into 8 ohms. For 12 volt operation on negative or positive earth.
- Integrated circuit output stage, pre built three stage IF Module.

Controls Volume, manual tuning and five push buttons for station selection, illuminated tuning scale covering full medium and long wave bands.

Size Chassis 7 ins. wide, 2 ins. high and $4\frac{5}{16}$ ins. deep approx.

NOTE: The ability to solder on a printed circuitboard is necessary to complete this kit successfully. Circuit diagram and comprehensive instructions 55p. free with kit.

Car Radio Kit


£6.60 + 55p. postage & packing.

Speaker including baffle and fixing strips

 ${f f1.65}+{f 23p.}$ postage & packing.

Recommended Car Aerial - fully retractable and locking. **£1.35 post paid.**

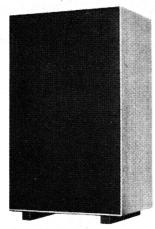THE ULTIMATE COMPLETE SPEAKER SYSTEM EMI LE 315



Recommended retail selling price, £86.00.

Our price £45.00 + £3.50 postage & packing.

A professional standard five way speaker system with enclosure giving top quality performance.

Enclosure Dimensions approx. (3 ft. \times 2 ft. \times 1 ft.). Drive Units

Hand built – 15" diameter bass with 3" voice coil, – two 5" diameter Mid

Range units,

– two 3¼" HF. units,
plus matching crossover
panel with two variable
potentiometers for mid and

high frequency adjustment.

Powder Handling

Continuous rating 35 W rms., Peak power rating 70 W. Frequency Response

20 Hz 20,000 Hz. Impedance 8 ohms.

EMI SPEAKERS FANTASTIC REDUCTION



15" 14A/780. Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

Recommended retail price £40·80. OUR PRICE £18·70 + £1·50 p & p



950 Kit – Five matched speakers and crossover unit for handling up to 45 watts, frequency response from 20 to 20,000 Hz.

Huge 19" × 14" (approx.) high efficiency Bass-Speaker with 16,500-gauss magnet built on a heavy diecast frame.

The four 10,000 gauss tweeters, each $3\frac{1}{4}$ " dia. approx., are fed by the crossover which critically adjusts signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil 2", others 0.5". Recommended list price f44-00.

OUR PRICE £25.00 + £1.50 p & p Special Offer.



Just write your order giving your credit card number

DO NOT SEND YOUR CARD Mail orders to Acton. Terms C.W.O. All enquires Stamped Addressed Envelope. Goods not despatched outside U.K.

Leaflets available for all items listed.* Send stamped addressed envelope.



Radio and TV Components (Acton) Ltd.
21 High Street, Acton, London W3 6NG(E)
323 Edgware Road, London W2

Edgware: 9 a.m.-5.30 p.m. Half day Thurs. Acton: 9.30 a.m.-5 p.m. Closed all day Wed.

RESCENT RADIO LTD

11. 15 & 17 MAYES ROAD, LONDON N22 6TL 888 3206

Components

galore for the

experimenter

Ex computer boards with: Resistors, Capacitors and

useful Transisto

transistors per board.

BARGAIN BOARDS

10% VAT TO BE ADDED TO ALL GOODS & CARRIAGE PRICES

7' × 4' LO UDSPEAKER
A top quality
speaker ideal where
small size is important. Manufactured
by E.M.I. for a wellknown hi-fi set
known hi-fi

postage on this item.

CRESCENT P.300. DISCO CON-

GRESCENT P. 300. DISCO CONTROL PACK.

A control unit which when connected to twin decks makes a disco of professional quality. We supply a smart front panel which incorporating, mixing, pre-amp and head-phone listening amplifier. The power pack enables this unit to work from the standard mains. Inputs include Mic. Tape, Cassett and Twin Decks. *Controls include Mic. Tape, Each Deck and P.F.L. Full instructions are included with every Pack. MONO = \$14 plus 20p PP. STEERO = \$17 plus TWO WAY STEREO
ADAPTOR
Stereo jack plug to two
stereo line sockets complete with 110 mm of
cable. For plugging two
stereo inputs into one. A
Bargain at 65p plus 5p P&P.

STEREO / MONO HEADPHONE
VOLUME CONTROL BOX
Plug Stereo phones into this control box
and you then incorporate a right and
left hand volume control and a stereo/ mono switch. Complete with stereo jack plug and 2 m cable. A Bargain at £1. Plus 10p P. & P.

LOW VOLTAGE AMPLIFIER Few only at plus 13p P. & P.

5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm

With high IMP input this amplifter will work as a record player, baby alarm, etc., amplifter. "CRESCENT" CATALOGUE If you are a construct should own a copy.
Send 20p inc. Postage.

MINI LOUDSPEAKERS

2½" (57mm) 40ohm — 50p each 2½" (57mm) 80ohm — 50p each Please include 5p. P. & P. up to 3 Mini-Loudspeakers

in contact with the whole world. We give

skilled preparation for the G.P.O. licence

MAIL ORDER

DEPT. No. II MAYES RD. LONDON **6TL**

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY (WE CLOSE ALL DAY THURSDAY)

13 SOUTH MALL, EDMONTON, N.9 803 1685

TRI-VOLT BATTERY ELIMINATOR Enables you to work your transistor radio, amplifier, or cassette, etc. from A.C. mains through this compact eliminator. Just by moving a plug lect the voltage you require — 6v, 74v

eliminator. Just by moving a plug you can select the voltage you require — 6v, 7½v or 9 volts. This means all your transistor power pack applications can be handled by this one unit. Approx. size: 2½° x 2½° x 3½°. OUR PRICE — 82°75p + 10°P. P. & P. Same model suitably wired for the Philips Cassette — 23°00 + 10p. P. & F.

200/250V MAINS RELAY

per 100 relays.

Heavy duty contacts. 2,500 Ω coil. All new and unused D.P.D.T. mains relays 50p + V.A.T. Carr. Free. Special quantity price: £40

CHANNEL
SOUND TO

This fantastic little box
approx. 4" × 3" × 24" when
connected to the output of a
sound source from 1 to 100 watts
produces a psychedelic light
display of up to 1000 watts.
Complete with a sensitive level
control the unit is fused and can
not harm your amplifier.
A Bargain at 27.50 plus 10p
P. 4 P.

MAINS TRANSFORMER

63p

mains Transfor Fused Primary 240V. Sc 220V @ 50mA. 6-3V This transformer is made to a very high standard and is a small size: 2in X

small size: 2in 2½in × 2½in. 6 plus 15p P. & P.

"CRESCENT BEAT BRITE" SINGLE CHANNEL

econdary @ 1A.

"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U. BUILD. IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

★ THE POWER AMP MODULE TP 100W 170W. r.m.s. sq. wave 300W instantaneous peak into 8 ohm (60W into 16 ohm). \$14.28, carr. 45p.

★ THE PRE-AMP MODULE Four control pre-amp, Vol. Bass, Treble. Middle controls. Designed to drive most ampli-fiers using F.E.T. first stage. £3.96 carr. 25p.

* THE POWER SUPPLY MODULE PS100
Is supplied complete with the mains transformer. 49-66, carr. 50p. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. If you purchase all three modules. 225, carr. 75p. Send S.A.E. for further details on this or our ready built amplifiers

TRI-VOLT CAR
CONVERTER
Enables you to work
your Transistor Radio,
Amplifier or Cassette etc. the supply positive or neg.

earth.
This converter supplies 6, 7½ or 9 volts and is transistor regulated. Approx. size 2½" × 3½" × 2"
Very easy to fit and a real money saving device for 22.50 + 10p. P. & P.

WAFER SWITCHES
1 pole 12 way
2 pole 2 way
2 pole 3 way
2 pole 4 way
2 pole 4 way
3 pole 4 way
4 pole 3 way
18p each. Please inc.
5p P. & P. Up to 3
switches.



POTENTIOMETERS

POTENTIOMETERS
All types 1' and less diameter.

SINGLES DUAL
5K Log or 5K
10K Lin Less 10K
25K Switch 50K
50K Switch 50K
50K Double 250K 40p.
500K Pole 1M
2M Switch 1M
2M 24pea,
Un to 3 Pots. Please add

Pots. Please add

Up to 3 5p. P. *P. MINIATURE RELAYS Brand new range of

range of
British made Relays.
Size—12* × 1" × 2"
All two changeovers with
250V, 1.5A contacts and
suitable for fitting on .1m

 suitable for fitting on ·1m

 Veroboard.

 Type
 Volts
 Current
 Ohms.

 27/A
 12v
 17M/A
 700 Ω

 21/A
 12v
 28M/A
 430 Ω

 12/A
 6v
 33M/A
 185 Ω
 6v 3:

Please include 5p P & P up to



free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL P.O. Box 156, JERSEY

NAME: ADDRESS : _

EEB 5.4. BLOCK CAPS please

YOU AIN'T HEARD **NOTHIN' YET!!**

. . . . until you tune in to stereo perfection with the 'varicap'



Approx. Size 83" x 23" x 65"

Features include push button "Spot On" tuning, with up to 5 pre-set stations (no difficult tuning dial and drive cord). Easy "Ino problem" construction, requiring only a few simple setting up adjustments with a D.C. Voltmeter. Uses NEW pre-set modules for R.F. and I.F. circuits—no circuit alignment. High efficiency Integrated Circuit Phase Lock Loop Decoder for perfect stereo reception, with stereo lamp indicator. TOTAL KIT price only £28.50 including V.A.T. and postage. With Fibre Glass P.C. Board, neat slimline teak veneered cabinet with brushed

aluminium front panels, push buttons etc.

All parts available separately.

IDEAL FOR USE WITH THE "TEXAN", "GEMINI"

AND ANY GOOD QUALITY STEREO AMPLIFIER.

Please send large S.A.E. for full details.

228, ECCLESALL ROAD, SHEFFIELD S11 8PE

Telephone No. (0742) 668888
THE COMPONENT CENTRE OF THE NORTH



SEMI-CONDUCTORS TO SUPPLIERS OF WORLD



TELEPHONES

EX. G.P.O

Normal Household Type Only £ 1-05p P&P 45p each

TELEPHONE DIALS

Post Office type. Guaranteed in working order POST & PACKING 16%

Tested and Guaranteed Paks

· H41



55p

55p

		1,000 PIV lamp plastic
B81	10	Reed Switches, 1" long, \$5p dia. High Speed P.O. type
B99	200	Mixed Capacitors. Approx. quantity, counted by weight 55p
H4	250	Mixed Resistors. Approx. quantity counted by weight 55p P & P 15p
H35	100	Mixed Diodes, Germ, Gold bonded, etc. Marked and Unmarked.
H38	30	Short lead Transistors, NPN Silicon Planar types 55p
H39	6	Integrated Circuits. 4 Gates BMC 962, 2 Flip Flops BMC 945

2 Sil Power transistors comp pair BD131/132

4 IN4007 Sil. Rec. diodes.

Unmarked Untested Paks

B1	50	Germanium Transistors	55p
B66	150	Germanium Diodes Min. glass type	55p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	55p
B86 ·	100	Sil. Diodes sub. min. IN914 and IN916 types	55p
H16	15	Experimenters' Pak of Integrated Circuits, Data supplied	55p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts:	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.	55p

Make a rev counter for your car

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition £1-10_{0 each}

Ex GPO Push Button Intercom Telephones

Exactly as internal telephone systems still in everyday use where automatic internal exchanges have not yet taken over. Available in 5, 10 or 15 ways. Complete with circuits and instructions. Necessary 24 pair cable 22p per yard. Price of each instrument is independent of the number of ways.

P.P. 382D

Cable can be sent by Parcel Post. Post and Packing per 50 yds. 73‡p. Extension Telephones. 71‡p each. p.p 27‡p. £1 37½ for 2. P.&P. 55b. These phones are outside.

A Cross Hatch Generator £3.85 post

A complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. A project in the Sept. '72 edition of Television. Subject to Availability

TESTED & GUARANTEED H65

UNTESTED' UNMARKED H67 IO 3819N Channel FETs 55p

Over 1,000,000 **Transistors** in stock

We hold a very large range of fully marked tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

Our very popular, 4p transistors

TYPE "A" PNP Silicon alloy, TO-5 can TYPE "B" PNP Silicon, plastic encapsulation TYPE "E" PNP Germanium AF or RF TYPE "F" NPN Silicon plastic encapsulation TYPE "G" NPN silicon similar ZTX 300 range TYPE "H" PNP silicon similar ZTX 500 range

RELAYS FOR VARIOUS TYPES P & P 27}p

High Speed Magnetic Counter



4 digit (non-reset) 24v or 48v (state which) 4 x 1 x 1in, 33p, p.p 5p.

Plastic Power Transistors 6

NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

6

world and Guaranteea tening our Tested and Guaranteea tening our Tested and Guaranteea tening our Tested and 15, HFE Min 15, 1-12 13-25 22p 20p 26ip 24ip 26-5 18p 22p

Range 2. VCE. Min. 40. HFE Min 40 1-12 13-25 31p 36½p 29p 33p 38±p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

LM380 Audio I.C. as featured in Practical Wireless December issue complete with application data £1·10

INTEGRATED CIRCUITS

We stock a large range of I.Cs at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available

This fantastically detailed conversion calcula-tor carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid-measure, weights etc. Pocket Size 15p Wall Chart 18p

LOW COST DUEL IN LINE I.C. SOCKETS

14 pin type at 16½ p each \ Now new low profile 16 pin type at 18p each \ type

BOOKS

We have a large selection of Reference and Technical Books in stock.

Send for lists of publications

Our famous P1 Pak

is still leading in value

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels, Identification Chart supplied to give some information on the Transistors.

11p P & P on this Pak. Please ask for Pak P.1. only 55p

	Market / State / Market / Market / Market
Please send me the FRE	E Bi-Pre-Pak Catalogue.

NAME .. ADDRESS

ALL PRICES INCLUDE 10% VAT

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 11p post and packing per order OVERSEAS ADD EXTRA FOR POSTAGE

BUY THESE GOODS WITH ACCESS

Dept.E. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX. TELEPHONE: SOUTHEND (0702) 46344.

GIRO NO. 331 7056 C.W.O. only. P. & P. 10p on orders below £5 Discount: £10–10%, £20–15% (except net items) Export Order enquiries welcome (VAT free)

Official Orders accepted from Educational & Government Departments

SPECIAL RESISTOR KITS (Prices include post & packing)

10E12 ±W KIT: 10 of each E12 value, 22 ohms—IM, a total of 570 (CARBON FILM 5%), £3·65 net

10E12 ±W KIT: 10 of each E12 value, 22 ohms—IM, a total of 570 (CARBON FILM 5%), £3·85 net

25E12 ±W KIT: 25 of each E12 value, 22 ohms—IM, a total of 1425 (CARBON FILM 5%), £8·35 net

25E12 ±W KIT: 25 of each E12 value, 22 ohms—IM, a total of 1425 (CARBON FILM 5%), £8·45 net

20E12 ±W KIT: 25 of each E12 value, 22 ohms—IM, a total of 1425 (CARBON FILM 5%), £10·35 net

15E12 ±W KIT: 15 of each E12 value, 10 ohms—IM, a total of 915 (METAL FILM 5%), £13·55 net

10E12 2W KIT: 10 of each E12 value, 10 ohms—IM, a total of 915 (METAL FILM 5%), £17·15 net

ALL	PRICES	INCLL	DE VAT	

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. Mounting: 0·01μF, 0·015μF, 0·022μF, 0·033μF, 0·047μF, 3½p. 0·068μF, 0·1μF, 4½p. 0·15μF, 4½p. 0·22μF, 5½p. 0·33μF, 8p. 0·47μF, 9p. 0·68μF, 12p. 1μF, 13p. 1·3μF, 23p. 2·μF, 12p. 1μF, 13p. 1·3μF, 23p. 2·μF, 12p. 1μF, 13p. 1·3μF, 13p.

15p. 1· Suf., 23p. 2· 2μf., 26p.

MULLARD POLYESTER CAPACITORS C296 SERIES
400V: 0·001μf. 0·0015μf. 0·002μf. 0·0033μf. 0·0047μf., 24p. 0·0068μf. 0·01μf.
0·015μf. 0·022μf. 0·033μf. 34p. 0·047μf. 0·068μf. 0·1μf., 44p. 0·15μf. 64p.
0·22μf. 84p. 0·33μf. 12p. 0·47μf. 14p.
160V: 0·01μf. 0·01μf. 0·02μf. 19. 0·02μf. 0·068μf. 19. 0·1μf., 44p. 0·15μf., 64p.
5p. 0·02μf. 5p. 0·03μf. 84p. 0·04μf. 0·068μf. 12p. 1μf., 14p. 14p. 0·15μf., 5p. 0·02μf. 3p. 0·047μf. 0·068μf. 12p. 1μf., 14p.

MINIATURE CERAMIC PLATE CAPACITORS
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 56, 68, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (μF) 0·01, 0·015, 0·022, 0·033, 0·047, 2jp. each. 0·1, 30V, 4jp.

2½p. each. 0·1, 30V, 4½p. **POLYSTYRENE CAPACITORS 160V** 5%
(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 4p. 6800, 10,000, 4½p.

		th Stah	Carbon Film	5% MF-	-High Stab Me	ral Film. 5º	V
	. Type	Range	1-99	100-499	500-999	1000+	Size mm
ŧ	CF	22-IM		0.75	0.60	0.55	2·4×7·5
Ŧ	CF	22-2M2	1000	0.75	0.60	0.55	3.9×10.5
Ť	CF .	22-IM		0.75	0.60	0.55	5.5×16
Ŧ	MF	10-2M7	2	1.54	1 · 32	1.1	3×7
Ţ	MF	10-2M2	2	1 · 43	1.21	0.99	4.2×10.8
î	MF	10-10M	3	1.98	1.81	1 · 65	6.6x13
2	MF	10-10M	4.5	3 · 52	3.08	2.75	8×17·5
Fo	r valu	e mixing	prices, please	refer to o	ur catalogue.	(price in	pence each)
V	LUE	SAVAIL	ABLE-E12 Se	eries only.	(Net prices abo	ve 100.)	

PRESET SKELETON POTENTIOMETERS

MINIATURE 0.25W Vertical or horizontal 6p each 1K, 2K2, 4K7, 10K, etc. up to IM Ω SUB-MIN 0.05W Vertical, 100 Ω to 220K Ω 5p each

B. H. COMPONENT FACTORS LTD.

(E.E.) 61 CHEDDINGTON ROAD, PITSTONE, NR. LEIGHTON BUZZARD, BEDS, LU7 9AQ Tel.: Cheddington 668446 (Std. Code 0296) PLEASE WRITE FOR FREE CATALOGUE

Miniature Mullard Electrolytics 1.0μF 63V 6½p 68μF 16V 6½p 1.5μF 63V 6½p 68μF 63V 12p	VEROBOARD 0·1 0·15 2½ × 5″ 28p 28p 2½ × 3½″ 26p 19p	POTENTIOMETERS Carbon Track 5K Ω to 2M Ω, log or lin. Single, 16½p Dual Gang 46p. Log Single with switch 26p Slider Pots. 10K, 100K, 500K. 30mm, 34p. 45mm, 47p. 60mm, 55p.
2. 2µ 63V 6‡p 100µF 25V 6‡p 100µF 25V 6‡p 4. 0µF 40V 6‡p 100µF 63V 14p 4. 0µF 40V 6‡p 100µF 63V 14p 6. 8µF 63V 6‡p 150µF 66 3V 15p 6. 8µF 63V 6‡p 150µF 6. 4V 6‡p 10µF 6. 0µF 60V 6‡p 220µF 6. 4V 6‡p 10µF 65V 6‡p 220µF 63V 21p 15µF 63V 6‡p 220µF 63V 21p 15µF 63V 6‡p 330µF 63V 21p 15µF 63V 6‡p 330µF 63V 25p 16µF 40V 6‡p 470µF 6. 4V 9p 16µF 40V 6‡p 470µF 6. 4V 9p 22µF 63V 6‡p 680µF 15V 15p 15V 15P 15V 15P 15P 15V 15P 15P 15V 15P 15V 15P	3½ × 5" 32p 33p 33p 33p 33p 33p 33g 33g 33g 32p 38p 28p 28p 24p × 1" 7p 7p 7p 7p 24p 32f (Plain) - 12p 24p 5 × 3½" (Plain) - 12p 1nsertion tool 5pp 59p 10p 10p 17rack Cutter 44p 44p 10p 10p 10p 17RANSISTORS ACI27 16½p 8C212L 12p 8C107 11p 8C214L 17p 8C108 12p 0C244 18p	DIODES N4001 64p DIN 2 pin 12p 3 pin 13p 3 p
33μF 16V 64p 1000μF 16V 20p 100μF 16V 20p 100μF 16V 20p 100μF 16V 20p 1500μF 16V 25p 150μF 16V 25p 150μF 16V 25p 150μF 16V 25p 150μF 16V 25p 16	BC109 13p OC71 13p BC148 12p OC81 16p BC149 12p OC170 23p BC183L 12p T1S43 33p BC183L 12p 2N2926 11p BC184L 13p 2N3702 11p	Integrated Circuits Screened Wire, Metre Twin Screened Wire, Metre 1/4709C 6+p 1/2p 55p (NEW KIT) (NEW KIT) μΑ730C 50p 50p 50p 50p 60p μΑ741C 55p 50p 50p 60p 60p 60p 60p 60p 60p 60p 60p 60p 6

LONDON E15 IHJ

S.A.E. FOR ALL ENQUIRIES MAIL ORDER ONLY

ELECTRONIC COMPONENTS FOR E.E. PROJECTS

ELECTRONIC V'METER APR.	74 £6.40 + 10p P & P
SPEED GUARD Mar. 74	£3.60 + 10p P & P
SLIDE TIMER FEB. 74	£2.10 + 10p P & P
FETSET JAN. 74	£2.00 + 10p P & P
TREMOLO DEC. 73	£2.10 + 10p P & P
WAA-WAA AUG. 73	£1.50 + 10p P & P
GEN. PURP. AMP. APR. 73	£4.50 + 25p P & P
20W SHAVER INV. JUL. 72	£4.10 + 30p P & P
BETA FUZZ-TREBLE JAN. 73	£1.50 + 5p P & P
(For Beta Fuzz-Treble, components only)	Component board
BETA TRANSFORMER	£1.85 + 5p P & P

ENGINEERS

JRSELF FOR A ETTER JOB 🞹 MORE PA



Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost B.I.E.T. home study course. There are no books to buy and you can pay-as-you-learn.	The B.I.E.T. guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will cal on you. It could be the best thing you ever did.
IN THE PART OF THE	IC COUDAN IN THE SECOND

Practical Radio & Electronics (Technatron) Electronics (Technatron) Electronic Bagineering Television Maintenace & Servicing General Servicing General Servicing Radio Servicing, Maintenance and Repairs (Ity & Guilds Radio, TV Electronics Mechanics Servicing)	Colour Television Computer Electronics C& GLI Radio TV Servicing Cert. Post Master General 1st & 2nd class Television C & G Electrical C & G Electrical Television C & G Electrical Technicians	
	Aldermaston Court, Reading RG7 4PF QK BEE	03



AUDIOTRONIC Model ATM1

opv pocket multi-meter. Ranges: — 0/10/50/250/1,000 volt AC and DC. DC current 0-1mA/ 100mA. Resistence: 0/150k ohms. Decibels: —10 to +22dB. Size 90 x 60 x 28mm. Complete with test leads.



OUR PRICE £2.95

U4323 MULTIMETER

30,000 opv. Over-load protection. 6/30/60/300/600/

6/30/60/300/600/ 1200V DC. 12/60/ 120/600/1200V AC. 60/µA/ 30mA/300mA.

OUR PRICE £7.50

30,000opv. Mirror scale. Overload protection. 0/0.6/3/15 60/300/1200V DC.

60/300/1200600/ 0/6/30/120/600/ 1200V AC. 0/30uA/ 6mA/60mA/300mA 600mA. 0/8k/80k/ 800k/8 Meg ohms. —20 to +63dB.

OUR PRICE £7.50

U4324 MULTIMETER

MODEL TE300

2K/200K/

2 Meg Ohm. 10 to 63 d 63 dB

U43Z3 MULTIMETER
20,000opv. Simple
unit with audio/IF
cosillator. Suitable
for general receiver
runing. Ranges:
0.5/2.5/10/50/250/
500/1000V DC.
2.5/10/15/250/500/1000V AC. 0.05/
5/5/5/50/500 AD DC. Resistance: 5/
50/500 ohms/5/10/100k ohms/1Meg.
Battery operated. Size: 180 x 97 x
40mm. Supplied in carrying case complete with test leads.

OUR PRICE £7.00

U4312 MULTIMETER extremely sturdy instrument for general electrical use. 657 cpv. 15/30. 60/150/300/600/ 900V DC & 75mV. 0/03/15.7/5/30/ 60/150/300/600/ 900V AC 0/300LA/ 15/6/15/160/600mA/ 15/6/15/160/600mA/ 15/6/15/160/600mA/ 15/6/16/16/ 60/150/600mA/ 15/6/A Co. 0/15/6/15/16/ 60/150/6/CD. 0/15/6/A Co. 0/15/6/A Co.



OUR PRICE £9.75 P&P 25p



MUDEL 500 30,000 opv with overload protect-tion. Mirror scale. 0/0.5/2.5/10/25/ 100/250/500/ 1000V DC. 0/2.5/10/25/100/ 250/500/1000V AC. 0/50uA/5/50 500mA. 12A DC. 0/60k/6 meg/60 me

MILLIAMETER

OUR PRICE £11.95 HIOKI MODEL 700X

HIUKI MUDEL /UU/ 100,000pp; Overload protection. Mirror scale. 0,3/0,6/1.2/1.5/3/6/ 12/30/60/120/300/ 600/1200V DC. 1.5/3/6/12/30/60/150/ 300/600/1200V AC. 15/30uA/3/6/30/60/ 15/50bQmA/6/12A DC. 12/200k/2M/20MOhms. -20 to +53dB.

OUR PRICE £14.95

OUR PRICE £15.00

MODEL AS. 100D VOM

Model HT100B4 MULTIMETER

Model HT100BA MULTIMETER
Overload protected,
shock proof circuits,
9,5uA Meter with
mirror scale. Sensitivity,
100KV. Polarity change
switch. Ranges: 0.5/2.5/
1/50/250/500/1,000
Volts DC. 2.5/10/50/
250/1,000 Volts AD.
200K/2/20 Meg. chms.
DC current: —0 10A.—20
to +62dB. Operates from 2 x 1.5V
batteries. Size: 180 x 134 x 79mm.
PUR PRIFE F15 n0

OUR PRICE £ 13.95 Carr. paid Leather case for above £1.75

MILLIAMETER
43 ranges 0-0.3/0.6/
1.5/3/6/12/30/60/150/
300/600/1.200V DC.
0-3/6/15/30/60/120/
300/600/1.200V DC.
Current: 0-30/60uA/
1.5/3/15/30/15/30/
mA/6/12A. Resistence:
0-3/30/6/3/30Mohms.
Decibels: -10 to +17dB. Output: -0-3/6/15/30/60/1/300V
acy 23 SD CC. 49/ACC. Sentitutivity
meter. Built in protection. Size: 57 x
102 x 153mm.

HIOKI 750X VOLT-OHM-



U4317 MULTIMETER

U4317 MULTIMETER
High sensitivity
instrument for field
and laboratory work.
Knife edge pointer,
Senm. mirror scale.
56.27.2.5710.725.90.100/250/500/1000
V DC. 0.5/2.5/10/55/50/100/250
500/1000V AC. Current: 50uA/0.5/
15/10/50/250mA/1/5A DC. 0.25/
0.5/15/10/50/250mA/1/5A DC. 0.25/
0.5/15/10/50/250mA/1/5A AC. Resistance: 0.5/10/100/200 ohms/1/3
Battery operated. Size: 210 x 115 x
90mm. Supplied in carrying case complete with leads.
11D 90IPF £15 01 9 P&P 200

OUR PRICE £15.00 P&P 20p





OUR PRICE £19.95

MODEL U4311 Sub-standard Multi-range Volt-Ammeter Sensitivity 330 Ohms/Volt AC and DC. Accuracy 0.5% DC. 1% AC. DC. 1% AC. DC. 1% AC. DC. 1565mm (J.300/750.4) 1.5/3/7.5/150/30/75/150/30/75/150/30/75/150/30/750mA/1.5/3/

P&P20

P&P 40p

30/75/150/300/ 750mA/15/3/ 7.5A DC. 0/3/ 7.5/15/300/750mA/ 1.5/3/7.5A AC. 0/75/150/300/750mV/1.5/3/7.5/15/ 0/75/150/300/750W DC. 0/750mW 15/3 /7.5/15/30/75/150/300/750V AC. Automatic cut out device. Supplied complete with test leads, manual and test certificates.

OUR PRICE £49.00

TE40 HIGH SENSITIVITY AC VOLTMETER

AC VOLIME 10
10 Meg input.
10 ranges: 0.001/
0.03/0.1/0.3/
1/3/11/30/100/
300V RMS.
5cps-1.2MHz.
-40 to +50dB supplied complete with leads and instructions.



OUR PRICE £17.50 P&P 25p

TE65 VALVE VOLTMETER

28 ranges. DC volts 1.5-1500V. AC volts 1.5-1500V. Resistance up to 1000 Megohms, 200/240V AC operation. Comoperation. Com-plete with probe and instructions.

OUR PRICE £17.50 Additional probes available RF £2.12, HV £2.50

LB3 TRANSISTOR TESTER

LB3 TRANSISTUM ILC.
Tests ICO and B.
PNP/NPN. Operates
from 9V battery.
Instructions supplied.
OUR PRICE P&P 20p

LB4 TRANSISTOR

12 Amp. 0/10K/ 1m/10m/100 Meg Ohms. – 20 to + 17 dB. OUR PRICE £12.50 P&P 20p.

MODEL AF.105 VOM 50,000 opv. Mirror scale. Meter protection. 0/-3/3/12/60/120/ 300/600/1200V DC. 0/6/30/120/ 300/600/1200V DC. 0/30µA/6/ 60/300 mA/

TESTER
Tests PNP or NPN
transistors. Audio
indication. Operates
on two 1.5V
batteries. Complete
with instructions etc. OUR PRICE

£4.50 P&P 20p U4341 Multimeter &

U4341 Multimetre & Transistor Tester 27 ranges. 16,700 pv. Charles By 16,700 pv. Charles

OUR PRICE £10.50 P&P 20p

KAMODEN HMG500

insulation resistance tester Range 0-1,000
Megohms, 500V.
Battery operated.
Wide range clear
meter 4"x 4%".
Complete with
deluxe carrying
case, batteries and

OUR PRICE £19.95

S100TR MULTIMETER TRANSISTOR TESTER

1MANSISTUM TE 100,0000pp. Mirror scale. Overload protection. 0/0.12/ 0.6/3/12/30/120/ 600V DC. 0/6/30/ 120/600V AC. 0/12/600V AC. 0/12/600V AC. 0/10/61 Meg/ 100 Meg. -20 to 450dB. 0.01-0.2 MFD. Transistor testor mea

ransistor tester measures Alpha, Beta nd ICO. Complete with instructions, atteries and leads.

OUR PRICE £15.95 P&P 25p

CI5 PULSE OSCILLOSCOPE

For display of pulsed and periodic wave forms in electronic circuits. VERT. AMP. Bandwidth: 10MHz. Sensitivity at 100kHz VRMS/mm; 0.1–25; HOR. AMP. Bandwidth: 500kHz Sensitivity at 100kHz Preset trimered ween

VRMs/mm: 0.3-25 Preset triggered sweep 1-3000usec. Free running 20-200 kHz in nine ranges. Calibrator pips. 220 x 360 x 430mm. 115-230V AC.

OUR PRICE £39.00 Carr. paid

RUSSIAN CI16 Double Beam OSCILLOSCOPE

SULTLUSCOPE

5 MHz pass band,
Separate Y1 and Y2

Separate Y1 and Y2

Calibrated tringered
sweep from 0.2usec.
to 100 millissec/cm.
Free running time
base, 50 Mz - 1 MHz.

Calibrator and amplitude Calibrator
and instruction manual
OILP DDICE C97 00.

OUR PRICE £87.00 Carr, paid

MODEL TE15 GRID DIP METER

Transistorised. Operates as Grid Dip, Oscillator, Absorbtion Wave Meter and Oscillating Detector. Frequency range 440kHz – 280MHz in six coils. 500uA meter. 9V battery operation. Size: 180 x 80 x 40mm.



OUR PRICE £19.95

Also see following pages

ALL PRICES **EXCLUDE VAT**

Top value 1,000 opv pocket multi-

P&P 15p

AUDIOTRONIC Model ATM5 MODEL HIOKI 730X

AUDIOTRUNIC Model A Jewel movement, attractively moulded case with edgwise ohms adjustment. Ranges: 0.3/15/150/300/1200V AC, (2500 opv). 0.6/30/300/600V DC, (3000 opv). 0.000 UA/0.300mA DC. Ranges: 0.300 opv). 0.000 UA/0.300 MC. 0.000 UA/0.000 UA/0.300 MC. 0.000 UA/0.300 UA/0.000 UA/0.300 UA/0.000 UA/0.300 UA/0.300 UA/0.000 UA/0.00

OUR PRICE £3.50

MODEL C1092 MULTIMETER

U4324 MULTIMETER High sensitivity, overload protected, 20,000opv, Ranges: 0.6/1.2/3/12/30 60/120/600/1200V DC. 3/6/15/60/150/3 30/600/900V AC. Current: 0.06/0.6/6 6/80/600mA/OAD AD. 3A AC. Resistence: 25/500 ohms/0.5/5/50/500k ohms/5 Mohms. Decibels: -10 to +12dB. Size 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions. **OUR PRICE £3.75**

MODEL U437 MULTIMETER

MODEL U437 MULTIMETER
10,000pw. A first
class, instrument
manufactured in
USSR to the highest
standards. Ranges:
2.5/10/50/250/
500/1000V DC.
2.5/10/50/250/
500/1000V DC.
2.5/10/50/250/
500/1000V DC.
4.5/10/50/250/
500/1000V DC.
4.5/1000V DC.
4.5/1000

OUR PRICE £4.95 P&P25p

MODEL TH12 20,000 pp. Overload protection. Slide switch selector. 0/0.25/2.5/10/ 50/150/1000V DC. 0/10/ 50/250/1000V AC. 0/ 50uA/25/250mA DC. 0/3k/30k/300k/3 Megohms. -20 to +50dB.

OUR PRICE £5.95 P&P 15p

HIOKI Model 720X VOM

A versatile, accurate measuring instrument. 20,000 opv. 0/5/25/100/500/1000V DC. 0/10,50/250/1000V AC. 0–50uA/250mA. 0–20k/2 Megohms. OUR PRICE £5.97 P&P 20p



MODEL PL436

0.000 opv DC. 8000 opv DC. Mirror scale -6/3/12/30/120/ 600V DC. 3/30/ 120/600V DC. 50/600μ Δ/60/



OUR PRICE £6.97 P&P 15p. OUR PRICE £10.50

OUR PRICE £8.00 TMK MODEL TW50K





P&P 15p

P&P 20n

OUR PRICE £8.50

DUR PRICE 68 75

P&P 17p U435 MULTIMETER

U435 MULTIMETER 20,000 pv. "verload protected. Ranges: 75m / 2.5 / 10.025 /

MODEL AS.100D 100,000 opv. Mirror scale. Built-in meter protection. 0/3/ 12/60/120/300/ 600/1200V DC. 0/6/30/120/300/ 600V AC. 0/10µA/ 6/60/300mA/ 12 Amp. 0/2K/ 200K/2M/20/ 00mm. = 20 to = 17 dB/ 01IR PRIFE F 17 d OUR PRICE £17.50 P&P 20p.

U91 Clamp VOLT AMMETER AMMETER
For measuring AC voltage and current without breaking circuit. Ranges: 300/600V AC. Current: 10/25/100/250/500A. Accuracy 4%. Size 283 x 4 x 36mm. Complete with carrying case, leads and fure.















H



and Simon

.. 6

1

SWR METER Model SWR3

JWYN IVIC I EM IVIODEI S
Handy SWR meter for
transmitter antenna alignment, with built-in field
strength meter. Accuracy
5%, Impedence 52' Indicator 100uA DC. Full
scale 5 section collapsible
antenna. Size 145 x 50 x
60mm.



OUR PRICE £4.25 P&P 25p

AT201 Decade **ATTENUATOR**

Frequency range 0 – 200kHz. Attenuator 0 – 111dB, 0.1dB steps. Impedence 600 ohms. Input power maximum 30dBm. Size: 180 x 90 x 55mm. **OUR PRICE £12.50** P&P 37p

TRANSISTORISED L.C.R. A.C. **BR/8 MEASURING BRIDGE**



BR/8 MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Ranges. 11 11.1 meg 6
Ranges: 11% L.1 H - 111.1
HENRY 6 Ranges 2 % C 10pF · 110mF 6 Ranges 2 % C 10pF · 110mF 6 Ranges 1 000 cps. Operated from 9 volts. 100 A Meter indication. Attractive 2 tone metal case. Size 7½ x 5 x 2in.

OUR PRICE £25.00 P&P 25p

TE16A TRANSISTORISED SIGNAL GENERATOR



OUR PRICE £8.97 P&P 25p

MODEL TE20 RF SIGNAL GENERATOR

GENEHA LUR Six bands. 120kHz-260MHz. Dual output RF terminals. Separate variable audio output. Accuracy ± 2%. Audio output to 8V. Power requirements: 105-125V, 220-240V AC. Size:193 x 265 x 150mm. Complete with test leade str.

OUR PRICE £17.50 P&P 40p TE-20D RF SIGNAL

GENERATOR GENERATUR
Accurate wide range signal generator covering 120 kHz-500 MHz on 6 bands.
Directly callbrated.
Variable R.F.

. 36 nuator audio output, Xtal socket for calibration. 220/240V Brand new with instruction Size 140mm x 215mm x 1

mm x 170mm OUR PRICE £17.50 P&P 30p

ARF 300 AF/RF SIGNAL

GENERATOR GENEKAIUH
All transistorised compact fully portable. AF sine-wave 18Hz to 220 kHz. AF square wave 18Hz to 100k Hz. Output Square/Sine wave 10V. P-P RF 100kHz to 200MHz. Output 1V maximum

1V maximum. 220/240V AC operation. Complete with instructions and leads. **OUR PRICE £29.95** P&P 50p

MODEL MG 100 SINE SQUARE WAVE AUDIO



GENERATOR Range 19-220,000Hz Sine

F

0

Wave 19—100,000 Hz Square Wave. Output Sine or Square wave 10v. P. to P Size 180 x 90 x 90mm.Operation 220/240v. A.C. DUR PRICE £19 95

MCA220 Automatic Voltage Stabiliser Input 88-125V AC or 176-250V AC. Output 120V AC or 240V AC. 200V/A rating. P&P 50

OUR PRICE £11.97 **PS100B** Regulated POWER SUPPLY UNIT

Solid state. Output 6, 9 or 12V DC up to 3 Amp. Meter to monitor current. Input 220/240V AC. Size: 100 x 82 x

OUR PRICE £11.97

PS200 Regulated POWER SUPPLY UNIT

Solid state. Variable output 5–20V DC up to 2 Amp. Independent meters to monitor voltage and current. Output 220/240V AC. Size: 190 x 136 x 98mm.

OUR PRICE £19.95

POWER RHEOSTATS

High quality ceramic construction. Wind imps embedded in imps embedded in Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing. W' diameter shafts. Bulk quantities available.

25 WATT 10/25/50/100/250/500/ 1000/2500 Ohms £1.15 P&P 10p 50 WATT 10/25/50/100/250/500/ 1000/2500/5000 Ohms. £1.62 P&P 10p

100 WATT 1/5/10/25/50/100/250/ 500/1000/2500 Ohms £2.34 P&P 15p

AUTO TRANSFORMERS

0/115/250V. Step up or step down. Fully shrouded.

£2.75 P&P 18p 80 WATTS £3.50 P&P 18p 150 WATTS P&P 23p £4.50 £6.95 500 WATTS P&P 33n £9.50 £12.50 £20.95 1000 WATTS P&P 38p P&P 43p 1500 WATTS 2250 WATTS P&P 50r £44.95 P&P £1 5000 WATTS

CP110 CHASSIS PUNCH SET



Carefully machined top grade steel. Contains 1/2", 5/8", 3/4", 1" and 1 1/8" punches complete with gripper

OUR PRICE £3.00 YAMABISHI VARIABLE

VOLTAGE TRANSFORMERS Excellent quality at low cost. Input 230V 50/60Hz. Output 0-260V. MODEL S260 BENCH MOUNTING

£10.50 £12.00 £17.50 £30.35 £33.75 £29.50 £85.00 £95.00 £120.00 30p 35p 37p 50p 75p 75p 125p 130p

MODEL S260B PANEL MOUNTING £10.00 30p £12.00 35p

240° Wide Angle 1mA METERS MW 1-6 60x60 £6.50 P&P 15p MW 1-8 80x80mm

£6.90 P&P 15p



BVD5 Vernier TUNING DIAL

BVD5 Verifier
App. 7: ratio planetary drive vernier dial. Log scale 0–180 degrees:
Blank scales 1–5.
Dial size 128 x 76mm. Oeerall size 190 x 117 x 41mm. deep including the hand coupling. W diam. shaft

OUR PRICE £1.62

WALKIE **TALKIES**

SKYFON 100mW OUR PRICE £24.95 per pair P302 Two Channel 300mV OUR PRICE £52.50 per pair 1003 Three Channel 1 Watt OUR PRICE £71.25 per pair P&P 50p per pair

NB. Licence required for use in UK

RUH6 Reflex Horn Speaker Built-in driver unit. Impedence 16 ohms. Power rating 10W. Response 380–7000Hz. Size app. 6" x 6". Weather and

OUR PRICE £4.97



Four bands covering 550kHz to 30 MHz continuous and electrical bandspread on 10, 15, 20, 40, and 80 mts. 8 valve plus 7 diode circuit, 4 to 8 ohm output and phone jack, SSB—CW, ANL, variable BFO, S Meter and separate band spread dial. IF frequency 445kHz, audio output 1½ watt. Variable RF and AF gain controls. 115/250V AC, with instructions.

Our Price £42.50 PARR

TRIO TR2200 TRANSCEIVER

Fully transistor-ised portable VHF transceiver Will transmit and receive on six channels between 144—146MHz. 144-146MHz.
1 watt transmitter. 12V DC
internal or external supply.
Built-in charger
for Ni-Cad cells.
Power/volume

vitch, squelch control, channel sel-

OUR PRICE £79.50 Carr.paid

BELTEK W5400 CAR TRANSCEIVER



Solid state mobile transceiver for 12 volt DC neg. Transmits and receives on any 12 of 28 channels between 144 and 146MHz. Power output 10W and 11W switchable. Controls: On/off volume, squelch and channel selector. Internal 3" speaker. Complete with dynamic mic. PTT switch, three sets of crystals for 144. 48, 144.6 and 145MHz. mounting bracket and instructions. Size: 150 x 70 x 220mm. OUR PRICE £75.00 P&P 50n DT55G DIGITAL CLOCK





Master and two sub-stations. Can be used on desk or wall mounted. Complete with cable and batteries **OUR PRICE £5.25**

LH02S STEREO HEADPHONES

Light weight head-phones with padded ear pieces. 4/16 ohms 20-20,000Hz. P&P 30p

TE1018 Deluxe Mono High Impedence Headset. Sensitive magnetic headset with soft ear pads. Impedence 2,60 ohms DC). Frequency response: 200-4,000Hz. 0

DHO2S STEREO HEADPHONES Wonderful value and excellent

OUR PRICE £2.50

Low cost with excellent response. Foam rubber earcups. Adjust able headband. 8 ohms

epie neadband. 8 ohms impedence. Frequency response 25Hz—18kHz. Complete with cable and stereo jack plus OUR PRICE £2.60

SH8DV MONO/STEREO HEADPHONES

Volume control for each channel. 4/16 ohms impedence. Frequency response 20Hz – 18kHz. Complete with 10ft. plug. OUR PRICE £4.97

BH001 HEADSET and Boom

Moving coil. Ideal for language

Model 350 13 x 8" with single tweeter/crossover. 20-20,000Hz. 15 watts RMS. Available 8 or 15 ohms. **OUR PRICE**

£7.25 each P&P 37p Model 450 13 x 8" with twin tweeter/crossover. 55–13,000Hz. 8 watts RMS. Available 8 or 15 ohm:

OUR PRICE £5.95 P&P 30p



P&P 50p

Complete with 6' lead and plug. OUR PRICE £1 97

OUR PRICE £2.25 P&P 30p

and excerning performance combined. Adjustable head band. Impedence 8 ohm 20–12,000Hz. Complete with lead and plug.

P&P 30p

TE1035 Stereo HEADPHONES

P&P 30p

P&P 30n

Microphone teachinic communications etc.
Headphone impedence 16.
Thone impedence 200 of 16 ohms. Mic

EMI LOUDSPEAKERS 60:0



HIGH QUALITY CONSTRUCTION KITS

WE ARE APPOINTED STOCKISTS AT ALL BRANCHES

All kits are complete with compresy to follow instructions and

covered by full guarantee.

st and Packing 15p per kit.	
F20 Mono amplifier	£4.8
F25 Mixer	£3.6
F30 Mono pre-amplifier	£2.6
F35 Emitter amplifier	£2.2
F80 0.5W mic, amplifier	£4.2
F305 Intercom	£9.5
F310 Mono amplifier	£5.9
T5 Automatic light control	£2.5
T25 Window wiper robot	£5.8
T30 Photo cell switch unit	£5.7
T50 400W triac light	
dimmer/speed control	£4.8
T56 2,200W triac light	
dimmer/speed control	£6.9
T60 1 channel light control	£7.8

AT56 2,200W triac light dimmer/speed control... £6,90 AT601 channel light control... £7,80 AT601 channel light control... £1,85 GP304 Circuit board... £1,80 GP310 Stereo pre-amplifier £4,94 GP310 Stereo pre-amplifier £4,94 GP310 Stereo pre-amplifier £1,45 GU330 Tremolo unit... £7,50 HF61 Diode detector... £3,32 HF65 FM transmitter... £2,70 HF75 FM receiver... £2,81 HF326 Diode detector... £2,81 HF326 Diode detector... £2,81 HF326 Diode detector... £2,81 HF326 Diode detector... £2,81 HF330 Decoder (HF310/325) E9,96 HF7326 Diode detector... £2,81 HF330 Decoder (HF310/325) E9,96 HF380 Illy Alfon FM turner... £24,12 HF330 Decoder (HF310/325) E9,96 HF380 Illy Alfon derial amp. £1,77 LF380 Cuadraphonic device... £1,35 M160 Multi-vibrator... £2,75 M1302 Transistor tester... £8,45 M170 Stabilised power supply 100mA, 9V... £8,15 M170 Stabilised power supply 100mA, 9V... £6,15 M170 Stabilised power supply 240V AC to 4,5/15V DC, 500mA... £9,57 Amateur Electronics by Josty-Kit.

Amateur Electronics by Josty-Kit, the professional book for the amateur covers the subject from basic principals to advanced electronic techniques. Complete with circuit board for AE1 to AE10.

OUR PRICE £3.30 (No VA ⁻ P&P 25p plus VAT.	r)
AE1 100mW output stage	£1.65
	£1.26
AE3 Diode receiver	£2.00
AE4 Flasher	£1.09
AE5 Astable multi-vibrator	£1.05
AE6 Monostable multi-vibrator	
	£1.06
AE7 RC generator	
AE8 Bass filter	99p
AE9 Treble filter	99p
AE10 CCIR filter	99p



No Soldering required. All connect-made with spring clips. Kit includes all parts and wire including ear-piece. Will receive all normal broadcasts on Medium Wave 535-1605kHz. Oper-ates from standard 9V battery or Solar Cell included.

OUR PRICE £1.30 P&P 30p

SPECIAL BARGAIN!! STEREOSOUND SPEAKERS

STEREOSOUN
Matched pair of
stereo bookshelf
speakers. Deluxe
teak veneered
finish. Size:
368 x 229 x
190mm. 8 ohms.
8 watts RMS, 16
watts peak.
Complete with
Din lead.



P&P 50p

OUR PRICE £12.95 SPECIAL BARGAIN FERGUSON

SPEAKERS High quality 2 way speaker systems. 25 Watts. 4-8 ohms. 40Hz-18kHz. Size: 560 x 340 x 255mm. approx. Wood grain finish with black fronts. OUR PRICE £26.95 PR. P&P £1

Model A1018 **FM TUNER** 6 transistor high quality unit— 3 IF stages and double tuned

discriminator. For use with most amplifiers. Covers 88–108MHz. Powered by 9V battery. OUR PRICE £13.50 P&P 30p



EW CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.

Over 200 ranges in stock-other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

CLEAR PLASTIC MODEL SD640

50uA	£3.80	
100u A	£3.75	
200u A	£3.70	i li
500uA	£3.65	1 ' 1
50-0-50u A	£3.75	1 ≜ 1
100-0-100uA	£3.70	
1mA	£3.65	
5mA	£3.65	=
10mA	£3.65	
50mA	£3.65	
100mA	£3.65	20V DC £3.65
500mA	£3.65	50V DC £3.65
1A DC	£3.65	300V DC £3.65
5A DC	£3.65	15V AC £3.75
10A DC	£3.65	300V AC £3.75
5V DC	£3.65	VU Meter £3 90

CLEAR PLASTIC MODEL SW100 Size: 100 x 80mm

50uA	£4.60	
100uA	£4.50	
500u A	£4.30	1 .
50-0-50u A	£4.50	۸ .
100-0-100u A	£4.45	=
1mA	£4.30	Action
1A DC	£4.30	
5A DC	£4.30	7
20V DC	£4.30	
50V DC	£4.30	300V AC £
300V DC	£4.30	VU Meter f

EDGWISE MODEL PE70

O120: 00 11 0 111111	
50uA	£4.15
100uA	£4.10
200uA	£4.05
500uA	£3.90
50-0-50u A	£4.10
100-0-100u A	£4.05
1mA	£3.85
300V AC	£3.95
VU Meter	£4.30



MODEL ED107 EDUCATIONAL METER Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experi-ments and other bench applications. 3" mirror scale. The meter move-ment is easily accessible to demonstrate internal working.



A DC	 	£7.60	\	
A DC	 	£7.60		
/ DC	 	£7.60	300V DC	£7.60
V DC	 	£7.60	500mA/5A DC	£8.60
V DC	 	£7.60	5V/50V DC	£8.60
V DC	 	£7.60	5V/15V DC	£8.60
OV DC	 	£7.60	1A/15A DC	£8.60

CLEAR PLASTIC MODEL MR 85P

50uA	£5.45
100uA	£5.40
200u A	£5.35
500u A	£5.25
50-0-50u A	£5.40
100-0-100uA	£5.35
500-0-500u A	
1mA	£5.20
1-0-1mA	£5.20
5mA	£5.20
10mA	£5.20
50mA	£5.20
100mA	£5.20
500m A	£5.20

SINCLAIR Project 80 Modules

SINCL AIR Project 80
240 Power Amplifier.
260 Power Amplifier.
Stereo 80 Pre-Amplifier.
Active Filter Unit.
Project 805.
PZ5 Power Supply.
PZ6 Power Supply.
PZ78 Power Supply.
Transformer for PZ8.....



15.20		
£5.20		
£5.20	January and	
£5.20		
£5.20		
£5.20	300V DC	£5.2
£5.20	15V AC	£5.3
£5.20	300V AC	£5.3
£5.20	S Meter 1mA	£5.2
£5.20	VU Meter	£5.5
£5.40	1A AC	* £5.2
£5.20	5A AC	* £5.2
£5.20	10A AC	* £5.2
£5.20	20A AC	* £5.2
£5.20	30A AC	* £5.2

. £5.45 . £6.95 ..£11.95 . £6.95 . £26.95 . £4.98 . £7.98 . £7.98

1021 Stereo Listening Station

For balancing and gain selection of loudspeakers of loudspeakers with additional facility for stereo headphone 0... sadphone vitching. Two ain controls, speakers on-off slide stereo headphone socket. **OUR PRICE £2.25** P&P 15t

> 10 £3.00 £4.25 £5.17 25 £7.08 £10.00 £12.24

£7.72 £19.12 £10.46 £25.22

SINCLAIR Project 80 Packages 2 × Z40/Stereo 80/PZ5£25.00	OUR PRICE £2.25 P8
2 x Z40/Stereo 80/PZ6 £27.75 2 x Z60/Stereo 80/PZ8 £30.45 POST & PACKING 35p each.	AUDIOTRONIC LOW NOISE CASSETTES
MP7 MIXER-PREAMPLIFIER 5 Microphone inputs each with individual gain controls enabling complete mixing	TYPE 5 10 C60 £1.57 £3.00 C90 £2.24 £4.25 £ C120 £2.73 £5.17 £ AUDIOTRONIC CrO2 CASSETTES

AUDIOTRONIC

8 TRACK CARTRIDGES

Each 85p £1.15 5 £4.00 £5.40

P&P Cassettes 3p, Cartridges 5p each OVER 10 of either POST FREE!

complete mixing accilities. Battery operated. Size: 235 x 127 x 76mm. Inputs: Mics. 3 x 3mV slob; 2 x 3mV 600 ohms. Phono. Mag. ImV 50k; Phono Ceramic 100mV 1 Meg. Output 250mV 100k. OUR PRICE £8.97



*Items with asterisk are Moving Iron type, all others are Moving Coil

CLEAR PLASTIC MODEL SD830

LEAD LLW9		DEF 20020	
Size: 110 x 83m:	m		
50uA	£4.30		_
100uA	£4.25		٦
200u A	£4.20		l
500uA	£4.15		ı
50-0-50u A	£4.25	· ·	И
100-0-100u A	£4.20		_
lmA	£4.10		
5mA	£4.10		
10mA	£4.10	-	=
50mA	£4.10	10V DC £4	. 1
100mA	£4.10	20V DC £4	.1
500mA	£4.10	50V DC £4	.1
IA DC	£4.10	300V DC £4	
5A DC	£4.10	15V AC £4	.2
10A DC	£4.10	300V AC £4	.2

CLEAR PLASTIC MODEL MR 45P

50u A	£3.20	
100u A	£3.15	(
200u A	£3.10	
500u A	£3.00	1 2000
50-0-50u A	£3.15	***
100-0-100u A	£3.10	
500-0-500u A	£2 95	_ • \ <u>_</u>
1mA	£2.95	31111(D)
5mA	£2.95	
10mA	£2.95	
50mA	£2.95	(0.1111111)
100mA	£2.95	-
500mA	£2.95	300V AC
1A DC	£2.95	S Meter 1m
5A DC	£2.95	VU Meter
10V DC	£2.95	1A AC
20V DC	£2.95	5A AC
50V DC	£2.95	10A AC
300V DC		20A AC
	£2.95	
15V AC	£3.05	30A AC



S Meter 1mA	£2
VU Meter	£3
1A AC	* £2
5A AC	* £2
10A AC	* £2
20A AC	* £2
30A AC	* £2

CLEAR PLASTIC MODEL MR 38P

	50uA		 £3.10			
	100u A		 £3.05	6		
	200u A		 £3.00	- 1	,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,	
	500u A		 £2.85	- 1	2	
	50-0-50u		 £3.05	- 1	*122E	
	100-0-100	υA	£3.00	- 1	1	- 7
	500-0-500	υA	 £2.80		•	٠.
	1mA		 £2.80	lin:	unite	
	1-0-1mA		 £2.80	10		
	2mA		 £2.80	i i		
	5mA		 £2.80	2)	11111	
	10mA		 £2.80	•		
	20mA		 £2.80	15V	DC	
	50mA		 £2.80	20V		
	100mA		 £2.80	50V		
	150mA		 £2.80	100\		
	200mA		 £2.80	150V		
	300mA		 £2.80	300		
	500mA		 £2.80	500		
	750mA		 £.280	750V		
	1A DC		 £2.80	15V		
١	2A DC	•••	 £2.80	50V		
	5A DC		 £2.80	150\		
	10A DC		 £2.80			
	15A DC		 £2.80			
	3V DC		 £2.80			
	10V DC		 £2.80			
			 	. •		

f2.80 f2.80 15V DC f2.80 f2.80 20V DC f2.80	0
£2.80 20V DC £2.80	0
	0
£2.80 50V DC £2.80	
£2.80 100V DC £2.80	0
£2.80 150V DC £2.80	٥
£2.80 300V DC £2.89	5
£2.80 500V DC £2.89	5
£.280 750V DC £2.90	o
£2.80 15V AC £2.90	0
£2.80 50V AC £2.90	Ò
£2.80 150V AC £2.90	o
£2.80 300V AC £2.90	0
£2.80 500V AC £3.00	o
£2.80 S Meter 1mA £2.80	o
£2.80 VU Meter £3.20	n

CLEAR PLASTIC MODEL SD460

126. 33 x 4011111		
50uA	£3.50	
100uA	£3.45	
200u A	£3.40	1 h
500uA	£3.35	· Andrews to the same
50-0-50u A	£3.45	1 A H
100-0-100u A	£3.40	1
ImA	£3.30	
5mA	£3.30	
10mA	£3.30	=
50mA	£3.30	
100mA	£3.30	10V DC £3.30
500mA	£3.30	50V DC £3.30
1A DC		
	£3.30	300V DC £3.30
5A DC	£3.30	15V AC £3.45
10A DC	£3.30	300V AC £3.45
5V DC	£3.30	VU Meter £3.65
	L U.30	* C

5mA 10mA 100mA 100mA 500mA 1A DC 2A DC 5A DC 15A DC 15A DC 50A DC 50A DC 50A DC 50A DC 50A DC 15OV DC 15OV DC 15OV DC POSTAGE & PACKING 15p

AUDIOTRONIC AHA101

Stereo Headphone Amplifier



sereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. INPUTS: 5mV and 100mV. OUTPUT: 50mV per channel.

OUR PRICE £8.50

HITACHI FLUORESCENT LANTERN LI901

motoring, campi etc. Approx. 10' tall. Provides ied). OUR PRICE £7.90

P&P 25p



200uA	£3.80	Vertical I
500uA	£3.75	
50-0-50u A	£3.85	* A *
100-0-100uA	£3.80	\ ~-L
500-0-500uA	£3.70	
1mA	£3.70	
5mA	£3.70	
10mA	£3.70	
50mA	£3.70	(Silililia)
100mA	£3.70	
500mA	£3.70	50V AC £3.80
1A DC	£3.70	150V AC £3.80
5A DC	£3.70	300V AC £3.90
10A DC	£3.70	500V AC £3.80
15A DC	£3.70	S Meter 1mA £4.10
20A DC	£3.80	VU Meter £3.70
30A DC	£3.85	1A AC * £3.70
50A DC	£4.05	5A AC * £3.70
5V DC	£3.70	10A AC * £3.70
10V DC	£3.70	20A AC * £3.70
20V DC	£3.70	30A AC * £3.70
50V DC	£3.70	50mA AC * £3.70
150V DC	£3.70	100mA AC * £3.70
300V DC	£3.70	200mA AC * £3.70
15V AC	£3.80	500mA AC * £3.70
101110 11 11	10.00	550mA A5 :: 25175
RAKELITE M	ODEL S	80 Enlarged Window

CLEAR PLASTIC MODEL MR 65P

Size: 80 x 80mm

OILE: OU A	00	
50uA		£4.50
100u A		 £4.45
500uA		 £4.20
50-0-50u A		£4.45
100-0-100	luΑ	 £4.40
1mA		 £4.20
1A DC		 £4.20
5A DC		 £4.20
20V DC		 £4.20
50V DC		 £4.20
300V DC		 £4.20
300V AC		 £4.30
VU Meter		 £4.70
300V DC 300V AC		 £4.20



CLEAR PLASTIC MODEL MR 52P

Size. Oo x comin		
50uA	£3.70	
100u A	£3.50	(
500u A	£3.35	1
50-0-50uA	£3.50	1
100-0-100u A	£3.45	12° 44
1mA	£3.30	\ -
5mA	£3.30	L
10mA	£3.30	William I
50mA	£3.30	
100mA	£3.30	
500mA	£3.30	Carlina
1A DC	£3.30	
5A DC	£3.30	S Meter 1mA
10V DC	£3.30	VU Meter
20V DC	£3.30	1A AC *
50V DC	£3.30	5A AC *
300V DC	£3.30	10A AC *

(2011)	
S Meter 1mA	£3.30
VU Meter	£3.80
1A AC	* £3.30
5A AC	* £3.30
10A AC	* £3.30
20A AC	* £3.30
30A AC	* £3.30
30A AO	20.00

£3.30 £3.30 £3.30 £3.40 £3.40 BAKELITE MODEL MR 65 Size: 80 x 80n 25uA 50uA 100uA 500uA ... 50-0-50uA 100-0-100uA ... 500-0-500uA

	III OJ OLEC. COX	
£5.25		
£4.00		~
£3.95		_
£3.65		
£3.95	**	`
£3.90	0.4	3
£3.60		-4
£3.60		
£3.60		
£3.60		
£3.60		
£3.60	30V AC '	£3.6
£3.60	50V AC 1	£3.6
£3.60	150V AC '	£3.6
£3 60	300V AC 4	. t3 E

23.00			_
£3.60		-	-
£3.60	30V AC		* £3.60
£3.60	50V AC		* £3.60
£3.60	150V AC		* £3.60
£3.60	300V AC		* £3.60
£3.60	500V AC		£3.60
£3.60	VU Meter		£4.10
£3.60	1A AC		* £3.60
£3.60	5A AC		* £3.60
£3.80	10A AC		* £3.60
£3.60	20A AC		* £3.60
£3.60	30A AC		* £3.60
£3.60	50A AC		* £3.60
£3.60	500mA AC		£3.60
£3.60	50mV DC		£3.75
£3.60	100mV DC		
13.60	100mv DC	••	£3.75

EA41 REVERBERATION

AMPLIFIER Self contained, 9 battery operated.
Simply plug in microphone, guitar etc. and output to your amplifier. Volume control and depth of reverberation control. Beauwalnut cabinet. 184 x 77 x 108mm. P&P 20p **OUR PRICE £7.50**

SPECIAL PURCHASE LIMITED QUANTITY Tannoy 12" DR/8 Bass Speakers 8 ohms, 30 watt Heavy duty, ideal for Hi-Fi P.A.

OUR PRICE £12.50. P&P 50p.

FREE HI-FI PRICE LIST

Send large S.A.E. for our latest Hi-Fi Price List containing over 2,000 items of Hi.Fi, P.A., In Car, Radio, T.V., Tapes Cassettes etc.

CALL INTO YOUR **NEAREST LASKYS** BRANCH OR ORDER WITH CONFIDENCE BY MAIL ORDER

CENTRAL LONDON

481 OXFORD ST. (Opening late April)				
10 TOTTENHAM CT. RD.	01-637 2232			
27 TOTTENHAM CT. RD.	01-636 3715			
33 TOTTENHAM CT. RD.	01-636 2605			
42/45 TOTTENHAM CT. RD.	01-636 0845			
87 TOTTENHAM CT. RD.	01-580 3739			
257/8 TOTTENHAM CT. RD.	01-580 0670			
3 LISLE ST. WC2	01-437 8204			
34 LISLE ST. WC2	01-437 9155			
118 EDGWARE RD. W2	01-723 9789			
193 EDGWARE RD. W2	01-723 6211			
207 EDGWARE RD. W2	01-723 3271			
311 EDGWARE RD. W2	01-262 0387			
346 EDGWARE RD, W2	01-723 4453			
382 EDGWARE RD. W2	01-723 4194			
109 FLEET ST. EC4	01-353 5812			
152/3 FLEET ST. EC4	01-353 2833			

ESSEX

ГН	ST.	ROMFOR	D	70-2021

KENT

86 SOU

53/57 CAMDEN RD., TUNBRIDGE WELLS 0892-23242

LEICESTERSHIRE

45 MARKET PLACE, LEICESTER 0533-537678

SURREY

1046 WHITGIFT CENTRE, CROYDON 27 EDEN ST. KINGSTON 32 HILL ST. RICHMOND

WARWICKSHIRE 116 CORPORATION ST., BIRMINGHAM

(Opening shortly)

ALL BRANCHES OPEN FROM 9am to 6pm MON. TO SAT.

HEAD OFFICE AND MAIL ORDER DEPARTMENT

AUDIOTRONIC HOUSE. THE HYDE INDUSTRIAL ESTATE, THE HYDE, LONDON NW9 6JJ. TELEPHONE: 01-205 3735 & 5651

MAIL ORDER SPECIALISTS

MAIL ORDER SPECIALISTS
We offer a speedy and efficient
service by mail order.
Remember to add 10 ... VAT to
total value of goods including
carriage and packing and send
cash with order to head office.
TO AVOID DELAYS PLEASE
PRINT NAME AND ADDRESS
CLEARLY IN CAPITALS.



BARCLAYCARD & ACCESS

Holders welcome call into any branch or telephone your order to head office.
CREDIT TERMS available for Personal Shoppers on sales of

BARGAIN CENTRE

Many special clearance offers and end of stock lines at 87 TOTTENHAM COURT RD. FOR PERSONAL SHOPPERS.

EXPORT Personal exports arranged for overseas visitors at all our branches. Goods despatched to all parts of the world through our Export Mail Order Department. Immediate attention given to

CHEQUES ACCEPTED FROM PERSONAL SHOPPERS ONLY WITH BANKERS CARD.

All prices correct at 13-3-74 but subject to change

A member of the Audiotre Group of Companies



A ready built unit, ready for connection to the I.F. stages of existing F.M. Radio or Tuner. A tell tale light can be connected. The unit is a small printed circuit, no further alignment necessary. A L.E.D. is recommended as the indicating light, suitable device available from us at 36½p. Instructions included

or 2 on one board for £2.86 Order Code 1.C.A.1/S

These amps. are supplied with a free booklet on connecting up, specifications and easy to build projects using the I.C.A.1



& 10W AM



5Wonly £1.98 10W ONLY £2.49

incl. P. & P. and V.A. T These matchbox size amplifiers have an exceptionally good tone and quality for the price. They are only $2\frac{1}{4}$ " x $1\frac{3}{4}$ ". The 5W amp will run from a 12V car battery making it very suitable for portable voice reinforcement such as public functions. Two amplifiers are ideal for stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit. Discounts are available for quantity orders. More details on request. Cheapest in the UK. Built and tested.

Now available for 5 & 10W AMPS

Pre-assembled printed circuit boards 2" x 3" available in stereo only, will fit ·15 edge connector.

Stereo Pre-Amp 1 (Pre 1). This unit is for use with low gain crystal or ceramic pick-up cartridges.

Stereo Pre-Amp 2 (Pre 2). This unit is for use with magnetic pick-up cartridges.

Stereo Tone Control (STC). This unit is an active tone control board and when used with the right potentiometers £1 · 21 will give bass and treble boost and cut.

Instruction leaflet supplied with all units. Post and packing and VAT included in prices.

<i>_</i>
I enclose £ for Decoders/
3W Amps/ 5W Amps/ 10W Amps/
Stereo Pre-Amps 1 Stereo Pre-Amps 2
Stereo Tone Controls
(Please insert quantities and delete those not applicable)
Name
Address

Co. Regn. No.820919

BI-PRE-PAK Dept. D, 222/224 West Road, Westcliff-on-Sea, Essex SS0 9DF Telephone: Southend (0702) 46344

Trannies

4 Bush House. Bush Fair, Harlow, Essex.

- * PRICES INCLUSIVE OF V.A.T.
- ★ Retail Shop open 9 to 5.30 Mon to Sat.
- ★ Post & Package 12p.
- ★ 1974 Catalogue 20p.
- ★ Tel. Harlow 37739.

everyday electronics construction kits

- Kits contain electronic parts only -

Slave Flash	£1 · 85	Tute
Electronic Door Bell	£4.00	VCC
Waa Waa	£1.50	F.E.
Personal Receiver	£3-10	Sew
Aquarium Thermosta	t	C
	£2.85	4 Ba
Train Controller	£3 · 15	
Light Dimmer	£3·50	Pow
Baby Snatch Alarm	£8.80	Slid
Stereo Headphone A	daptor	Eme
	£1 85	Spec
Gas Alarm	£6.60	Plan
Auto-water for Plants	€2.25	A.F.
Tremolo Unit	£2·10	1

-	
Tutor Board	£7·20
VCO Effect Unit	£3·80
F.E.T. Receiver	£2.00
Sewing Machine Spee	d
Control	£1 · 45
4 Band T.R.F. Receive	r
	£12.00
Power Supply Unit	£7·85
Slide Projector Unit	£2 · 00
Emergency Lighting	£7.00
Speed Guard	£3.60
Plant Propagator	£5 · 00
A.F. Oscillator	£6.60
71111	

TRANSISTOR ASSISTED IGNITION LIGHT POWERED RECEIVER **ELECTRONIC VOLTMETER**

for kits in this months issue send the quoted approximated cost of components in box-reprint of any project 20p.

£1 BARGAIN PACKS

- 10 Silicon NPN Power Transistors (2N3055) tested/unmarked.
- 30 Plastic FET's unmarked/ untested, similar to 2N3819.
- 20 TO5 transistors NPN or PNP, state which. 2 to 5 amp untested/unmarked.
- 20 TO18 transistors PNP like BC178, BC179 etc. untested/unmarked.
- 30 Plastic 2N3055 un-
- 10 General Purpose, fully tested FET's.
- 500 carbon resistors \$\frac{1}{4}\$, \$\frac{1}{2}\$, I. 2 watt.
- 100 Electrolytic condensers.
- 250 Ceramic Polystyrene, Silver Mica etc. Conden-
- Polyester, Polycarbonate, Paper, etc. condensers.
- 25 Potentiometers assorted.
- 250 High Stab 1%, 2%, 5% resistors.
- £1 IIb Assorted nuts, bolts, washers, spacers, etc.
- 25 Assorted Switches, rotary, lever, micro, toggle,
- £1 50 Preset Potentiometers.

★any 5 packs £4.50

P/P 25p for each pack



We have been appointed stockist of Amtron high quality construction kits.

UK65 Transistor tester £1 · 89 UK92 Telephone Amplifier

£7·91 UK110 Stereo Amp. 4 UK220 Signal injector UK230 AM/FM Antenna £3·23 Amplifier

UK300 Four channel Radio Control Transmitter

UK310 Radio control Receiver £3 · 28

UK325 "GCX2" channel splitting unit 1000 and 2000 Hz £7-86

splitting unit 1500 and 2500 Hz £7 · 86 UK345 Superheterodyne radio

control receiver £6.55 UK415 Resistor Box £8 · 69 UK425 Capacitor Box £8·39

UK525 VHF tuner 120 to 160mHz £ £12.44 160mm2 UK540 LW/MW/FM tuner £27-54

UK790 Capacitive Burglar

UK835 Guitar pre-amplifier

UK875 Capacitive discharge electronic ignition for internal combustion engine £14.51 engine

★Many other kits available.★ Send for the free Amtron catalogue.

We also stock a large range of electronic semiconductor at competitive price. Our new 74 catalogue is now available

DON'T RELY ON YOUR MEMORY BUY NOW AT BARGAIN PRICES

Hi Fi and Transistors - Up to date Brochures on request



TEST EOUIPMENT



MULTIMETERS

(carr. etc. 30p)	
ITI-2 20K/Voit Slimline	5.95
M210 (Case £1.25) 20K/Volt Slimline de-luxe	6.75
TLH33D 2K/Volt Robust	7 · 50
U437 10K/Volt Steel case. AC up to 40 KH	
U4324 20K/Volt with AC current ranges	8 - 00
AF105 (Case £1.90) 50K/Volt	11 . 95
U4313 20K/Volt AC current. Steel case	10.50
U4341 Plus Built in transistor tester	10 - 50
Model 500 (Case £1.95), 30K/Volt	9 · 95
OTHER EQUIPMENT	

OTHE	R EQUIPMENT			
SE250B	Pocket Signal Injector	2.10	carr.	15p
SE500	Pocket Signal Tracer	1.70	carr.	15p
TE15 ·	Grid Dip meter 440kHz-			
	280mHz	15.00	carr.	30p
TE40	AC Millivoltmeter 1 · 2mHz	19.75	carr.	35p
TE65	28 Range valve voltmeter	22.50	carr.	40p
TE20D	120kHz-500mHz RF Genera	tor		
		18 . 95	carr.	40p
TE22D	20Hz-200kHz Audio Gener		15	
		19.95	carr.	40p
SE350A	Deluxe Signal Tracer	12.50	carr.	20p
SE400	Volts/ohms/R-C sub./			
	RF field/RF gen.	14.75	carr.	20 p

New Revolutionary Supertester 680R



Accessories Transistor tester Transistor tester
Elactronic voltmeter
Ampclamp
Temperature probe
Guass meter
Signal Injector
Phase Sequence
EHT Probe
Shunts 25/50/100A 18 · 00 11 · 95 11 · 95 11 · 95 5 · 95 5 · 95

A CELECTION OF INTERESTING ITEMS

A SELECTION OF INTERESTING ITEMS
C3025 Compact transistor tester 6.95 p & p 15p
Q4002 Photoelectric System £13.70
E1310 Stereo mag. cart. preamp. 4.80 p & p 25p
Easiphone D1201 telephone amplifier 7 50 p & p 25p
D1203 Teleamp, with PU coil 4.95 p & p 20p
LL1 Door Intercomm. and chime 8.40 p & p 25p
1 Kw Dimmer/controller 3.00 p & p 10p
9" Twin spring unit For 3.30 p & p 15p
16" Twin spring unit Reverbs 6.85 p & p 25p
US50 Ultrasonic Switch Transmitter/Receiver £12.75
C3041 1-250 MHz £4·25
C3043 5CH 1-300 MHz £5.75
VHF 105 Aircraft Band Convertor 4.50 p & p 15p
B2005 4 Ch. mic. mixer 4.20 p & p 15p
B2004 2 ch. Stereo mixer 6.75 p & p 15p
PK3 Kit. Etch your own circuits £1.95 p & p 20p

BUILD THIS RADIO

Portable MW/LW radio kit using Mullard RF/IF module. Features MW—bandspread for reatures MV—bandspread for extra selectivity. Slow motion tuning. Fibre glass PVC cabi-net. 600MW output. All parts £7:98 (battery 22p), carr. etc.



EVOLUCIVE, CDECIAL OFFED

EXCLUSIVE: S	PECIAL OFFERS
MW/LW CAR RADIO	
+ or - Earth with speaker	Stereo Amplifier (List
and fixings. £6.50 carr./	£52·00) £34·52.
packg. 30p.	Wein W500 Battery/Mains
8 TRACK CAR STEREO	
(- Earth) with speakers in	
Pods & fixings. £12.50	
carr/packg. 40p.	£59 95 carr/packg. 50p.
Portable Battery Cassette	
	phones. £6.95 carr/packg.
Car Lighter Plug and adaptor	
for all cassette and radio	
6/7½/9 volt output (state	
width) £1.95 each	for car or carry around. £7.25
Rotel Stereophones	carr/packg. 20p.
	HANIMAX BC808 POCKET
	CALCULATOR WITH
RH430 £3·30	% KEY. £28.95 (continued)

SPECIAL PURCHASES

HANIMAX BC811M MEMORY VERSION MAINS UNIT for BC808, BC811M £37·50 £2·85 HANIMAX H101 STEREO COMPACT RECORD PLAYER 2 x 7 watts. Complete with Speakers (List £54·50) Price £39·95. Plus free pair of stereo phones.

£54-50) Price £39-95. Flus no pull the TV TUNERS CHANNELS 21 TO 64 Brand new transistorised geared tuners for 625 Line Receiver IF output. £2-50,



EASY TO BUILD KITS BY AMTRON—EVERYTHING SUPPLIED

Mod	el No.	
310		2.98
300	4-channel R/C transmitter	5.95
345	Superhet R/C receiver	5.95
455	AM signal generator	12.33
65		1 · 40
115	8 watt Amplifier	3.90
120	12 watt amplifier	4.70
125	Stereo control unit	5 · 70
130	Mono control unit	3.60
605	Power supply for 115	4.55
610	Power supply for 120	4 - 55
615	Power supply for 2 x 120	5.73
230	AM/FM aerial amplifier	2.93
240	Auto packing light	5.90
275	Mic. preamplifier	6.08
570	LF generator 10Hz-1mHz	15.80
575	Sq. wave generator 20Hz-20Khz	14-60
590	SWR meter	12.85
620	Ni-CAD Charger 1 · 2-12v	8.00
630	STAB Power supply 6-12v 0·25-0-1 A	8 - 15
690	DC motor speed Gov.	2.87
700	Electronic Chaffinch	7.00
705	Windscreen wiper timer	6.80
760	Acoustic switch	10.75
780	Metal Detector (electronics only)	9.65
790	Capacitive Burglar alarm	6.85
835	Guitar preamp.	4 - 25
840		6-15
875	CAP. Discharge ignition for car engine	
0,0	(-Ve Earth)	13-15
80	Scope Calibrator	2 . 25
255	Level indicator	6-15
525	120-160mHz VHF timer	11.30
715	Photo cell switch	7.70
795	Electronic continuity tester	4.30
860	Photo timer	13 - 25
871	Slide projector auto feed control	7.15
235	Acoustic Alarm for driver	7.60
465	Quartz XTAL checker	8 - 75
220	Signal Injector	2 . 30
390	VOX	15.50
432	Testakit	19 - 30
670	Buffer Battery Charger	6 - 55
885	Capacitive Contact Alarm	6 - 25
850		18 - 75
820	Electronic Digital Clock	58 - 50
020	ALL KITS OF	
	SUBJECT TO	
	STOCK STOCK	,
	AVAILABILIT	TV
1	AVAILABILI	

Prices correct at time of preparation. Subject to change without notice.

BUILD THIS TUNER

MW/LW Radio Turner to use with any amplifier. Features Mullard RF/IF module Ferrite aerial, built in battery. Excellent results. Size 7" x 2\frac{2}" x 3\frac{7}{4}". All parts £4.85, carr. 15p.

MUL	.TI-USE &	RADIONIC	KITS
10-1	10 Projects		3 - 60
50-1	10 Projects	事 事 化二烷二烷二烷	8.00
1E0 1	150 Projects		42.90

10-1	10 Projects		3.6
50-1	10 Projects		8.0
150-1	150 Project	s	13 · 2
Telepi	hone Commun	nicator	7.2
X20	20 (Elec.)	Projects	4.9
X40	40 (radio)	Projects	9 - 4
(carr./	packing 40p)	•	
Allt	rancietoro	ircuite with han	d books

TBA800 5 WATT I.C.
Suitable alternative to SL403D.
5/30 volt operated. 8/16 ohm
5 watt output.
With circuits and data £1.50.





ST2 (D32) DIAC 25p CRS1/40 SCR 45p. ZFT4 £3 00 ZFT8 £3 50 ZFT12 £4 50

HENRY'S CATALOGUE

Due to rapid price changes, shortages of paper and raw materials, all prices in the existing catalogues no longer apply. Call or phone for latest prices. A new catalogue will be available for Aug/Sept. 1974.

UK'S LARGEST RANGE OF TRANSISTORS AND DEVICES

JUST A SELECTION *TBA800 5 Watt IC *Sinclair ICR 6 Watt IC *Sinclair ICR 6 Watt IC *ZN4141C Radio *Ultrasonic Transducers *3015F 7SEG Indicator TIL 209 LED * With circuits/data sheet

£1·50 £1·80 £1·20 £5·90 pr. £1·70 24p each. 22p each per 10

with circuits/data sheet
OVER 1590 DIFFERENT SEMI - CONDUCTOR
DEVICES IN STOCK
Free stock list—latest edition (Ref. 36) on request.
Includes radio valves, I.C.'s Rectifiers, Triacs, SCR's,
LED's, etc. More types—better prices—discounts for
quantity small or large.

GARRARD BATTERY TAPE DECK



GARRARD 2 speed 9 volt tape decks. Fitted record / play and oscillator/Erase heads. Wind and rewind controls. Takes up to 4" spools. Brand new complete with head circuits. \$9.50 carr. 30n. £9 50 carr. 30p.

TOP QUALITY SLIDER CONTROLS

60mm stroke high quality controls complete with knobs (post, etc. 15p any quantity).

Singles Log and Lin 5K, 10K, 22K, 50K, 100K, 250K, 500K, 1 Meg. 45p each.

Ganged Log and Lin 10K, 22K, 50K, 100K, 250K, 65p each. (Quantity discounts available) Complete with knobs.

MARRIOT

MARRIOT
TAPE HEADS
4 TRACK MONO or
2 TRACK STEREO
'17' High Impedance £2-50
'18' Med. Impedance £2-50
'36' Med. Impedance £3-50
'36' Med. Impedance

75p pair.
Erase Heads for '17', '18'
and '36' £1.00
'63' 2 track mono, Hi Imp.

'63' 2 track mono, Hi Imp. £1·75 '43' Erase Head for '63' 75p (Post, etc. 15p any qty).

SINCLAIR, MINIATURE AMPLIFIERS & TUNER/DECODER

AMPLIFIERS (carr., etc. 20p)
4-300, 0-3 watt 9 volt 3-75
104.1 watt 9 volt 3-19
304.3 watt 19 volt 3-19
555, 3 watt 12 volt 4-10
E1208, 5 watt 12 volt 5-10
608, 10 watt 24 volt 4-95
11206, 30 watt 45 volt 4-95
E1210, 2½ + 2½ watts
12 volt 7-75

1210, 2‡ + 2½ warrs
12 volt
7.75
RE500, 5 watt IC mains
operated Amplifier with
controls
SAC14, 7+ 7 watt Stereo,
with controls
11.75
SAC13, 15 + 15 watt
Stereo with controls
14.95



FIBRE OPTICS

0·01 Diam. Mono Filament £3·00 per 50 metre reel 0·13 Diam. 60 Fibres Sheathed. £1·00 per metre. SPRAYS 15mm Diam. (Mares Tail Spray £10·50 7mm. Diam. £5·00)



All types offered subject to availability. Prices correct at time of press E & OE. 10% VAT TO BE ADDED TO ALL ORDERS. UK post etc. 15p per order unless stated.

RADIO LIMITED **EDGWARE ROAD, LONDON W2**

406 Electronic Components and Equipment 01-402 8381

404-406 Electronic Components and Equipment 01-402-8381 309 PA – Disco – Lighting High Power Sound 01-723 6963 303 Bargains Store (Callers only) Home and Car Entertainment Centres London and branches now of 120 Shaftesbury Avenue, London W1 01-437 9692 104 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7402 190-194 Station Road, Harrow, Middlessey 01-663 7788/9 354-356 Edgware Road, London W2 01-402 5854/4736

All mail to 303 Edgware Road, London W2 1BW All stores open 9 am to 6 pm six days a week Hi-Fi – Tape Equipment Discount Stock List Free at all stores

everyday electronics

PROJECTS.. THEORY....

SOUNDS DIFFERENT

Now, for something quite different, as they say, in sound. We are all familiar with a host of unique sounds (musical or otherwise!) that electronics has been entirely responsible for. But in addition to creating original sounds, electronics is of course very good at imitating sounds, such as those characteristic of traditional musical instruments. Many examples have already appeared, but so far as we are aware the Bagpipes have not been singled out for this favoured treatment-until now.

We wonder why. Anyhow to demonstrate our strict neutrality in matters musical as well as geographical, we offer our readers this latest musical novelty. It is, incidently, yet another example of the inspired use of fairly conventional circuitry. So please remember, all you would-be inventors, it is that original thought for applying electronics to some account in an unusual or novel way, that is all important; the actual circuitry comes quite naturally thereafter, in many cases.

SPEED GUARD

The tendency of motorists to travel at unsafe speeds when caught in fog has a perfectly reasonable explanation, so the experts tell us. It is really because sense of speed is seriously affected when sight of external reference points is lost due to poor visibility, the need to concentrate fully on the road ahead precluding any diversion of attention-even momentarily-

Our June issue will be published on Friday, May 17

from windscreen to speedometer. So an unconscious steady acceleration is all too commonly the result.

In an attempt to overcome this particular problem we understand that the authorities are currently investigating a "head-up" display speedometer, where the appropriate data is projected onto the windscreen and is readable without interfering in any way with the driver's normal view.

It is to be hoped that success is the outcome of this attempt to produce a cheap and relatively simple version of the more sophisticated system already employed in aircraft, so that in time it could become standard equipment for all vehicles. In the meanwhile it occurs to us that the Speed Guard described in the March issue of Everyday Electronics could very well be widely adopted as a fog hazard aid, providing an audible indication that some pre-determined speed (reasonably low—30 m.p.h. for example) has been reached. The addition of an on/off switch is all that would be necessary to make the Speed Guard suitable for this kind of function; it could then be easily brought into operation directly visibility deteriorated to a dangerous level.

For a quite modest outlay of about £4 the motorist could equip his vehicle with an extremely useful, and maybe life-saving, electronic aid.

feel bennett

B. W. Terrell B.Sc.

EDITOR F. E. Bennett ASSISTANT EDITOR M. Kenward

> ART EDITOR J. D. Pountney P. A. Loates K. A. Woodruff

> > ADVERTISEMENT MANAGER D. W. B. Tilleard

© IPC Magazines Limited 1974. Copyright in all drawings, photographs, and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden.

All reasonable precautions are taken by EVERYDAY ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Everyday Electronics Fleetway House, Farringdon Street, London, E.C.4. Phone: Editorial 01-634-4452; Advertisements 01-634-4202.

.. EASY TO CONSTRUCT .. SIMPLY EXPLAINED



VOL. 3 NO. 5 MAY 1974

CONSTRUCTIONAL PROJECTS

ELECTRONIC BAGPIPES Simulation of the real thing	by T. Richardson	254
SIMPLE BUZZER An audible alarm by A. Russell		258
TRANSISTOR TESTER (E.E. Test Gear Five)		266
EGG TIMER Times from two to five minutes by R. A. P.	enfold	276

GENERAL FEATURES

EDITORIAL	252
TEACH-IN '74 Lesson 8: The Astable and Alternating Current by Phil Allcock	260
COUNTER INTELLIGENCE A retailer comments by Paul Young	270
ELECTRONICS AND THE MOTOR CAR by C. S. Pointer	271
SHOP TALK Component supply matters by Mike Kenward	275
PLEASE TAKE NOTE	275
RUMINATIONS by Sensor	280
SEMICONDUCTOR PRIMER Facts and figures by A. P. Stephenson	281
HELP! Your problems answered	282
JACK PLUG AND FAMILY Cartoon	285
DOWN TO EARTH Impedance by George Hylton	286
READERS' LETTERS From you to us	289
WHAT DO YOU KNOW? Capacitors	289

Publisher's Annual Subscription Rate, including postage to any part of the world, £2.95. International Giro facilities Account No. 5122007. State reason for payment "message to payee". Address to Everyday Electronics, Subscription Department, Carlton House, Great Queen Street, London, WC2E 9PR. Binders for volumes 1 to 3 (state which) and indexes for volume 1 and 2 available for £1.25 and 11p respectively, including postage, from Binding Department, at the above address.

We are unable to supply back copies of Everyday Electronics or reprints of articles and cannot undertake to answer readers' letters requesting designs, modifications or information on commercial equipment or subjects not published by us. An s.a.e. should be enclosed for a personal reply. Letters concerning published articles should be addressed to: The Editor, those concerning advertisements to: The Advertisement Manager, both at the address shown opposite.

PREE ENTRY
FREE COMPETITION

MULTIMETERS TO BE WON

Make sure of your copy-Order Now!

Electronic simulation of the bagpipe sound.

This instrument is an attempt to simulate, fairly simply, the sound and method of playing the bagpipes. The finished instrument is also capable of producing other types of sound and is fitted with a vibrato effect and switching for the drone sound in the bagpipe simulation.

CIRCUIT

The complete circuit diagram is shown in Fig. 1, TR3 is the main unijunction oscillator (chanter oscillator) which is fine tuned by VR2 wired in series with resistors R19 to R26. These resistors being inside the chanter. Transistor TR2 forms a vibrato oscillator which can be switched off and on as desired, by the tone switch S1. This same switch in another position will operate the drone oscillator (TR1). This is necessary for simulation of bagpipes.

The drone oscillator has a larger value tuning resistor VR1, which allows the drone to be tuned to either the treble or bass end of the scale as desired. Both oscillators are fed to TR4 via resistors R12 and R13; it will be noticed R13

is a higher value than R12, so that the chanter will be predominant while playing the pipes.

Transistor TR4 is a signal amplifier the output of which is fed to a screened lead via the tone forming network comprising C10, C12, C13 and R18. These components suppress some of the higher harmonics, and make a more realistic bagpipe sound. Switch S2 is simply a microswitch wired in series with battery B1. It is situated in such a position that by squeezing the unit with the elbow, S1 is closed and switches the unit on for playing. The unit is switched off when pressure is released. This leaves both hands free on the chanter to enable the player to start, or end a tune on any note desired.

It will be seen that with the tone switch in position one, the bagpipe sound is produced; in position two only the main oscillator is in circuit. This will give a sound not unlike the clarinet, but adjustments of controls on the amplifier it is plugged into, could make a lot of difference to the tone. In position three, the sound is modulated by the vibrato, and becomes a pleasing sound, not unlike an organ.

CONSTRUCTION

As seen from the Fig. 2. most of the components are mounted on a Veroboard panel

ELECTRONIC BAGITES

BY T. RICHARDSON

measuring 20 holes by 13, the copper strips running along the 20 holes. The strips are cut at the points marked on the underside drawing and all the components are laid out in straight lines from top to bottom; it must be noted that components (C2, R13; C7, R8; C9 and R12) are stood up on end and the junctions are **not** connected to the panel after wiring.

This panel can be tested on its own, by connecting in VR1 and a temporary connection from VR2 free end to battery positive. Either connect phones across the output or feed into an amplifier, connect the battery positive and negative. This should cause the chanter oscillator to function, adjustment of VR2 should change the pitch by about two or three notes.

Now connect the wire from C1/R2 to negative, and the drone will be heard, VR1 should alter the drone by well over an octave. If all is well, connect a wire from R7 to negative and test the vibrato.


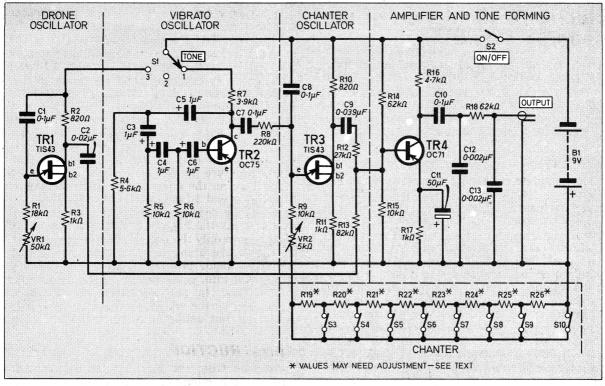


Fig. 1. Complete circuit diagram of the Electronic Bagpipes.

Components. **Potentiometers** VR1 50kΩ lin carbon VR2 5kΩ lin carbon Resistors R1 18kΩ R14 62kΩ Semiconductors R2 TR1 TIS43 unijunction **820**Ω **R15** 10kΩ 4.7k() TR2 OC75 germanium pnp R₃ 1kΩ **R16** TR3 R4 5.6kΩ R17 1kΩ TIS43 unijunction R₅ 10kΩ R18 62k() TR4 OC71 germanium pnp R₆ 10kΩ R19 1kΩ **Switches** 3.9k() R7 R20 3 · 3kΩ approximate S1 single pole three way wafer switch R8 220kΩ 2.4k() R21 values, S2 push to make single pole microswitch R9 10kΩ -R22 1.2kΩ may need S3-S10 push to break single pole miniature **R10** 820Ω R23 2.2k() alteration push buttons (8 off) **R11** 1kΩ **R24** 1.5kΩ to tune 2·1kΩ R12 27kΩ R25 chanter Miscellaneous R13 82kΩ R26 62002 B1 9V PP3 battery All ±5% ¼W carbon Knob to suit S1, screened lead, 25mm diameter plastic tube 270mm long, materials for case, connecting wire, Veroboard 13 strips by 20 holes by 0.15 inch matrix, 4 BA fixings, Capacitors 0.1 / F 0.022/1F plastic or Formica for facia panel. C3 1µF 1/1F may be elect. 12V 1/LF 1/1F **Approximate cost** C7 0.1/1F **C8** 0·1/4F of components C9 0.039µF including V.A.T. C10 0.1nF C11 50µF elect. 12V 0.002µF C12 excluding case C13 0.002µF £6.00

255

Everyday Electronics, May 1974

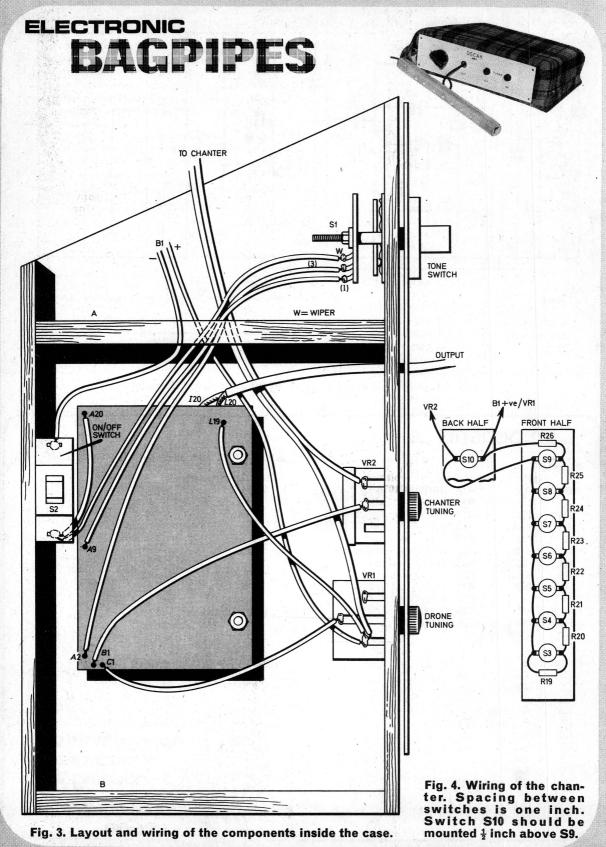

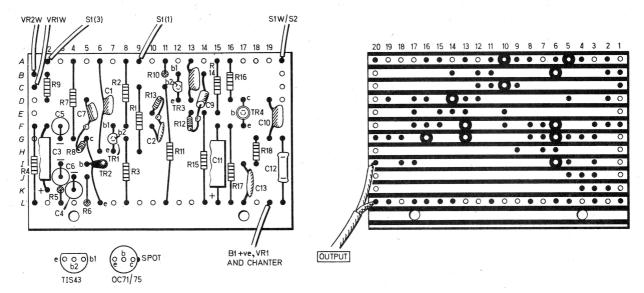


Fig. 2. Component layout and wiring on the Veroboard.


It should be mentioned at this point that R4 (5.6 kilohm) and R8 (220 kilohm) are used in the prototype, but may be adjusted to suit individual requirements, R4 controls vibrato speed and R8 the amplitude. An OC75 transistor or similar is used in the vibrato and must be a high gain type, TR4 is an OC71, but this could be any similar transistor. TR1 and TR3 are both unijunction type TIS43 but similar alternatives can be used.

CASE

A box must be assembled in the way shown in Fig. 3, but at this stage the top panel is not fixed. The left hand panel in Fig. 3 is 6mm narrower than the rest. The two upright supports (A and B in Fig. 3) should be tapered from halfway along, to the side panel. This allows the top panel to be squeezed in under the armpit, to actuate the microswitch S2.

After drilling holes on the side panel to accommodate controls VR1 and VR2, and switch

Photograph of the component board.

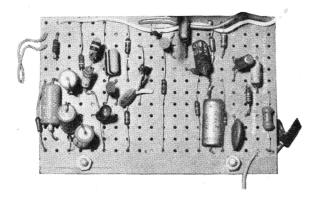

S1, the components may be mounted inside the case.

Switch S2 must be bolted to the side panel near the front edge, so that the actuator will be pressed in when the side panel is pushed onto it.

After all the wiring is completed as shown in Fig. 3 the side panel is screwed on, with two screws near the right hand side. Finally the case is covered in thin foam rubber and a tartan bag covers the whole unit. This bag may either be tacked or glued to the control panel, and the fascia screwed on to finish the unit off (see photographs).


CHANTER

The chanter is made by sawing 25mm diameter plastic tube (such as water pipe etc.) down the centre and drilling suitable sized holes to take miniature push button switches. After wiring to Fig. 4, join the two halves together.

The chanter resistors are chosen to play the diatonic scale. To select the proper key R9 may have to be varied, so as to play the top note of the scale with VR2 near mid travel.

PLAYING

The unit is plugged into an amplifier of almost any type. A suitable design will be published in our July issue. The instrument is placed under the arm, control panel downwards, and squeezed. Switch to position two or three and once you're certain the chanter is tuned properly, switch to position one and tune drone to either top, or bottom note. When fingering this instrument the same method is used as for playing a tin whistle or similar instrument, i.e. the highest note left open is sounded.

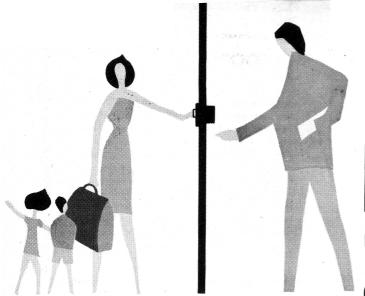

An audible warning device useful for many applications

A BALANCED armature earpiece can be converted into an effective buzzer by the addition of only a few components. The prototype "converted" earpiece was used in a continuity tester but the buzzer can be used in any application requiring an audible alarm.

CIRCUIT

The circuit diagram of the Simple Buzzer is shown in Fig. 1. and operates as follows.

When the supply is connected, C1 starts to charge up via VR1, and when a certain voltage level is reached at the junction of VR1 and C1, the transistor starts to conduct.

The change in voltage across the earpiece, TL1, induces a voltage in L1 which tends to help TR1 turn on (positive feedback), TR1 thus turns on very quickly. When TR1 is fully on, the voltage induced in L1 reduces to zero and C1 discharges through TR1 base/emitter; as this occurs, the voltage on TR1 base is reduced, and a point is reached when TR1 starts to turn off.

The voltage change across TL1 is now in the opposite direction and this induces a voltage in L1 which assists TR1 to turn off.

When TR1 is fully off the cycle repeats itself—thus producing an audible tone. The frequency of the tone is dependant on the values of VR1 and C1. Reducing VR1 will enable C1 to charge up more rapidly and thus increase the frequency, i.e. a higher pitched tone.

CONSTRUCTION

The components can either be mounted inside the earpiece itself, as in the prototype, or may be mounted seperately on a piece of Veroboard or printed circuit board.

BY A.RUSSELL



Approximate cost of components including V.A.I.

£1.50 inclusive

It is necessary to dismantle the earpiece and remove the coil; with this done, wind on 10 turns of 26 s.w.g. enamelled copper wire and replace the coil. Mount the other components in the earpiece as shown in Fig. 2.

If this exact type of earpiece is not used it may be necessary to redesign the layout of the components or alternatively an exterior circuit board will have to be employed.

SETTING UP

Turn the potentiometer VR1 to its maximum resistance position and switch on.

With a small screwdriver, turn VR1 until a tone emanates from the earpiece. If the buzzer


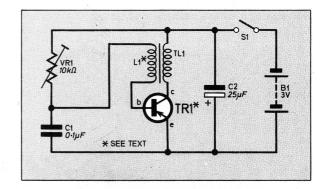


Fig. 1. Circuit diagram of the complete Simple Buzzer.

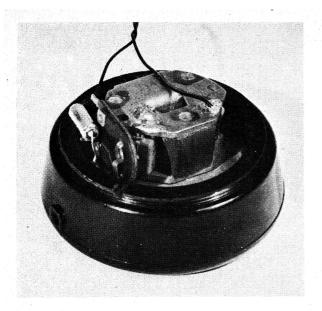

Photograph of the original unit with part of the case removed.

refuses to oscillate, even when VR1 is one quarter of the maximum value, intercharge the connections to the added feedback windings, and repeat the above procedure. The buzzer, when correctly set up can be activated by closing S1, this is useful when used as a door buzzer; if

Components....

Capacitors

C1 0.1 µF

C2 25μF elect. 12V

Potentiometer

VR1 $10k\Omega$ skeleton preset

Transistor

TR1 2N3702 silcon *pnp* or any similar transistor

Miscellaneous

L1 26 s.w.g. enamelled copper wire

S1 on/off switch if required, e.g. door bell push, etc.

B1 3V battery (2 x U2 etc)

TL1 ITBA No. 5 or any balanced armature earpiece of approx. 50 ohms to 100 ohms impedance.

Connecting wire.

used in an alarm circuit, the switch can be replaced by a set of relay contacts or a thyristor.

COMPONENT NOTES

The earpiece used in the prototype was one from an army field telephone unit, type ITBA No. 5. It has a coil resistance of 50 ohms. This type and similar earpieces should be available from government surplus stores.

The transistor type is not critical, almost any pnp transistor with a gain (h_{te}) greater than 20 would do.

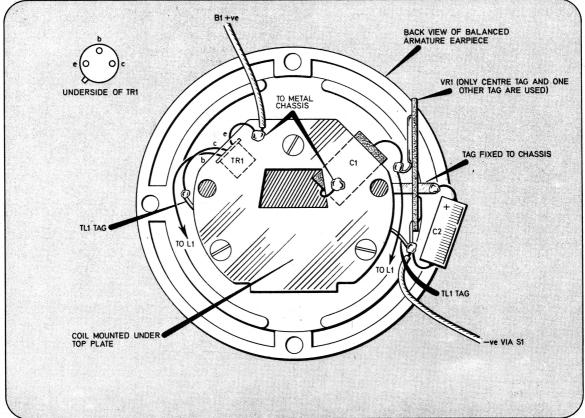


Fig. 2. Complete layout and wiring of the simple buzzer.




This month we examine the astable multivibrator and go on to look at some new ideas and theory relevant to basic circuit elements, in order to extend the range of electronic circuits that can be covered in the remainder of the Teach-In '74 series. The additional components required for the Tutor Board experiments for future parts are listed later.

ASTABLE CIRCUIT

The **astable circuit** does not have any permanent stable states and switches continuously between two temporary states. The basic idea follows on quite naturally from the previous monostable but the circuit is modified so that a second charge/discharge timing element is introduced between point *Z* and the base of TR2 in Fig. 7.4 of last month.

Instead of the switching state being controlled directly from point Z it is controlled instead by a duplicate of the coupling circuit C1, R1. The simplest arrangement is illustrated in Fig. 8.1 where it can be seen that the astable consists

Fig. 8.1. The astable multivibrator.

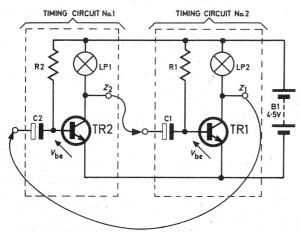

of two similar timing circuits connected so that the transistor of either circuit acts as the "switch" for the other "half". Consequently the recharging of (say) C2 via R2 determines the instant at which TR2 can switch from off to on and it is the switching on of TR2 which initiates the timing interval during which C1 can recharge via R1.

This recharging of C1, in turn controls the switch *on* instant of TR1, which in turn controls the start of the timing interval for TR2 again. The cycle of events continues indefinitely and as one transistor switches *on* the other is automatically switched *off* for a time duration determined by the choice of C—R values.

It is not necessary to have C1=C2 or R1=R2 although the maximum values of R1 and R2 are limited in this circuit by the need to ensure adequate current for the lamps LP1, LP2.

In normal circumstances the circuit will start operating as soon as the supply voltage is connected but occasionally both transistors can switch *on* together, in which case the circuit will not self-start. This failure to start sometimes occurs when the supply voltage builds up slowly, as can happen when the circuit is operated from a power supply derived from the mains, but is less likely to happen when the two timing circuits are made dissimilar by using (say) different values for C1 and C2, with R1=R2.

The waveforms of base voltage against time for the two transistors are illustrated in Fig. 8.2 for the case where C1 is larger than C2 and R1, R2 are equal. The recharging of C1 via R1 involves the larger time constant and this makes the on/off times unequal. For equal on/off durations the transistors must be "identical" and the two time constants must be equal.

VOLTAGE REVERSAL

In both the monostable and the astable circuit we have seen that the voltage at the base of the transistor reverses at the instant of switching,

^{*} North Staffordshire Polytechnic Any communications arising from the Teach-In '74 series must be addressed to Everyday Electronics, Fleetway House, Farringdon Street, London E.C.4).

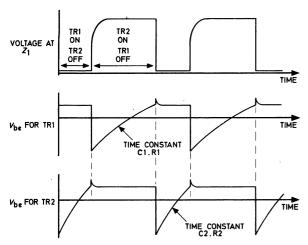


Fig. 8.2. Voltage waveforms for the astable multivibrator.

due to the charge storage characteristic of the capacitor and in some circuits the reverse bias across the base/emitter junction can exceed the safe reverse voltage rating given by the manufacturer. For the BC107 device this rating is given as:—

$$V_{\rm ebo}$$
 (max)=6.0 volts

Consequently when a supply voltage of more than $6 \cdot 0$ volts is employed there is a risk of transistor damage, or circuit malfunction, since we have already shown that the instantaneous value of the reverse bias has a maximum value which is only about 500 mV less than the supply voltage used. For the circuits shown in Fig. 7.4 and 8.1 this voltage is about $4 \cdot 0$ volts and is within the transistor rating.

It is often necessary to operate a circuit such as the astable from a supply voltage considerably larger than the 6·0 volt $V_{\rm obo}$ rating (which is incidentally a typical value for many modern silicon transistors). Certain modifications can be made to the basic circuit to protect the transistor emitter/base junctions from excess reverse voltage and two possibilities are shown in Fig. 8.3.

In Fig. 8.3a a silicon diode is used in series with the transistor base lead so that when the voltage reversal occurs the higher reverse voltage rating of the diode (typically 50 volts or more) protects the transistor junction against possible breakdown. The reverse voltage is shared between the diode and the transistor junction and since the diode will maintain a very high back resistance even when subjected to large reverse voltages, the current flow is severely restricted and breakdown cannot occur.

The forward voltage drop across the diode increases the voltage level at which the transistor turns on, and with a silicon diode the voltage V_1 in Fig. 8.3a will become clamped at about $1\cdot 0$ volt instead of the previous value of approximately $0\cdot 5$ volts. Fig. 8.3b works in a similar manner but has the additional effect of raising

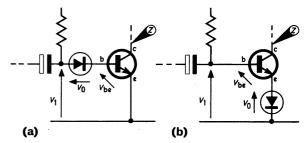


Fig. 8.3(a). Protection by base diode (b) protection by emitter diode.

the voltage level at point Z, when the transistor saturates, due to the diode voltage drop.

Since the change of voltage at point Z determines the negative excursion at the base of the other transistor, the emitter connected diode will reduce this excursion by about 0.5 volts. Note that V_1 for the emitter diode arrangement will be slightly larger than V_1 for the base diode circuit because the emitter connected diode must carry the full emitter current of the transistor and as a result will have a larger forward voltage drop, V_0 . The only effect of these small differences is that the circuit timing changes slightly but this need not concern us here.

OFF TIME AND FREQUENCY OF OPERATION

We have seen that the transistor TR1 in Fig. 7.1 turns off for a short interval immediately the switch is closed. The "off time" can be obtained by considering the waveform shown in Fig. 7.3 which shows that TR1 remains off for the interval (t_2 — t_1). During this interval the capacitor voltage V_c changes from $+4\cdot0$ volts to $-0\cdot5$ volts and it can be shown that the "off time" is given by the following equation.

"off time" =
$$(C1 \times R1) \log_e \left[\frac{1}{1 - N} \right]$$

Where N is the ratio of the actual change in the voltage V_c , to the maximum change that would occur if the emitter/base clamping action was not present. For our circuit this ratio is:

$$N = \frac{4 \cdot 0 - (-0 \cdot 5)}{4 \cdot 0 - (-4 \cdot 5)} = \frac{4 \cdot 5}{8 \cdot 5} = \frac{9}{17}$$

The symbol log₀ means natural logarithm and is given in books of mathematical tables.

For our circuit:

$$\log_{\mathbf{e}} \left\lceil \frac{1}{1-N} \right\rceil = \log_{\mathbf{e}} \left\lceil \frac{17}{8} \right\rceil = 0.75$$

In fact N is always approximately equal to one half because the actual change of capacitor voltage is nearly equal to the supply voltage whilst the maximum voltage change is about twice this value. (For N=0.5 the \log_0 term would be 0.7 approximately). We have therefore a simple way of estimating the off time as 75 per cent of the

CR constant. If $Cl = 1000 \mu F$ and $Rl = 4.7 k\Omega$ the off time will be given by:—

"off time" = $(0.75 \times 4.7 \times 1000)$ milliseconds, which is approximately 3.5 seconds.

In the case of the astable circuit one complete sequence of events, called a cycle, will take a time that is the sum of the individual off times for the two halves of the circuit. The "number of cycles" that occur in one second is known as the frequency. One cycle per second is called one hertz (Hz).

We can express these circuit parameters as follows:

Total "off time" 0.75 (C1.R1+C2.R2) and if C1.R1=C2.R2=T say, then

Frequency
$$\frac{1}{(1.5 \times T)}$$
 Hz. (must be in seconds)

It must be noted that this result is only approximate but does give a simple method of estimating the circuit frequency.


The astable circuit is just one of many oscillator circuits that can generate voltages (in this case at either the transistor collectors or bases) which are periodic i.e. have a repetitive waveform. The normal household mains supply is another example of a periodic (alternating) voltage, and has a smoother waveform than the square wave output produced at the collectors of the astable multivibrator circuit.

REFERENCE OR COMMON CONNECTIONS

Most of the circuits covered so far have involved currents and voltages that were either steady, or that varied in magnitude (but not polarity) with time. In many circuits one side of the power supply is taken as the common or ground side even though no connection is actually made to "ground or earth".

This concept of a common point or datum is useful since we can refer our measurements to this point and in Fig. 8.4 a circuit is shown that in effect uses two separate power supplies B1, B2 which provide opposite polarity. With reference to the datum or common point, B1 provides a positive voltage to one end of R1 and therefore sets up an emitter current in TR1.

Fig. 8.4. Common base amplifier using two power supplies.

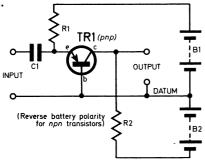

The collector current flows via R2 which is supplied with a negative voltage (relative to datum) by B2. The small base current must flow in the datum lead which is *common* to input, output, B1 and B2.

We have seen that it is possible to produce a reversal of voltage polarity in the astable multivibrator (Fig. 8.2) and in many electronic circuits alternating voltage and current waveforms of this type are produced.

ALTERNATING WAVEFORMS

It is not necessary for all alternating waveforms to have the same shape as Fig. 8.2 and some other common variations are illustrated in Fig. 8.5. In Fig. 8.5a the waveform is smooth and there are no abrupt changes.


An example of such a waveform is the household mains supply and in this case the waveform is very nearly **sinusoidal**. This simply means that the voltage or current varies with time according to the mathematical sine function and can therefore be expressed by $V = V_{\text{III}}$ sin $(2\pi ft)$. We will come back to this expression later on.

The Figs. 8.5b and 8.5c show a triangular waveform and a square waveform respectively. Notice that in each of these examples the waveform "shape" repeats itself at regular intervals and that the waveform is symmetrical insofar as the shape of the positive and negative portions are mirror images of each other.

In Fig. 8.5d we have a "repetitive pulse" waveform. The waveform still repeats its particular shape at regular intervals but the waveform symmetry is no longer present since the positive portions are "tall and narrow" whilst the negative portions have smaller amplitude and greater width.

Actually it is somewhat artificial to consider the waveform as two portions, positive and negative, but at this stage we shall find the idea useful for discussion purposes.

Fig. 8.5. Some common waveforms.

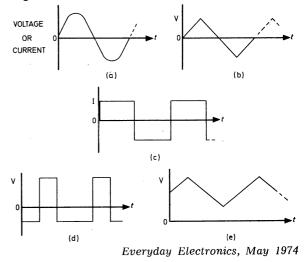

The waveform in Fig. 8.5e is not, strictly speaking, an alternating waveform, since it is always positive, but it can be considered to be made up of two parts. If we add a steady positive voltage to an alternating voltage such as that in Fig. 8.5b we can produce a waveform exactly like that in Fig. 8.5e. This idea of breaking a waveform into steady and alternating portions is also very useful.

AVERAGE VALUES

Waveforms that contain alternating and steady components are very common and the steady component is known as the average value of the waveform. The meaning of this is best illustrated by considering the current waveforms shown in Fig. 8.6. In (a) the waveform is symmetrical and the shape repeats itself every two milliseconds. We say that the periodic time is 2ms since this is the time occupied by the waveform in tracing out its characteristic shape for one complete cycle of variation.

The waveform is made up by a series of such cycles and the number of cycles that occur every second is known as the frequency, measured in hertz (Hz). Thus the waveform of Fig. 8.6a can be described by the following:—

shape—squarewave period—2ms (for one complete cycle) frequency—500Hz (number of cycles per second)

other features—symmetrical ± 1A, average value zero.

The zero average value results from the perfect symmetry of the positive and negative half cycles. The area under the positive half cycle is (lamp)×(lms) and represents a flow of charge of one millicoulomb in a given direction through some circuit. The area under the negative half cycle represents an equal amount of charge flowing in the opposite direction. The nett or average flow is therefore zero over one or more complete cycles of the square waveform.

A similar shape is illustrated in Fig. 8.6b but this time the current is either 2A or zero. The period, frequency and peak to peak current swing (2A) are the same as before but this time the average value is not zero. Every complete cycle a charge of 2mC is passed round the circuit in the positive direction—nothing is ever passed back in the reverse direction. The

average flow is therefore 2mC every 2ms and is equivalent to an average current of 1 ampere.

This can be seen in Fig. 8.6b since if the top half of each rectangle is removed and used to fill the following space a continuous constant current of +1 ampere results. It is easy to see that by adding a constant current of one ampere to the waveform of Fig. 8.6a the waveform of Fig. 8.6b results.

A.C. THEORY

To extend our knowledge of electronic circuits it is necessary to examine the behaviour of all our previous components under alternating conditions. In fact to gain a full understanding of the behaviour of components it is necessary to consider time varying current or voltage waveforms in general and fortunately this is possible by introducing one fundamental concept—namely the idea of rate of change. If the voltage across a capacitor is varying with time the current flow will be given by

 $i=C\times rate$ of change of voltage.

If C is in farads and the rate of change is in volts per second the current will be in amperes. If the rate of change of voltage is varying with time then the current will vary in a similar manner. To illustrate some of the possibilities let us consider Fig. 8.7. Diagram (a) shows a voltage which is rising uniformly with time. In this case the rate of change is *constant* and is equal to the slope of the line which is +20 volts per second. Since the capacitor has a fixed value of $1000\mu F$ the current will be constant and equal to

Current = $1000 (\mu F) \times 20 (V/s) = 20,000 \mu A = 20 mA$

As long as the rate of change of voltage is maintained constant at 20 V/s the current will remain at 20mA. After say ten seconds the capacitor voltage will have increased from zero to +200 volts and the charge, Q, stored in the capacitor will be


$$Q = C \times V$$
= 1000 (μ F)×200 (V)=0·2 coulomb

Notice that this result agrees with the charge transferred by the current flow using

$$Q=i\times t$$

= 20 (mA)×10 (s)=0·2 coulomb

A voltage that rises and falls in a regular way is illustrated in Fig. 8.7b, if this voltage appeared

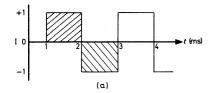

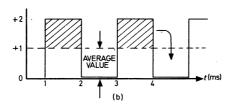


Fig. 8.6. Illustrating average values.

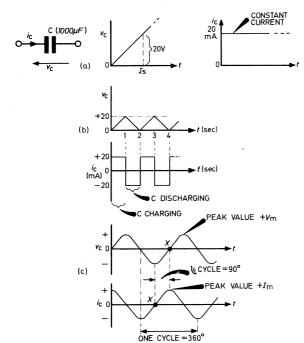


Fig. 8.7. Voltage and current waveforms for a capacitor.

across a capacitor C the resulting current would be a square wave. The current is positive when the voltage has a positive rate of change of +20volts per second, whereas the current flow is reversed (i.e. negative) when the voltage falls at 20 volts per second. A falling voltage gives a negative rate of change.

Notice that the capacitor is charging when the current is positive and discharging when the current is negative, Fig. 8.7c illustrates the be-

Components..

Capacitors

(Additional to those listed in Part 1)

Semiconductors

silicon diodes (3 off) IN4001

TIS43 unijunction transistor (1 off) 2N3819

field effect transistor (1 off) BC477 silicon pnp transistor (1 off)

BTX30-25 triac (1 off)

0.22 pF polyester (2 off)

Loudspeaker

35 Ω 65mm (approx) (1 off)

Miscellaneous

Friedland bell transformer 8V secondary (1 off); Ferrite rod 150 to 200mm long, 10mm (zin) diameter (1 off); 30 s.w.g. enamelled copper wire (2 oz. reel); Plastic cotton bobbin (1 off from Woolworths); Reed switch type 6-RSR-A (1 off). 12-way terminal blocksimilar to that already in use.

haviour when the capacitor voltage is a sine wave. At the positive and negative voltage peaks the rate of change (i.e. slope of the waveform) is zero. The current waveform has the same sinusoidal shape but it is displaced in time relative to the voltage waveform.

The displacement is seen to be equivalent to a shift of a quarter of one cycle and since one complete cycle corresponds to a change of 360 degrees in the angle θ of a sine function, such as 10 sin θ , the displacement can be expressed as a shift of phase of 90 degrees. The current is said to lead the voltage by 90 degrees since it passes through any specified point, such as X, 90 degrees ahead of the corresponding point on the voltage variation.

INDUCTANCE

When current flows in a wire or conductor a magnetic field is set up in the vicinity. If the wire is formed into a coil the magnetic field links the various turns and this gives rise to the property known as inductance. In our previous experiments we have not needed to use this property which is incidentally always present to some degree, just as stray capacitance is always present, in electronic circuits.

Some components utilise the magnetic effects produced by current flow and two well known examples are the relay and transformer.

Next month we shall look at inductance in a.c. circuits and go on to examine reactance, resonance and r.m.s. values.

For the experimental work of the remainder of the Teach-In '74 series, some additional components will be required; these are listed on this page.

TUTOR BOARD EXPERIMENT

Test No. 19

Disconnect the battery and modify the Tutor Board wiring to match the circuit of Fig. 8.1. Use 4.7 kilohm resistors for R1 and R2 and check the operation of the circuit for each of the following capacitor values in turn. Observe capacitor polarity!

1. C1 and C2 both 250μ F.

2. C1 = 1000μ F; C2 = 250μ F.

3. $C1 = 1000 \mu F$; $C2 = 125 \mu F$ (made from two 250μF capacitors in series).

The on state for each transistor is indicated by the lamps and the voltage at Z_1 and Z_2 can be examined using the standard 0-10V voltmeter circuit. The layout for this test is left as an exercise for readers. The effect of the different capacitor values can be determined by observing the "on time" of the lamps.



Plus 3 Constructional Projects...

80m and 160m **AMATEUR BANDS** RECEIVER

Ordinary a.m. receivers are unsuitable for single sideband reception and also for the other main transmission mode used by amateurs, carrier wave (morse code). The most simple type of receiver suitable for amateur band reception is the direct conversion type and the construction of such a receiver covering the 80 metre and 160 metre bands will be described next month.

FREEZER TEMPERATURE ALARM

Many homes now possessadeep freeze unit and it is logical, particularly if the unit is fitted in a garage or other "outbuilding", to have an indicator available in the house to show that a temperature variation has occurred before the contents of the freezer are spoiled. The unit to be described next month indicates any rise or fall in the temperature with an audible and visual warning.



TEST GEAR FIVE 5th. Instrument GENERAT

R.F.SIGN

JUNE ISSUE ON SALE MAY 17

C RHH HHI

TRANSISTOR

TESTER

Gives a direct reading of six transistor parameters

ENTHUSIASTS spend a large proportion of their time testing and commissioning electronic circuits. Transistors employed within these circuits can become suspect and therefore a simple transistor test meter is an asset. The Transistor Tester described in this article is cheap and simple to build yet checks the basic parameters of the transistor under test. These parameters are static forward current transfer ratio $(h_{\rm FE})$, collector leakage current $(I_{\rm CEO})$ and base/emitter, base/collector forward and reverse resistance.

The instrument functions with a supply voltage between 10 and 20 volts, which is within the range of the *Power Supply Unit* described in the February issue.

TEST SYSTEM

The meter measures gain by injecting a known current $I_{\rm B}$ into the base of the transistor under test and monitoring the collector current $I_{\rm C}$. This gives a direct reading of gain which satisfies the formula:

$$h_{\rm FE} = \frac{I_{\rm C}}{I_{\rm B}}$$

Large changes in collector current or collector/emitter voltage affect the transistor gain. The Transistor Tester is designed so that these variations are small enough to be ignored.

As the symbol, $I_{\rm CEO}$ indicates, the meter ascertains the level of collector leakage current by leaving the base open circuit and applying a constant voltage across the collector/emitter junction, $V_{\rm CE}$. Indicated current flow is the leakage current taken from the collector supply.

Fig. 1 shows that when subjecting an *npn* transistor to resistance checks the transistor acts as two *pn* junctions connected back to back. This enables the junctions of the base/emitter and base/collector to be treated as two diodes. A similar mechanism explains how the system makes resistance checks of *pnp* transistors. However, as the doping in each region is reversed, the diode connections need to be inverted to obtain the same action.



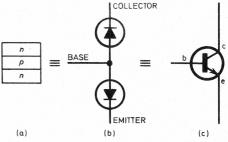


Fig. 1. (a) Schematic layer representation (b) diode representation (c) circuit symbol of an npn transistor.

THE CIRCUIT

The complete circuit diagram, Fig. 2, shows switch S1 set to npn and therefore the collector voltage of the transistor under test is positive with respect to the emitter. A voltage of 4.7V drives the base of the transistor via resistors R2, R3 and R4 depending on the position of the gain switch S4.

A maximum collector current of 10mA provides a suitable and safe value for testing general purpose transistors. The meter used to indicate the gain is connected in series with collector, via switches S1, S2 and S3, and because it is 1mA full scale deflection (f.s.d.), it is shunted with R5 to give the required 10mA f.s.d. Thus by switching S4 the unit can measure a direct gain up to 1000.

Testing a transistor whose collector and emitter are short circuited will cause a large current



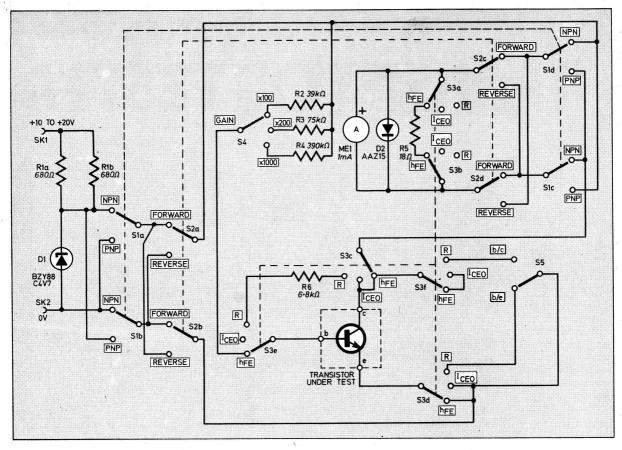


Fig. 2. The complete circuit diagram of the Transistor Tester.

to pass through the meter. To protect the meter against damage, a germanium diode D2 is connected across it. However, the internal resistance of the meter must be about 170 ohms. The short circuit fault in transistors will cause the meter to register hard over in all positions of switch S4, also when S3 is switched to check leakage.

As most leakage currents are in the order of a few microamps the meter is not shunted, so the 1mA f.s.d. will indicate a "leaky" transistor. Switching S3 from position shown removes the shunt resistor R5 and open circuits the base connection (at S3e) thereby giving a direct indication of leakage current ($I_{\rm CEO}$).

FORWARD REVERSE RESISTANCE

Testing the forward resistance of the base/emitter junction of an *npn* transistor requires its base to be positive with respect to the emitter. Switching S3 to its resistance position and S5 to its base/emitter position achieves this and the meter in series with the base measures the current flow.

A large base current is not required or advisable for this test and therefore R6 is included to limit this current below 1mA. Hence the

meter does not require a shunt when making resistance measurements.

To check the junction is behaving like a diode the forward/reverse switch S2 is changed to its reverse position. This reverses the supply voltage applied to the base/emitter junction, also the meter connections.

As the diode is now reverse biased, only leakage current will flow. One can test the base/collector junction in the same manner with switch S5 in the relevant position.

Most general purpose transistors have a minimum base/emitter breakdown voltage ($V_{\rm EBO}$) of 5V and as a safety measure the test voltage is set below that limit at 4·7V. The Zener diode D1 and resistors R1a and R1b achieve this and also enable the unit to function with a supply in the range of 10 to 20V.

CONSTRUCTION

The prototype unit was built in an Olsen type 25A metal instrument case with louvres, of approximate size $160 \times 110 \times 100$ mm, although any similar case will do.

With reference to Figs. 3 and 4, drill the front panel to suit the components and then fit them in position and secure.

TRANSISTOR TESTER


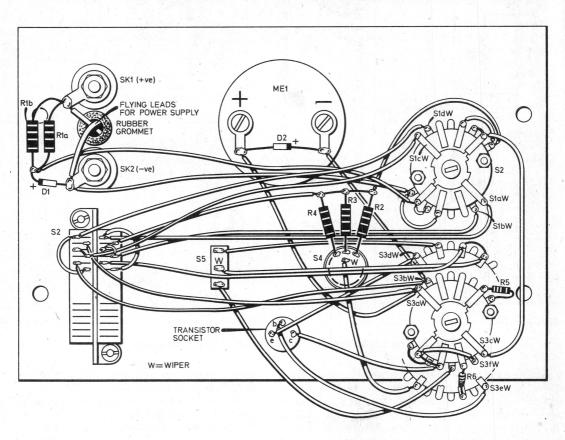


Fig. 3. The positions of the components, all of which are mounted on the front panel showing wiring details. For clarity the top half of S2 is detailed below left.

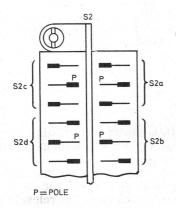



Photograph of the completed Transistor Tester.

Components....

Resistors

R1a 680Ω ½W

R1b 680Ω ½W R2 39kΩ

R3 $75k\Omega$

R4 $390k\Omega$ R5 18Ω

R6 6·8kΩ

All $\frac{1}{4}$ W \pm 5% carbon or better, except where stated

Diodes

D1 400mW 4 7V Zener diode type BZY88 or similar

D2 AAZ15 germanium or similar

Switches

S1 four-pole two-way Maka

S2 four-pole two-way biased lever type MLK03 4CN/S (Keyswitch)

S3 six-pole three-way Maka

S4 single-pole three-way rotary type

S5 single-pole changeover toggle

Miscellaneous


ME1 1mA d.c. SEW SD460

SK1, 2 heavy duty insulated terminals (one

red, one black) (2 off)

Knobs: two large, one small with indicators

(3 off); three-pin transistor socket.

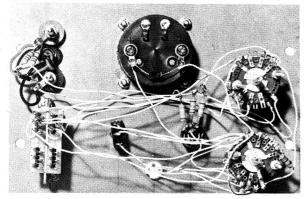

Photograph of completed prototype unit removed from case.

The majority of switches used (e.g. S1—3) have several poles and wiring can easily become confused. It is therefore advisable to wire according to Fig. 3 in conjunction with Fig. 2, starting at the left-hand side of the diagram and working methodically through to the right completing each switch position before going on to the next.

Another aid in clarifying this exercise is to cross off on the diagram each wire as it is connected.

When this has been done and thoroughly checked out, the front panel should be labelled as detailed in Fig. 4 and the knobs screwed on.

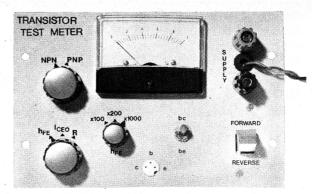


Fig. 4. Details of component positions and labelling on the front panel of the unit.

TEST PROCEDURES

Set the npn/pnp switch to its relevant position and place a transistor in the test socket. To check gain, position the test mode switch S3 to $h_{\rm FE}$ and the gain control to its x100 position.

If the meter indication is greater than full scale, switch the gain control until a direct reading can be taken. Multiplying this reading by the gain control position gives the $h_{\rm FE}$ of the transistor under test.

Remember that the parameter $h_{\rm FE}$ is related to collector current when testing high-power transistors, as there is a large difference between the test and normal operating collector currents.

To check that the transistor's collector leakage current is not excessive, position the test mode switch to $I_{\rm CEO}$ and check that the meter registers a small, if any, current flow. Again, if testing a high-power transistor, some of which have a high leakage current, it is advisable to refer to this particular transistor's data before dismissing it as faulty, purely on the strength of high leakage current.

RESISTANCE

If the previous tests give incorrect results the transistor is faulty and a resistance check will confirm this. To perform the latter test, position the mode switch to resistance and the base/collector, base/emitter switch to base/emitter. Check that the meter indicates a current flow; if not the base/emitter is open circuit.

If the meter indicates a current flow, position the forward reverse switch to reverse and check that only leakage current is flowing. If the meter registers a current flow, the base/emitter junction is short circuit or acting as a resistance and not a diode.

Check the base/collector junction by the same procedure, but with the base/emitter, base/collector switch S5 in the relevant position.

The forward, reverse switch action is such that it is non-locking in the reverse position.

This is necessary as inadvertently leaving this switch in the reverse position will alter the sense of the *npn/pnp* switch. Biasing the switch in the forward position resolves this problem.

DIODE TESTING

This system can be used equally well for resistance measurements of a diode. Proceed as for a transistor measurement, but ensure that the *npn/pnp* switch is in the *npn* position and the base/emitter, base/collector switch is in the base/emitter position.

As stated earlier the base connection is now positive with respect to the emitter and therefore they can be used for the respective anode/cathode connection of the diode to be tested. Place the diode in the base and emitter connections of the transistor test socket and operate the forward, reverse switch to check the diode action.

UNKNOWN TRANSISTORS

If a transistor type or lead connections are unknown, adopt the following procedure. Posi-

tion the mode switch to resistance, and ensuring the base/emitter connection (be) has been selected, place any two of the three transistor leads in the base/emitter test points.

Using the forward and reverse switch, check to see if this connection behaves like a diode. If it does, continue the process combining other pairs of leads until a particular pair give no indication of current flow in either position of the forward reverse switch. This will indicate that these leads are the collector and emitter connections thereby proving the remaining lead is the base.

Connect the known base lead to its relevant position and with either of the remaining leads in the emitter connection, position the npn/pnp switch to give a meter reading. As the forward reverse switch is biased in the forward position, the npn/pnp switch will indicate transistor type when current flow is registered.

Finally, distinguish between collector and emitter leads by positioning the mode switch to h_{FE} and then interchanging the collector/emitter lead positions until the highest gain reading is obtained. The transistor has now been identified with respect to type and lead connections.



.Counter Intelligence

A retailer discusses component supply matters.

HAVE often wondered what percentage of the amateur electronic enthusiasts visit exhibitions? The Boat Show is crammed with boating enthusiasts, the Motor Show with motorists and this list could be considerably extended, but I get the impression that the majority of people at an electronic exhibition are from industry or like myself connected with the trade. If I am correct I think it is a great pity.

The only exception to this was the Radio Hobbies Exhibition (now I believe, defunct) which used to be held at the Horticultural Hall, Victoria and later at Seymour Hall, Seymour Place. It was held in November and it was packed full of the amateur fraternity.

All the same we have a very fine "professional" electronics exhibition in London every year around May and smaller exhibitions are held in Leeds and Brighton. If you venture to the Continent there are large exhibitions in Berlin, Hanover and Paris.

I never miss the London ones and in the last 10 years I have

only missed the Paris one *once*. It was the fact that I have just read a notice in the press to the effect that the "Salon International des Composants Electroniques" in Paris is on, from the 1-6 April inclusive which prompted this article. This is an international exhibition and some 23 different countries are represented including of course the U.K.

I certainly urge you all (especially if you are London based) to visit one of these exhibitions. You will learn a lot, and be able to examine the most up to date circuitry in electronics, you will also find the staff on the stands most helpful. No matter that you are not placing any orders, they know that the amateur of today may be the chief buyer of a large concern tomorrow.

Paris

If you enjoy the London ones, then be extra daring and next year try Paris. Everyone ought to visit Paris once in their life, so combine two pleasures and do the Eiffel Tower, the Louvre, and the Lido as well!

Having said all that, I would like to make a plea to have an exhibition for the amateur electronics constructor, including the "ham". I think the only way it will come about is if the electronics magazines themselves sponsor it!

There is at Olympia, an annual "Do It Yourself" exhibition and since they don't take all the space it might be tacked on to that. I am sure we could rely on the support of many component retailers—even to the extent of taking stands.


Should any of you wish to go to either the "R.C.E.M.F." or "Electronics Instruments and Automation" Exhibition (they alternate each year) these are the two London Exhibitions and announcements should be appearing in the press in April giving the dates, or visit your reference library and have a look in "Whats On" at the exhibitions page.

With reference to the Paris exhibition for information write to:

The French Trade Exhibitions, 196 Sloane Street, London S.W.1

or telephone 01 235 3234. You will also find the French Tourist Office in Piccadilly, London W.1 very helpful on hotels and travel facilities.

Everyday Electronics, May 1974

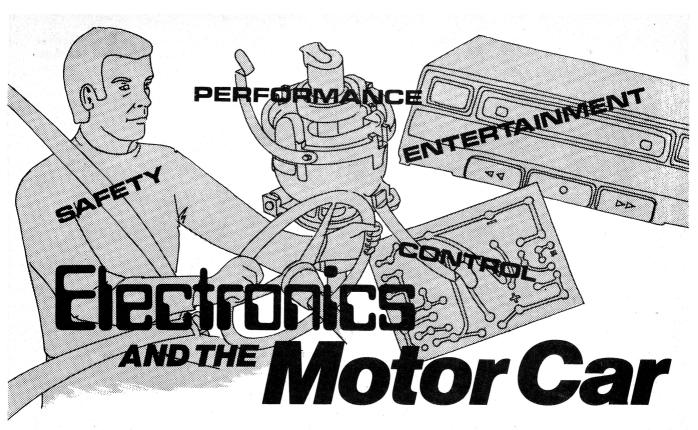

By C.S.POINTER

The electronic content of some of the new more advanced cars now reaching the dealers' showrooms is increasing each year. Many of the more expensive cars have as standard equipment or optional extras electronically controlled fuel injection, transistorised ignition, electronic tachometer, stereo cassette player, a.m./f.m. transistor radio, etc.

This trend can be expected to continue in the future with developments such as ignition cut-out systems operated when seatbelts are not correctly worn and automatic control of vehicle speed at a pre-set value. There are many developed systems and production electronic extras available and *some* of these will be covered in this article.

SAFETY DEVICES AND SYSTEMS

Electronics can be used to operate such safety devices as ice warning units (to warn the driver of a temperature approaching freezing point), direction indicators, speed warning devices, automatic headlamp dipping units and emergency flasher units.

One company has developed a system to prevent a car fitted with the system being driven if the seat belts are not correctly worn. This system cuts out the ignition to prevent the car from being driven unless the driver and passenger wear their seatbelts. Fig. 1 shows the system attached to a car, the system operation is as follows.

The weight of a person sitting on the seat operates a sensor in the seat Fig. 1c. The ignition circuit is then broken unless the seatbelt is correctly worn and the sensing circuit is com-

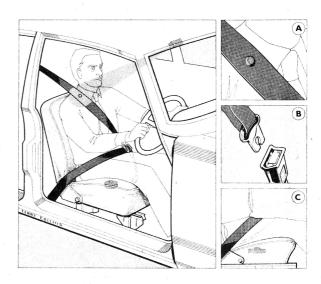


Fig. 1. The seat belt system developed by Mullard and the Ford Motor Company.

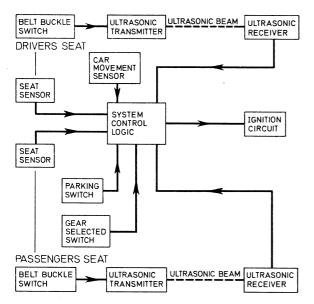


Fig. 2. Control logic of the system shown in Fig. 1.

plete. When the belt buckle Fig. 1b is closed, an ultrasonic transmitter mounted above the car windscreen emits a signal. If the belt is correctly worn across the driver's body then the ultrasonic signal beam will be picked up by an ultrasonic receiver on the belt, Fig. 1a, the signal at the receiver completes the sensing circuit and then the system logic closes the ignition circuit enabling the car to be driven.

The system has been designed to filter out short term interference from such things as cigarette smoke or quick hand movements across the ultrasonic beam. A delayed action and possibly some warning of pending ignition cutout would be required in the event of the seatbelt being removed whilst the vehicle was in motion.

The system control logic can be arranged so that the car can be parked or garaged in low gear or reverse without the need for the seatbelt to be worn by the driver. The block diagram, Fig. 2, shows a system with the facility for overriding control for parking as mentioned above.

The passenger seat sensor provides a signal to the system control logic if the passenger seat is occupied, the ignition circuit is then broken unless both seatbelts are correctly used. The delayed action and warning lamp control circuits would be built into the system control logic circuit, the warning lamp being flashed on and off to attract the driver's attention.

There are many safety systems which have been developed in the last few years, these include an experimental radar unit to give the driver warning of obstructions or vehicles ahead of his car in foggy conditions, there are also several anti-lock braking systems.

Anti-lock braking systems have been developed to prevent any one or all of the wheels of the car from locking and putting the car into a skid. A set of wheel sensors detect the onset of wheel lock and transmit a signal to the control unit which varies the operating pressure of a pressure limiting valve in the hydraulic brake line to the wheel brake cylinder, Fig. 3.

PERFORMANCE AND PERFORMANCE MEASUREMENT

There are two fields in which electronics can be used in connection with performance, the first production of performance, the second measurement of performance.

The two main types of electronic unit used in performance production are transistorised ignition systems and electronically controlled fuel injection systems.

Transistorised ignition systems fall into two types, transistor assisted ignition and capacitor discharge ignition. Transistor assisted ignition systems use a transistor amplifier switched by the contact breaker points to switch on and off a high voltage power transistor in the ignition coil primary circuit; since the transistor amplifier input current is small, and non-inductive arcing at the contact breaker points is virtually totally eliminated, point wear is greatly reduced; with the use of a high ratio ignition coil the ignition h.t. voltage is increased, raising ignition efficiency. This system can be used with contact breakerless ignition systems where the transistor amplifier is switched by a magnetic pickup in the distributor.

Fig. 4 shows the block diagram of a transistor assisted ignition system using a magnetic pickup in place of the conventional contact breaker. An oscillator in the amplifier unit connected to the

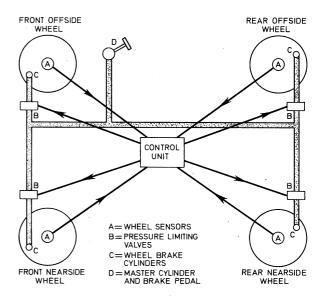


Fig. 3. Block diagram of an antilock braking system for vehicles.


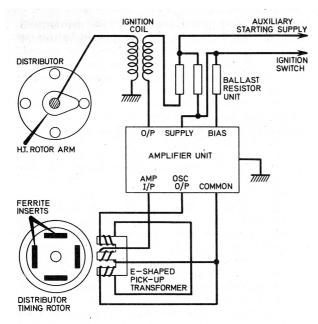


Fig. 4. A transistor assisted ignition system using a magnetic pickup.

pickup supplies a signal voltage to the input windings wound on the outer limbs of the "E" shaped pick-up transformer.

The signal voltage sets up a field around each outer limb, the two fields oppose one another and the magnetic fluxes produced in the centre limb are arranged to cancel, therefore the voltage induced in the output winding wound around the centre limb is very small.

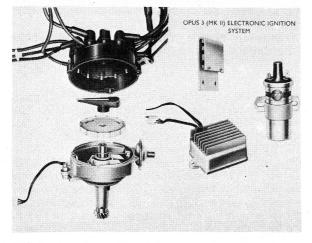When one of the timing rotor ferrite inserts passes the pick-up transformer, bridging the gap between one of the outer limbs and the centre limb of the transformer, the magnetic fields no longer cancel and the resulting flux induces a voltage in the output winding of the pick-up. The output from the pick-up is fed to the amplifier unit and the presence of a signal resulting



The Lucas Opus 3 (Mk I) ignition system using a magnetic pickup.

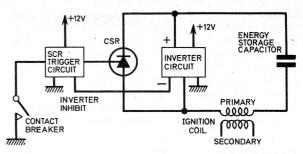


Fig. 5. A block diagram of a capacitor discharge ignition system.

from the ferrite insert lining up with the pick-up turns off the normally conducting power output transistor in the ignition coil primary circuit.

When the power output transistor turns off the current flow to the ignition coil, a large voltage is induced in the coil secondary, the h.t. voltage produced is switched to the appropriate sparking plug by the distributor h.t. rotor and ignition occurs.

Control of ignition timing with vacuum and centrifugal advance can be incorporated in this system by vacuum control of pick-up module position and centrifugal control of timing rotor position. The ballast resistor unit provides bias to the power transistor and also increased ignition coil voltage for cold starting.

This system requires much less maintenance than conventional ignition systems, and will operate efficiently at much higher engine speeds. Since this system is unlikely to go out of adjustment, correct timing is maintained resulting in more control of exhaust emission, fuel economy and constant performance.

Shown in Fig. 5 is the block diagram of a capacitor discharge ignition system. The inverter circuit running at about two thousand cycles per second and rectified by a high voltage bridge, charges the energy storage capacitor to a high voltage (approximately 500 volts).

When the contact breaker points close, the trigger circuit switches on the silicon control rectifier and the storage capacitor is connected across the ignition coil primary. The energy stored in the capacitor causes the coil primary voltage to reach, very quickly, a large negative voltage; the capacitor then discharges and the current in the coil primary passes through zero cutting off the thyristor.

The fast change in the coil primary induces a large voltage in the secondary which supplies h.t. to the plugs via the distributor head rotor arm.


This system will operate more efficiently than normal systems even with fouled plugs and gives easier starting with smoother running from cold. A standard ignition coil can be used since a high ratio coil is not required as used with transistor assisted ignition circuits.

Electronic fuel injection systems are now used on some production cars. One of the units used contains a plug-in printed circuit board plus power transistors mounted on a suitable heat-sink. The unit monitors engine temperature and inlet manifold pressure and operates the fuel injectors to deliver the correct amount of fuel for the operating conditions. Since the amount of fuel delivered is controlled, the efficiency of the engine may be inceased, and fuel economy together with pollution control may be achieved.

DIAGNOSIS

Separate measuring instruments are mainly used for setting up and checking that the car is properly tuned. Many garages have electronic tuning aids for measuring ignition settings and performance, battery charging circuit efficiency and engine performance. These instruments range from those displaying the measured performance on a meter to those displaying waveforms on a screen or giving a digital display or printout.

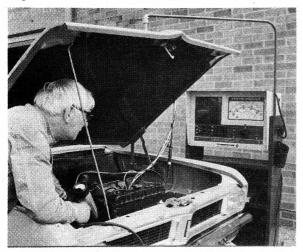With the use of an oscilloscope display unit, it is possible to monitor the ignition system performance with the engine running. By displaying on the screen the ignition coil primary



The Crypton "Motorscope" Mk VI engine analyser shown in use.

voltage waveform, diagnosis can be made of damaged plugs and fouled plugs, open-circuit h.t. cables, etc. The complete waveform for all the engine cylinders can be displayed and the faulty components associated with a particular cylinder can be pinpointed.


A network of dealers are now using a diagnosis system to check customers' cars; all new cars sold by the dealer network being fitted with sockets for connection to the diagnosis equipment, older models not fitted with sockets are connected to the equipment via adaptor leads. For each model to have diagnosis service a programme card supplies data to the diagnosis equipment controlling the tests carried out and giving the correct readings that should be

obtained for comparison, within the equipment.

After connection of the equipment to the car and programming the unit using the correct card, a digital display indicates the number of the test to be carried out and the value measured then appears on the digital display. If the measured value is within the specified limits the measured value is printed out on the test record which is presented to the customer at the end of the tests. Those operations and tests which are not automatically carried out are completed by the mechanic using a manual input unit.

The diagnosis covers steering, brakes, electrical equipment, tyre pressures, oil, brake-fluid, water levels, engine cylinder compression and engine dynamic tests. One test automatically carried out is measurement of wheel alignment which is measured by reflecting a projected light beam across a measuring plate; another check is to measure the battery fluid using a sensor mounted in the battery.

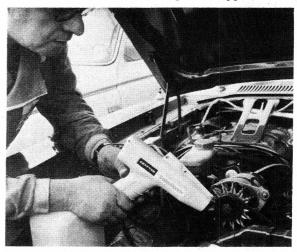Using this system allows a mechanic to check 88 test operations in about half an hour. The police also use electronics to check the speed of vehicles on the road using the Doppler effect




A Crypton timing light being used to set the ignition timing with the engine running.

to measure the speed of a car passing the radar unit.

The most widely used electronic instrument for measuring performance fitted to today's cars is the electronic tachometer unit; this device converts the pulses produced by the ignition circuit contact breaker points into meter deflection current, thus giving a meter reading proportional to the engine speed. The input to some tachometer units is taken from an input sensor which consists of a coil of a small number of turns wound around the contact breaker to coil connection wire.

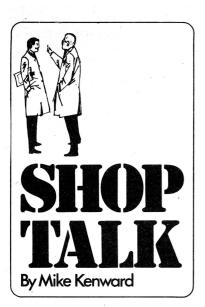Next month. This article will be continued and will cover car security, entertainment and communication.



Both our series of constructional projects concerning test gear (the E.E. Test Gear Five), which will finish next month when the R.F. Signal Generator is published, and last month's special supplement Test Gear may have aroused some interest in many constructors.

The section on multirange meters in the supplement started by saying: "A multirange test meter is probably the first and most useful item of test gear anyone is likely to purchase." This is, of course, quite true and if you do not have any test gear you should look at meters before anything else.

To get a worthwhile instrument you will probably have to spend about £8 or more. However, next month we are presenting an exciting opportunity for you to win a multimeter. A number of good quality meters will be presented as prizes in our free entry competition, so don't miss this chance.

Transistor Tester

One or two problems concerning components for the *Transistor Tester* may arise, mainly with the switches' specified. The miniature Maka switches should be generally available—if you have trouble one of the larger London based suppliers should be able to help. You will probably have to buy the parts separately and assemble them. The wafers used on the prototype were two 4 pole, 3 way (used for the 6 pole 3 way

switch) and one 4 pole, 3 way (used for the 4 pole, 2 way switch).

Obviously 2 poles are not used on the first switch and one "way" is not used on the second. The switch assembly has a "stop washer" which can be adjusted so that the switch will rotate only through the required number of positions.

The lever key switch is available from Farnell Electronic Components Ltd., Canal Road, Leeds, LS12 2TU. The switch is type MLK03 4CN/S and will only move in one direction, without locking. It will only have contacts on one side as shown in the wiring diagram. The switch costs 78p plus 3p for the handle plus 25p small order surcharge plus VAT—we make that about £1.17. Handles are available in a vast range of colours, red, dark green, blue, yellow, grey, ivory, maroon and black being the main onesstate colour required when order-

Electronic Bagpipes

Once again the problems with parts for the *Electronic Bagpipes* article seem to be confined to switches. This time very simple, small **press to break** switches which are available from a few of the larger suppliers. The switches should be miniature types—not exceeding about 35mm overall and must be **press to break**

The microswitch used for the on/off switch must be capable of

being operated when the side is squeezed and is best if it can be screwed to one side and operated by the other. Most types with a button operator are suitable.

Chanter material will depend on what is available but make sure the switches will go inside the connection tags may need bending over for this. Most other parts should be readily available.

Egg Timer

All parts for the *Egg Timer* should be generally available, although you may have to shop around a bit for the loudspeaker. The case used in the prototype came from Trampus Electronics. PO Box 29, Bracknell, Berks, but quite a few similar types are available from many suppliers.

Simple Buzzer

The Simple Buzzer is built around a balanced armature earpiece. The most important things to check when buying this is that the impedance is correct and that the whole thing can be taken apart. For this reason one of the ex. W.D. types in a plastic case will probably be best.

Stop Press!


The twin ganged potentiometer for the Audio Frequency Oscillator (March 1974) is available from Radio and T.V. Components Ltd., for a total cost of 75p including postage, packing and VAT.

PLEASE TAKE NOTE

In the Electronic Voltmeter article last month, Fig. 3 (page 28) some of the resistor numbers are shown incorrectly. The following alterations should be made to the drawing: R12 becomes R10, R8 becomes R7, R5 becomes R4, R10 becomes R8, the unmarked resistor is R5

In Demo Circuits last month (page 221) the formulae for inductive reactance and capacitive reactance are shown under the wrong headings, they should be transposed.

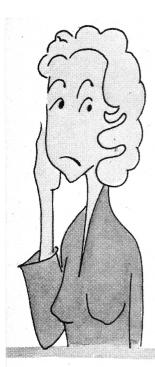
In Teach-In '74 Lesson 6, Fig. 6.3. The wire from B2+ve should go to the centre tag of S1. Lead from D2+ve should go to junction of R3/B1-ve.



... WELL! MAKE THE E.E.

EGG TIMER !

By R.A. PENFOLD

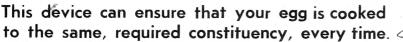

THE device to be described here is a timer which gives an audible warning when the set time interval has elapsed. Although designed specifically as an egg timer, it can be used for any application requiring an audible alarm output after up to five minutes (approx.).

This simple device is quite compact and it is completely self contained. Power is obtained

from an internal 9 volt battery.

Being a piece of household equipment, it must of course be easy to operate. There are only two controls, one being a dial on which the required period of time is set (this is continuously variable from 2 to 5 minutes), and the other is the on/off switch.

When the desired time has been set on the dial, the unit is turned on, and then left. When the set time has elapsed, an audible warning (a howling noise) is produced by the timer. This will continue until the unit is turned off, whereupon it is ready for use again.

The unit is not only suitable for use as an egg timer, but can be used on any process taking a similar time, providing a high degree of accuracy is not required.

BASIC OPERATION

There are really three separate circuits which comprise the timer, bistable and oscillator, and Fig. 1 shows these three stages, and the output waveform of each in block diagram form.

The first stage is the timing part of the circuit, and this produces a short, positive electrical

pulse at the end of the timing period. This pulse is used to trigger the second stage of the unit, and this is a bistable multivibrator, which is sometimes just termed a "latch", for reasons which should become obvious.

The latch is required in order to turn the short output pulse from the timer circuit, into a continuous positive output, which is used to operate the third stage. This is an audio oscillator which feeds a loudspeaker. Thus the short pulse from the timer circuit will cause a continuous tone from the loudspeaker which will persist until the unit is turned off

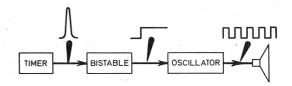


Fig. 1. The block diagram of the Egg Timer.



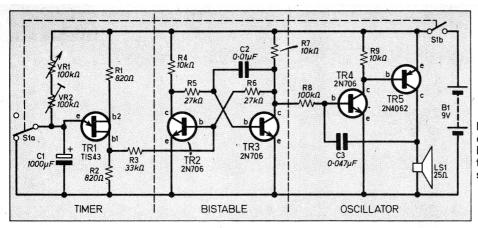


Fig. 2. The complete circuit diagram of the Egg Timer showing the three major sections.

THE CIRCUIT

A complete circuit diagram of the Egg Timer is shown in Fig. 2; dotted lines break the circuit into the three sections outlined above.

Transistor TR1 is a unijunction transistor, and the operation of this is completely different to that of an ordinary transistor. The unijunction has an emitter, two bases, and no collector. With no voltage present at the emitter terminal, the base 1 and base 2 connections of the transistor will have the characteristic of a resistor with a value of a few kilohms between them.

With reference to Fig. 2, with S1 in the on position, there will be a potential of about one volt at TR1 base 1. The input resistance to the emitter of TR1 will be extremely high at low voltages, perhaps several hundred megohms, therefore C1 will begin to slowly charge through VR1 and VR2.

Since C1, VR1 and VR2 all have high values, the voltage across C1 will increase slowly.

Eventually, when there is a potential of a few volts across C1, the triggering point of TR1 will be reached. When this happens, the input resistance to the emitter of TR1 drops to a very low level, and C1 will discharge very rapidly. As this occurs, the resistance between TR1, base 1 and base 2 will drop to about half it's previous level, thus causing the voltage at base 1 to rise to about 4 volts. This will only last for the time it takes for C1 to discharge (a fraction of a second), and then the circuit returns to the beginning of the cycle.

Both VR1 and VR2 can alter the time taken between turn on, and the pulse at TR1 base 1. Potentiometer VR2 is a preset type connected as a variable resistor which is adjusted so that VR1 (which is fitted on the front panel of the timer, and has the dial marked around it) covers the required range of 2 to 5 minutes. Component VR2 has to be a preset, rather than a fixed resistor, so that compensation for the wide tolerances of the electrolytic capacitor used for C1, can be made. The tolerance of this component can be as much as plus 100 per cent and minus 50 per cent.

BISTABLE MULTIVIBRATOR

Transistors TR2 and TR3 form the bistable. When the supply is turned on, the voltage at the collector of each transistor will begin to rise. Due to the component tolerances, the voltage at one collector will rise more quickly than that at the other collector. To ensure that the voltage rises more quickly at the collector of TR2, C2 has been included.

As the voltage at TR3 collector rises, this rise will be coupled by C2 to TR3 base, where it will have the effect of reducing the voltage at TR3 collector. The effect of C2 is only slight, but is enough to ensure correct circuit action.

The voltage at TR2 collector will therefore rise quickly to almost the full supply potential, and this will be coupled through R5 to TR3 base, causing the potential at TR3 collector to go to almost zero. Thus each time the unit is switched on, TR2 will be off (not conducting) and TR3 will be fully on (conducting).

Base 1 of TR1, and the base of TR2 are coupled by R3. Therefore, when base 1 goes positive at the end of the timing period, TR2 base will also go positive. This will cause TR2 collector to go more negative. Because the collectors, and bases of TR2, and TR3 are cross coupled by R5 and R6, a regenerative action will take place. The base of TR3 will go more negative, causing TR3 collector to go more positive, bringing us full circle back to TR2 base which will go still more positive. This regenerative action will continue until the transistors have changed states, with TR3 collector at nearly full supply potential, and TR2 collector at almost earth potential. In other words TR2 is fully on and TR3 fully off.

It is seen from this that the bistable will have only a small output voltage until it is triggered by the short output pulse from TR1, whereupon its output will rapidly swing to a high level, and stay at this level.

AUDIO OSCILLATOR

The audio oscillator is formed by TR4, and TR5. These are both operated as common emitter amplfiers, R9 being the collector load


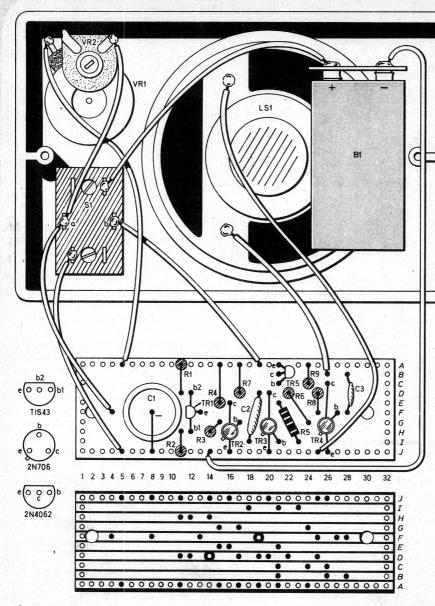


Fig. 3. The layout of the components on the Veroboard wired to the components mounted in the case.

Photograph showing the completed Egg Timer.

EGG TIMER

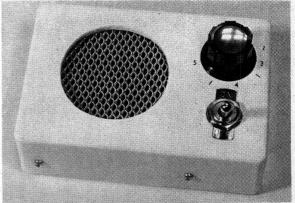

Components....

Res	istors

K1	82077
R2	820Ω
R3	33 k Ω
R4	10k Ω
R5	27kΩ
R6	27kΩ

SHOP TALK

R7 10kΩR8 100kΩR9 10kΩ

All ¼W carbon ±10%

Capacitors

C1 1000 µF elect. 10V

C2 0·01*μ*F C3 0·047*μ*F

Semiconductors

TR1 TIS43 unijunction

TR2, 3, 4 2N706 silicon npn (3 off)

TR5 2N4062 silicon pnp

Miscellaneous

VR1 $100k\Omega$ carbon lin. VR2 $100k\Omega$ preset lin.

S1 double-pole double throw toggle or

slide switch

LS1 25 ohm loudspeaker approx. 70mm

diameter B1 9 volt PP3

Veroboard, 0-1in. matrix size 10 strips by 32 holes; speaker fret; connectors to suit B1; plastic case size 110 x 72 x 30mm or larger; knob.

resistor for TR4, and LS1 is the collector load for TR5. The input, and the output of the circuit are in phase, and C3 will therefore introduce positive feedback, which will cause the circuit to oscillate when a suitable biasing current is present at TR4 base.

However, the biasing resistor, R8, is connected to the output of the bistable, and will normally be at a very low potential, and will not introduce a proper biasing current. At the end of the timing period when the output of the bistable changes to a higher potential, then the required biasing current is introduced, and the circuit will then oscillate, producing an audible tone from LS1.

When the circuit is turned off, S1a shorts across the terminals of C1, ensuring that this is fully discharged, and that the unit is immediately ready for use again.

CONSTRUCTION

Most of the components are mounted on piece of $0 \cdot 1$ in. matrix Veroboard size 10 strips by 32 holes as shown in Fig. 3. All the components with the exception of R5 are mounted vertically.

Begin construction by making the breaks along the copper strips on the underside of the board and then drill the two fixing holes for 6BA clearance (No. 31 twist drill). Now position and solder all the resistors and capacitors in place as detailed and then position and solder the transistors in place using a heatshunt to avoid thermal damage.

The prototype Egg Timer was housed in a commercially available plastic case, size $110 \times 72 \times 30$ mm (internal dimensions). Any case of similar size is equally suitable but do not choose one that is any smaller than employed on the prototype otherwise it may be impossible to fit all the components into it.

Should a metal case be used, steps must be taken to insulate the Veroboard panel from this, and it should be ensured that no other parts are in electrical contact with it.

Make the necessary cut-outs and holes in the case to suit the components and board fixings and then secure the remaining components in position as indicated in Fig. 3.

A cut out about 50mm in diameter should be made in the front of the case, where the loudspeaker is to fit, and a piece of speaker fret glued to the inside of the case to cover the hole. The speaker is then glued to this.

As can be seen, the preset potentiometer VR2 is soldered directly to VR1. Either a horizontal or a vertical mounting type can be used, but in either case it should be orientated so that it can be easily adjusted when soldered in place. Now wire up according to Fig. 3 and when completed fix the board to the inside of the case as shown in Fig. 4.

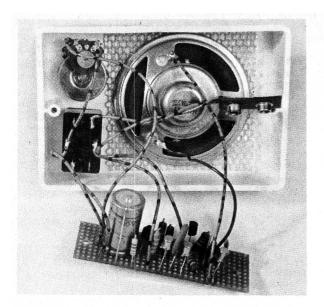


Fig. 4. The completed unit with lid removed.

No battery bracket is detailed as this was found unnecessary; a piece of foam rubber below and above the battery will hold it securely in position when the lid is screwed on.

ADJUSTMENT AND CALIBRATION

The only adjustment required is that of VR1. This should be set with the slider half way around the track at the outset; VR2 is adjusted




Photograph of the completed unit with battery and board removed.

for minimum resistance (turned fully anti-clockwise), and the unit is turned on.

If it is functioning correctly, after about two minutes the alarm will sound. The exact time taken should be monitored. If it takes less than two minutes, the resistance of VR1 must be increased, and if it takes more than two minutes, the resistance of VR1 must be decreased. The

process should then be repeated until it takes two minutes (plus or minus a few seconds) for the alarm to sound, from when the timer is turned on.

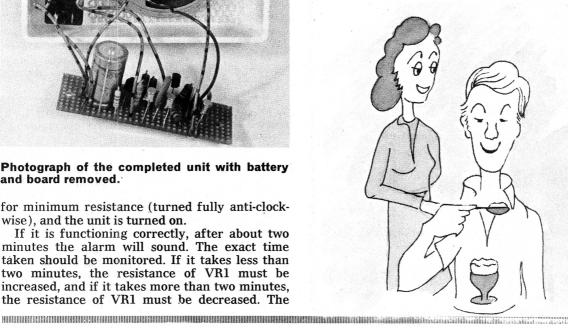It is then necessary to calibrate a scale around the control knob of VR2. The two minute has already been found, and now every half minute point up to five minutes must be found, by trial, and error. This is a lengthy business, but there is unfortunately no short cut to this.



Ruminations By Sensor

A Woman's Work

I suppose that those people unacquainted with the electronics industry tend, when thinking of it, to give it a masculine imageserious looking men with slide rules in their top pocket, scribling abstruse calculations and speaking to each other in a near incomprehensible jargon. while men like these undoubtedly exist, for they are the visionaries and the innovators without whom the industry would soon stagnate, women dominate the scene to a remarkable extent.

In some branches of the industry women make up 95 per cent of the workforce and their jobs range from assembly work (of all degrees of complexity) through planning, drawing office, laboratories and inspection and testing right through to senior management level.

Women, of course, also occupy the secretarial and clerical positions. I knew two young women who gave up secretarial jobs in order to work on the bench, both felt that bench work was much more satisfying than their former jobs and enabled them to employ themselves creatively. Although working conditions were not as good, and the hours worked a little longer than those they enjoyed formerly, they had no regrets about their change of occupation.

As You Like It

I once asked a woman who was doing a minor repetition job, how she could do the same thing day after day without becoming bored beyond endurance. She replied that she enjoyed the work because it left her mind free to think of other things! I have since found this to be a useful way of approaching one's own chores. We all have boring work to do at times, and if we let our hands work automatically we can daydream, think or plan to our hearts content; thus viewed, a monotonous task can be a welcome respite from more demanding employment.

Many of the jobs done by women in the electronics and electrical industries are very demanding indeed and require a high degree of skill. I am thinking, particularly, of some of the soldering work such as soldering the "hair" springs on to a microammeter-a steady hand and a good eye together with a great deal of patience, are essential; I know-I've tried it myself.

Look around your home and you will see the work of our womenfolk-the electricity meter, the light bulbs and electrical fittings, even the wire that connects them together, the T.V., radio and all the domestic appliances were built or made almost entirely by women. And when you reach for the telephone you are touching a woman's work again.

Everyday Electronics, May 1974

SEMICONDUCTOR PRIMER

By A.P. STEPHENSON

11= IMPORTANT TRANSISTOR CURVES

Graphs showing the effect of base current and collector voltage on the collector current.

Although collector current is very sensitive to base current, it is hardly affected by collector *voltage*. The graphs in Figs. 11.1 and 11.2 illustrate.

Note


If base current is increased, the collector current also increases by a much greater amount.


The ratio $\left(\frac{\text{base current}}{\text{collector current}}\right)$ is called the forward current gain h_{FE} . In Fig. 11.1, for example, $h_{\text{FE}} = 100$.

Note

Unlike the base, the collector voltage is unable to change the collector current by any appreciable amount (except for very low voltages).

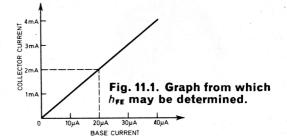As far as collector voltage is concerned, the transistor behaves almost as a **constant current** device see Fig 11.2.



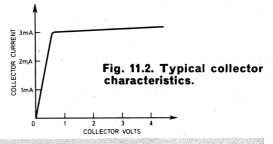

12 BC107, BC108, BC109 TRANSISTORS

These form a useful trio for general audio or video circuitry and have the advantage of cheapness (about 10p each) and easy availability in almost any district.

They are silicon *npn*, planar epitaxial transistors encased in TO-18 form. **BC107** is a higher voltage version, quite suitable as a driver for

audio output stages.

BC108 is a general purpose "dogsbody".

BC109 is a low noise version, particularly suitable as an input stage for low level signals.

For military use, they arrive disguised as:

CV 0374882 CV 0375395 CV 0375627

(BC107) (BC108) (BC109)

BRIEF SPECIFICATION

PARAMETER	BC107	BC108	BC109	UNITS
V _{CE max} .	50	30	30	V
I _{C max} .	200	200	200	mA
Power dissipation max at <25°C	300	300	300	mW
T _{J max} .	175	175	175	deg. C
h_{FE} (at $I_C = 10\mu A$, $V_{CE} = 5V$) (at $I_C = 2mA$, $V_{CE} = 5V$)	90 180	150 300	270 500	typical
h_{fe} (at $I_{\text{C}} = 2\text{mA}$, $V_{\text{CE}} = 5\text{V}$) measured at 1kHz	125 500	125 500	240 900	minimum maximum
$f_{\rm T}$ (at $I_{\rm C}=10{ m mA},\ V_{\rm CE}=5{ m V}$)	300	300	300	MHz
$V_{\rm CE}$ saturation voltage when $\frac{I_{\rm B}}{I_{\rm C}} = 20$	300	300	300	mV
NOISE at $I_C = 200\mu A$, $R_s = 2k\Omega$ (max) at 1kHz B = 200Hz	10	10	. 4	dB

Everyday Electronics, May 1974



Interference

I want to fit a radio in my car. How do I go about suppressing the engine?

The main sources of interference are from the sparking plugs, the generator brushes and the coil. To overcome the loud clicking type of interference from the plugs you must suppress the leads from the distributor to the plugs. Modern cars are usually fitted with carbon leads that are already suppressed and in those cases you need not worry (in fact you will degrade your engine's performance if you try to insert suppressors). You can buy plug suppressors which are in the shape of plug caps; these screw into the cables running from the distributor-all they consist of are high value resistors that go in series with the normal plug lead.

To cure coil interference—which again is a clicking noise—connect a $0 \cdot 1 \mu F$ capacitor between the coil's connection to the contact breaker and ground (the car's chassis). Noise from the generator is a loud whine that rises and falls in pitch as you rev the engine. Again connect a $0 \cdot 1 \mu F$ capacitor between the generator's main output connection and ground—the main connection of the generator is usually the larger terminal. Do not connect the capacitor between the field coil terminal and ground.

Should interference still persist tighten up the battery connections, check the aerial is properly fitted to the radio and make sure the aerial lead's screening is well connected to the car's chassis at the aerial end. Worn cut-out contacts can produce spurious interference which is difficult to identify. The $0\cdot1\mu F$ capacitors we mention can be purchased from any auto spares shop and usually have the correct sized terminals to make fitting easy.

Hum Loop

Someone told me it is good practice to earth a hi fi system—not only for safety reasons but to remove hum. My amplifier was earthed but I had a bit of hum so I earthed the record player only to find the hum got worse. Is there any logical reason for this?

It sounds as though by earthing the record player you have introduced what is called "an earth loop". This is very easy to do and is often a very bad source of hum. Certainly your system should be earthed, but the connection back to the main earthing point (in your case we suspect this was the mains plug) should be by one route only. By connecting separate earths (a) from the amplifier and (b) from the turntable unit to separate (?) mains plugs you form an inductive loop (from the mains earth through the chassis of your amplifier, down the coaxial screening, through the chassis of your turntable and back to mains

If you are unfortunate and have a transformer or similar inductor in the system carrying 50Hz mains the earth loop will pick up currents by induction from the source and this signal is superimposed on your pick up signal giving rise to the worsening hum. It is better to earth the amplifier and make sure that the screening of your pick up cable is grounded to the amplifier's chassis at one end and to the turntable unit's chassis at the other. This way the whole system is earthed but you do not introduce any loops.

Battery Leakage

My electronic flash gun runs off dry batteries and unfortunately these leaked and made a mess inside. However I cleaned out the battery compartment but it still won't work. Could the material from the batteries have caused any problem

or is it more likely to be something else?

Almost certainly the material from the battery is the cause of the malfunction. You must check the circuitry inside the gun and remove all traces of the paste. It can cause leakage across capacitors, bridge gaps in printed circuit boards and worse still will actually dissolve the copper from circuit boards. If you see green deposits on the copper wiring of the circuit you can bet that the last has occurred and you may have to do a bit of re-wiring.

If you do attempt to have a go yourself be warned; very high voltages at high currents are present in electronic flash guns—do not be deceived by the small batteries! So, be careful if you test it out when it is not in its case; in particular do not touch the terminals of the main capacitor unless you have discharged it first with an insulated handled screwdriver!

Transistor Selection

Your instructional articles always make the operation of a transistor seem very simple and it seems that the only parameter of importance is the $h_{\rm te}$. Is this true, and if so why are there so many different types?

It is true that $h_{\rm fe}$ is a very important parameter but there are other obvious ones that are just as critical. There are also a few less obvious ones. One has to consider the reverse breakdown voltage across the base/collector and base/emitter junctions— $V_{\rm cbo}$ and $V_{\rm ebo}$; also the breakdown voltage between collector and emitter ($V_{\rm ceo}$). There is always a limit to the collector current you can draw through the device before it fuses internally ($I_{\rm cmax}$).

A transistor cannot dissipate unlimited power without overheating. Too high an operating temperature changes the base emitter forward voltage drop and this effects the biasing conditions. There is thus a complicated link between power dissipation and operating characteristic—apart from the obvious effect of excessive dissipation melting connections inside the device and ruining it.


Maximum power dissipation

Everyday Electronics, May 1974

electronics really mastered

... practical ... visual ... exciting!

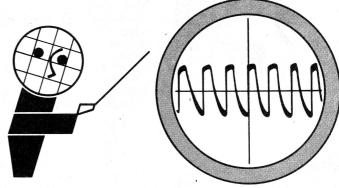no previous knowledge no unnecessary theory no "maths"





RAPY


BUILD. SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

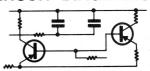2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT
OVER
40 EXPERIMENTS
ON BASIC ELECTRONIC
CIRCUITS & SEE HOW
THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW BROCHURE

To: BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL,

P.O. Box 156, JERSEY. Please send your free brochure, without obligation, to:

we do not employ representatives

BLOCK CAPS

or write if you prefer not to cut page

ADDRESS

NAME

PLEASE EEL 5.4.

special free gift also to all our students



An A to Z guide to component buying

On the index page of Catalogue 7, between "Aluminium Boxes" and "Zener Diodes" are over 200 references to contents amounting in all to thousands of items, classified, described, often priced and illustrated. There are many technical diagrams and data. At 25p, Catalogue 7 is excellent value by any standard. With the 25p Refund Voucher it costs you virtually nothing when you order £5-worth or more.

25p INCLUDING 25p REFUND VOUCHER ALLOW-ABLE ON ORDERS £5 OR MORE NET VALUE

A SELECTION FROM EV CATALOGUE 7

TRANSISTORS and semi-conductors of many types from simple diodes to ICs photo-sensitive devices, threshold switches, etc. etc.

MINITRON DIGITAL INDICATORS
3015F Seven segment filament, compatible with standard logic modules. 0-9 and decimal point; 9mm characters in 16 lead DIL. Now available in 8mA or 15mA segment ratings £1·20. Suitable BCD decoder driver 744T £1·15.
3015G showing + or — &1 & dec. pt. £1·29.

DALY ELECTROLYTIC CAPACITORS

in cans, plastic sleeved 1000mF/25V 28p 1000/50 41p 5000mF/25V 62p 2000/50 57p 5000/50 £1 18 5000/100 £2.91

POLYESTER CAPACITORS TYPE C.280
Radial leads for P.C.B. mounting, Working voltage
250V d.c.

0.01, 0.015, 0.022, 0.033, 0.047 ea. 3p 0.068, 0.1, 0.15 ea. 4p 0.22 5p; 0.33 7p; 0.47 \$p; 0.68 11p; 1.0 14p; 1.5 21p; 2.2 24p.

SILVERED MICA CAPACITORS
Working voltage 500V d.c.
Values in pFs-2-2 to 820 in 32 stages, each 6p.
1000, 1500 7p; 1800 8p; 2200 10p; 2700, 3600 12p;
4700, 5000 15p; 6800 2pp; 8200, 10,000 25p.

POTENTIOMETERS

ROTARY, CARBON TRACK, Double wipers for good contact and long working life

P.20 SINGLE linear 100 ohms to 4.7 megohms. ea. 14p.
P.20 SINGLE log. 4-7 Kohms to 2-2 megohms,

ea. 14p. JP.20 DUAL GANG linear 4·7 Kohms to 2·2 meg-

ohms, ea. 42p. JP.20 DUAL GANG log. 4.7 Kohms to 2.2 megohms. ea. 48p. JP.29 DUAL GANG Log/antilog 10K, 22K, 47K,

JP.29 DUAL GANG Log;antilog 10K, 22K, 4/K, 1 megohm only ea. 48p.
JP.29 DUAL GANG antilog 10K only, 48p.
ZA DP mains switch with any of above 14p extra.
Decades of 10, 22 and 47 only available in ranges

SLIDER POTENTIOMETERS
Linear or log. 10K to 1 meg. in all popular values ea. 30p.

Escutcheon plates, black, white or light grey, ea. 10p

Control knobs blk/wht/red/yel/grn/blue/dk. grey/
It grey, ea. 6p.

ELECTROLYTIC CAPACITORS Axial Lead

aF .	3V	6-3V	10V	16V	25V	40V	63V	100V	
0.47	-	-	-	-	-	-	11p	8p	
1.0		-	-	-	-	11p	-	8p	
2.2	-			-	11p	-	8p	9p	
4.7	-	-	-	11p	_	8p	9p	8p	
10	-			_	8p	8p	8p	8p	
22		-	8p		9p	8p	8p	10p	
47	8p	-	9p	8p	9p	8p	10p	13p	
100	9p	8p	8p	8p		10p	12p	19p	
220	8p	8p	9p	10p	10p	11p		28p	
470	9p	10p	10p	11p	13p	17p		45p	
1,000	110	13p	13p	17p	20p	25p	41p		
2,200	15p	18p	23b	26p	37p	41p			
4,700	26p	30p	39p	44p	58p		-	_	
10 000	420	40				200			

Available on all items except those shown with NETT PRICES, 10% on orders from £5 to £15, 15% on orders £15 and over.

PACKING AND POSTAGE FREE in U.K. For mail orders for £2 list value and under, there is an additional handling charge of 10p. **GUARANTEE OF QUALITY**

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, 'seconds' or sub-standard merchandise is offered

V.A.T. Prices quoted do not include V.A.T., for which 10% must be added to total nett value of order. Prices subject to alteration without notice. S.A.E. with written enquiries please.

RESI	STORS				
Code	Watts	Ohms	1-9	10-99	100 up
_	4 100			(see n	ote below)
C	1/20	82-220K	9	8	7.5
C	1/3	4 · 7-470K	1.3	1.1	0.9 nett
CCC	1/2	4 · 7-10M	1.3	1-1	0.9 nett
C	3/4	4 · 7-10M	1.5	1.2	0.97 nett
C	1	4 · 7-10M	3.2	2.5	1-92 nett
MO	+	10-1M	4	3.3	2·3 nett
ww	1	0.22-3.9	9	8	8
ww	3	1-10K	7	7	6
ww	7	1-10K	8	8	8
Code	s: C-ca	rbon film, h	nigh sta	ability, lo	w noise.

Codes: C—carbon film, high stability, low noise.

WW—wire wound, Plessey.

Values: All E.12 except C1/3, C3/4, MO 1/2

10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their

10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24; as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades. Tolerances: All 5% except MO 1/2 at 2%, WW. at $10\%\pm0.05\Omega$ Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) 100 price rates for units of 100 only.

ZENER DIODES full range E24 values: 400mW: 2-7V to 36V, 14p each; 1W: 6-8V to 82V, 21p each: 1-5W: 4-7V to 75V, 48p each, Clip to increase 1-5W rating to 3 watts (type 266F) 5p.

TRANSFORMERS—MAINS MT3 30V/2A plus 4 taps MT103 50V/1A plus 4 taps MT104 50V/2A plus 4 taps MT127 60V/2A plus 4 taps 13TO5 13V/3A, CT 28TO5 + 12V, 2-0-2V £3 · 70 £3 · 40 £4 · 70 £5 · 10 £1 · 66 £1 · 70

GIRO ACCOUNT No. 38/671/4002

All postal communications, mail orders etc. to Head Office at Egham address, Dept EE.4.

28, ST. JUDES ROAD, ENGLEFIELD GREEN EGHAM, SURREY TW20 0HB Telephone Egham 3603; Telex 264475. Shop hours: 9-5.30 daily. Sats. 9-1.0 p.m.

NORTHERN BRANCH: 680, Burnage Lane, Burnage Manchester M19 1NA Telephone (061) 432 4945

Shop hours: 9-1 and 2-5.30 daily. Sats. 9-1.0 p.m.

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

(Ptot) has to be specified for a certain temperature differential between the device and its surroundings and whether or not the transistor is on a heat sink. Some not so obvious parameters are that the $h_{\rm fe}$ of a transistor varies depending on the level of collector current: a high collector current causes noise generation inside the device (when amplified it sounds like background hiss) and this is undesirable in the front stages of hi fi amplifierssome transistors are specially selected to have low noise.

The diode capacities of reverse biased junctions in the transistor can influence high frequency circuits and must be allowed for in circuit calculations as must any internal resistance the transistor might have.

Transistors are designed, manufactured and selected to meet permutations on all these parameters (plus a few more) so you can see why there is such a vast number of different types—apart from obvious differences like silicon/germanium, or pnp/npn.

Wire Size

When winding coils (e.g. aerial rods or suppression inductors) I can see it is desirable to keep to the right number of turns—this, presumably, sets the inductance—but is the wire thickness important because you usually specify an s.w.g. number?

There are some instances where wire thickness is not important but as a general rule we suggest

you stick to recommendations. The coil might be carrying high current (suppressors) and unless the wire is heavy enough it might overheat. In the case of aerial rods, the length of the coil around the rod might be an important factor in setting the inductance (as might be the spacing between turns); changing the wire gauge might affect these.

At high frequencies (short waves) one should always use thicker wire because the a.c. currents only flow along the outer edges of the conductor (skin effect) and to avoid excessive internal d.c. resistance (which reduces the efficiency or "Q" of a tuned circuit) you need as large an outer circumference as possible. Sometimes multistrand (Litz) wire might be specified for the same reason. When winding bobbins for high value inductors it may not be possible to get sufficient turns on if you use a heavier gauge.

Microphony

I have quite a good quality amplifier with a microphone input. If I connect a crystal microphone to this input (which is supposed to be matched for a high impedance input) I get very good reproduction but when I kick the microphone cable I get a "clunking" noise in the loud-speaker. This is not due to pick up in the microphone as I have done this with a very long extension cable—it even happens with no microphone connected to the end! I am using coaxial cable

so I cannot see what can possibly be causing the trouble which, while not disastrous, is a bit of a nuisance.

This effect is quite common particularly with high input impedance amplifiers fed from a predominately capacitive source (such as a crystal microphone). The cause is the capacitance between the central core and the screening of the cable you are using. When you kick the cable, or bend it quickly, you can change the spacing between the core and the screen by a small amount (due to the deformation of the insulating sleeve between them). This change in spacing gives a rise to a very small change in the cable's capacitance.

If there is any standing potential on the core a minute current will flow into, or out of this localised change in capacity. This current is amplified by your system and gives rise to the "clunk" you can hear. We say the cable is microphonic. There are two solutions. The first is to ensure that the cable contains twin conductors one of which is connected to the outer screening at both ends.

A more expensive way—which will give you better results with a crystal microphone—is to make a microphone pre-amplifier that will reduce the output impedance of the microphone. This should be connected into the circuit as close to the microphone as possible—you can then use much longer cables without affecting the low frequency response and use the low impedance input of your main amplifier.

JACK PLUG & FAMILY...









By GEORGE HYLTON

"Is there any simple way of telling how impedance varies with frequency?"

No, there isn't. There seems to be a lot of confusion about the meaning of "impedance". Some people seem to think that impedance must imply a circuit with capacitance or inductance in it—it ain't necessarily so.

A square is a rectangle but all rectangles aren't square. A circuit which offers impedance may contain capacitance or inductance, but it could contain just resistance, and nothing else.

IMPEDANCE

Impedance is a general term, which includes resistance, inductive reactance, capacitive reactance, or any combination of these. Impedance, in a.c. circuits, is like resistance in d.c. ones. It describes the ability of a circuit to impede the flow of current, irrespective of what is doing the impeding.

A 100 ohm resistor has an impedance of 100 ohms. In this case, the impedance doesn't vary with frequency. But a $1\mu F$ capacitor has an impedance which decreases as the frequency increases, while a 1 henry inductor has an impedance which increases with frequency. But place this inductor and capacitor in series and you find that the impedance of the combination varies with frequency in an unexpected way.

At low frequencies it's high. At high frequencies it's high. But at about 160Hz it is very low. Place the same two components in parallel, and the combined impedance is low at all frequencies except near 160Hz, when it becomes very high. Impedance can be very puzzling.

REACTANCE

What some people mean by "impedance" is the special kind which should be called reactance,

that is, the impedance of a capacitor or an inductor. These impedances vary with frequency, and although measured in ohms are really rather special quantities. They have a sort of polarity; if you think of inductive reactance as positive then capacitive reactance is negative. This explains the strange behaviour of the series and parallel *LC* circuits.

SERIES AND PARALLEL

The starting point for this understanding is a knowledge of the net resistance of two resistances in series and parallel:

Series combination R = R1 + R2

Parallel combination R = R1R2/(R1+R2)

The rules for two impedances Z1 and Z2 are the same:

Series combination = Z1+Z2

Parallel combination = Z1Z2/(Z1+Z2)

On the face of things, this doesn't seem to cast any light on LC circuits and their resonant frequencies. But that's because we haven't put the signs in If Z1 is an inductive reactance, and Z2 a capacitive reactance, then to allow for the "polarity" if we put Z1 for inductive reactance we must put -Z2 for capacitive reactance.

Thus the series LC circuit has an impedance of Z1-Z2, and it's obvious that if Z1 and Z2 each have the same number of ohms, as they must have at one special frequency, then the combination has an impedance of zero.

The parallel combination becomes a fraction with -Z1Z2 at the top and Z1-Z2 at the bottom, and if Z1-Z2=0 the combination is something divided by

zero. As any mathematician will tell you, the result of dividing any number by zero is an infinitely large number. Hence the very high impedance of the parallel *LC* circuit at its resonant frequency.

OPERATOR "i"

There's just one snag. The simple "positive inductive, negative capacitive" approach gives the parallel-resonant LC circuit a negative impedance. Measurement shows that this is not so. At resonance, the impedance is just a high resistance. So the simple "positive-negative" approach isn't the whole story. In order to make the maths correspond with reality, mathematicians play a trick. They call the inductive reactance jZ1 and the capacitive reactance — jZ2.

The series LC circuit is now jZ1-jZ2=j(Z1-Z2) which is zero, as before, when Z1=Z2, since $j\times 0=0$. The parallel LC circuit becomes:

$$\frac{(jZ1) \times (-jZ2)}{jZ1 - jZ2} \ = \ \frac{-j^2 Z1Z2}{j(Z1 - Z2)}$$

and when Z1=Z2, this becomes $-j^2Z1Z2/0$, which is infinity times $-j^2$. Now comes the clever bit. Let $-j^2=1$. So infinity times $-j^2$ becomes infinity times 1, or just plain infinity.

That embarrassing negative sign has disappeared. The "j" is called an "operator", which is a mathematical name for something you invent to make it possible to get your sums right, and which obligingly disappears from the scene when you've finished.



"He constructed a device, fixed it to the lock and opened the door —I knew we shouldn't have let him subscribe to EVERYDAY ELECTRONICS!"

PLUGS
Pack 107 5 pin Din 25p
Pack 108 3 pin Din 20p
Pack 135 ½" Jack 30p
Pack 134" Jack Stereo 50p
Pack 103 Loudspeaker Plug 20p
Pack 100 Phono Plug 10p
Pack 230 3 pin Socket 35p
Pack 234 L/speaker Socket 35p Pack 234 L/speaker Socket READY MADE LEADS 3 pin to 3 pin Din 35p 70p pin to open end pin to 5 pin Din 55p pin to open end pin to 4 phono plugs 70p All leads approx. 6ft. in length. Speaker lead Din to spade 50p Extension lead Din plug to socket 12ft.

DIAMOND STYLI 8TA; 9TA; 9TAHC; GP91; ST4; ST9; EV26; GC8 All at 80p each. Double Diamond £1 .25. Diamond suitable for Orbit NM22; G800; M3D £2.25 each. Orbit

HEADPHONES Sennheisser HD414 AKG K50 £12.50 £6.50 £35 · 00 Beyer DT48S

RECORD CARE ecil Watts Dust Bug £1 .20 Parastatic Disc Preener 45p Antistatic Fluid 20p Dust Bug Spares (Brush & Roller) Prices inc VAT and Post.

Prices correct when going to press but subject to change without notice

CASSETTE TAPES

Audio-Magnetics C60 £1.00 £1.90 £3.20

5" Standard 600ft 51" Standard 900ft

(Blue or green)

MICROPHONES

Sennheisser MD211N

Sennheisser MD413N

E.M.I. 350 Kit 8 ohms E.M.I. 450 Kit 8 ohms

Sonotone 9TAHC (Dia) Sonotone 8T4A (Dia)

Ronnette 105 (Dia)

Audio RMS7F Radio Mike

AKG D109 AKG D202EI AKG D190C AKG D190E

AKG D224

Sony ECM50

SPEAKERS

CARTRIDGES Goldring G800 Orbit NM22 Shure 75/6

Cassette Caddy £1 · 20
Cassette Head Cleaner 35p

ZONAL ILFORD TAPE

7" (Plain boxed) 1200ft 7" (Westminster Boxed)

1800ft. Reel of Leader Tape

£6.30

£1 .25

75p

£12.65

£43 · 45 £18 · 70

£20 · 02

£55.00

£49.50

£29.70

£93.50

£231 · 00

£4.50

£4.00

£6.00

£2.00

J. Francis (WOOD GREEN) Ltd. MANWOOD HOUSE, MATCHING GREEN, HARLOW, ESSEX CM17 0RS Tel: Matching 476

SOURNAITEMKII **ELECTRONIC IGNITION KIT**

COMPRISES

Ready Drilled Case and Metalwork, Cables, Coil Connectors, Silicon Grease, Printed Circuit Board, 5 year guaranteed components and a full 8-page instruction leaflet

WHEN COMPLETE THE UNIT CAN BE FITTED TO YOUR CAR IN ONLY IS MINUTES USING THE STANDARD COIL AND CONTACT BREAKER POINTS: TO GIVE YOU:— BREAKER

Instant all weather starting, Up to 20% fuel saving, Longer battery life, Higher top speed, Faster acceleration, Spark plugs last about five time longer, Misfire due to contact breaker, bounce electronically eliminated, Purer exhaust emission resulting in less air pollution, Contact breaker burn eliminated.

Suitable for all petrol engines up to 8 cylinders

KIT PRICE ONLY £11-62

Ready Built Car Unit £14-85 Single coil C.B. Motor Cycle Unit £17-60 Twin coil C.B. Motor cycle unit £23-24 Triple coil C.B. Motor cycle unit £27.50

(prices include V.A.T. and post & packing)

When ordering state positive or negative earth and 6 or 12 volt.


MOTOR CYCLE UNITS NOT AVAILABLE IN KIT FORM ORDER NOW FROM

ICE ELECTRONIC SYSTEMS DEPT E.E. 114 PARK FARM ROAD BIRMINGHAM B43 7QH

AMTRON WENTILATED METAL CASES

Ideal for Stabilised Power Supply Units. A lightweight case with per-forated sides and top. The front panel

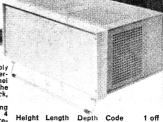forated sides and top. The front panel is of heavy gauge anodised all. The top, bottom, sides and back interlock, secured by 4 screws.
The front frame is a clever moulding holding the panels allowing for 4 hidden fixings for a chassis if required (not supplied). Integrally moulded front feet also form the mounting for the tilt support which is standard with this matt blue painted case.




Height Length Depth Code 120mm 120mm 120mm 284mm 224mm 284mm 138mm 138mm 188mm 00/3009-00 00/3009-10 00/3009-20 £6·40 £5·61 £7·07 incl. feet tilt, VAT and P & P. Less for quantity

CONTIL handles

(1) No. 265 Anodised aluminium centre bar. Black plastic brackets with moulded-in core. 75mm @ 97p. 5 more sizes up to 154mm. (2) No. 281.1

lon 112mm, Load 50 Kg. @ 45p Nylon 112m (3) No. 277

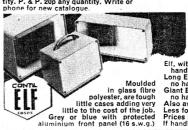(3) No. 277
Ali, ground, polished, anodised.
88mm @ 94p, 120mm @ £1-95.
(4) No. 288
Satin ali. 57-5mm @ 94p, 102mm @
£1-91, 145-5mm @ £1-17.
(5/5) No. 250
Black nylon Very comfortable. 75mm
@ 29p, 110mm. @ 41p, 155mm. @ 67p.
Prices include VAT. Less for quantity. P. & P. 20p any quantity. Write or phone for new catalogue.



Elf, with handle 6"×4"×4" £1-93 £1-76 Long Elf, no handle 9"×4"×3" £1-98 £1-93 Glant Elf, no handle 8"×5½"×5" £3-19 £3-08 Also available less panels. Less for quantities. P. & P. and VAT. If handle not available, price less 9p. 1 off 5 off

Brightlife neons,



10

illustrated are PC/A or C, PC/F, PC/D, PC/G or I, PP/A or B, Q & S, are brighter and give average of 25,000 hrs. life. The 0.5" dia. are red or white, the 0.375" are red, amber or white; these have 3 cap shapes and all may be supplied for 115, 240V. or the PP neons in 110, 240 and 440V.

with 6" or 30" leads. Send for details in new catalogue.

The design of these cases permits the instrument to be built or serviced within their panels. 48 external shapes. Low cost. Blue PVC/Steel with white P.V.C. coated aluminium panels.

Prices correct to 30th April 1974 WEST HYDE (M)

WEST HYDE DEVELOPMENTS LTD., RYEFIELD CRES., NORTHWOOD HILLS, NORTHWOOD, MIDDX. HA6 1NN.
Tel: Northwood 24941 or 26732 Telex: 923231

Project 80

the slimmest, most elegant hi-fi modules ever made

Living with hi-fi takes on new meaning with Project 80 modules. They can be assembled virtually anywhere, creating opportunities to install systems hitherto only dreamed about and never before made practical. Quality and reliability are everything you could wish for. Units are mounted by 6BA bolts at rear passing through drilled holes, cases are in higher with white embellishment.



Stereo 80 pre-amplifier and control unit

Each channel has independent tone and volume slider controls enabling exceptionally good environmental matching to be obtained. A virtual earth input stage forms part of the up-dated circuitry which includes generous overload margins. Clear instructions with template are supplied.

R.R.P. £11.95 $^{+£1\cdot19}_{-V,A,T}$



 $\begin{array}{l} \textbf{Size} - 260 \times 50 \times 20 \text{mm} \ (10\frac{1}{4} \times 2 \times \frac{3}{4} \text{ ins}) \\ \textbf{Inputs} - \textbf{Mag. P.U. 3mV RIAA corrected;} \\ \textbf{Ceramic P.U.,Radio,Tape} \\ \textbf{S/N ratio} - 60 \text{db} \end{array}$

Frequency range – 10Hz to 25KHz + 3dB Power requirements – 20 to 35 volts Outputs – 100mV + AB monitoring for tape Controls – Press button for tape, radio and P.U. Sliders for Volume, Bass and Treble.

Project 80 FM tuner and stereo decoder

FM Tuner
Size – 85 × 50 × 20mm
Tuning range – 87.5 to 108 MHz
Detector – 1.C. balanced
coincidence.
AFC – Switchable
One 26 transistor I.C.
Twin dual varicap tuning

Distortion 0.2% at 1 KHz for 30% modulation 4 pole ceramic filter in I.F. section Sensitivity – 4 microvolts for

30dB quieting
Output – 300mV for 75 KH
deviation





New circuitry

Decoder— With gallium arsenide tuning beacon and 19-transistor I.C.

Size $-47 \times 50 \times 20$ mm

FM tuner £11.95 +£1-19 V.A.T.

Decoder £7.45 +0.45p R.R.P. £7.45

Project 80 active filter unit



 $\label{eq:Size-108} \begin{array}{l} Size-108\times50\times20mm~(4\frac{1}{4}\times2\times\frac{3}{4}ins)\\ Voltage~gain-minus~0·2dB\\ Frequency~response-36Hz~to~22KHz,\\ controls~minimum\\ Distortion-at~1KHz-0·03\%~using~30V \end{array}$

HF cut off (scratch) – 22KHz to 5.5KHz,

L.F. cut off (rumble) -28dB at 20Hz, 9dB/oct. slope

R.R.P. £6.95 +0.69p V.A.T.

Z.40 & Z.60 power amplifiers

Z.40 Size – 55 × 80 × 20mm

Output – 15W RMS continuous 8 Ω (35V). Frequency response – 10Hz – 100KHz ±1dB Signal to noise ratio – 64dB Distortion – less than 0·1% at 10W into 8 Ω Power requirements – 12-35 volts

Input sensitivity - 100mV

R.R.P. £5.45 +0.54p



Z.60 Size $-55 \times 98 \times 20$ mm Input sensitivity - 100-250mV Output -25W RMS 8 Ω (45V). Distortion - typically 0-03%

Frequency response –
10Hz to more than
200KHz ±1dB
S/N ratio –
better than 70dB

R.R.P. £6.95 +0.69p

Sinclair power supply units

PZ.8

The worlds most advanced unit in its class. It is a stabilised unit. Reentrant current limiting makes damage from overload or even direct shorting impossible, a principle never before incorporated in a commercially available constructor module. Normal working voltage (adjustable) 45V.

R.R.P. £7-98 +0-79p V.A.T. Without mains transformer PZ.5 30V unstabilised R.R.P. £4-98 +0-49p V.A.T. PZ.6 35V stabilised


R.R.P. £7.98 +0.79p V.A.T.

Guarantee


If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair appointed Stockists also offer this guarantee.

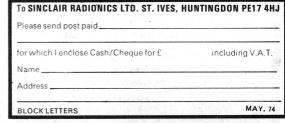Should any defect arise in normal use, we will service it without charge. For damage arising from mis-use a small charge (typically $£1\cdot00$) will be made.





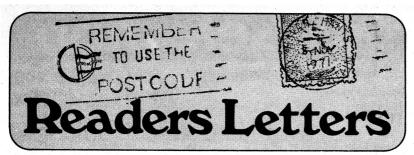R.O. London Road, St. Ives, Huntingdon, PE174HJ Phone St. Ives (0480) 64311 Reg. No. 699483 England




F.E.T. Connections

With reference to your January '74 EVERYDAY ELECTRONICS Fetset I must point out that I have just spent two hours trying to sort out why the diagram given for the field effect transistor differs from the actual component I received.

As a beginner in this field perhaps you may be able to help me know the difference between the three connections of any transistor. I hope you can find time to explain.

J. Waterhouse, Lancs.

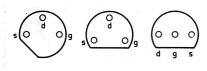Various transistors have different leadout configurations and the only way to find these is to consult the published data. Some transistors are made with more than one leadout configuration and usually a suffix letter is added to the number to denote the different construction. Three different connections for the f.e.t. are shown below.



Malaysian Praise

I have been a regular reader of your fabulous magazine since I started reading it in January '73. I must say that it is both instructive and educational.

My enthusiasm in electronics grew with the regular reading of your magazine and I am sure many of my fellow Malaysian readers are finding your mag. just as interesting.

I have built some of your projects e.g. the General Purpose Amplifier, Egg Timer, Waa Waa unit etc, and they all worked wonderfully. My compliments to you and your staff!

Poon Chee Seng, Malaysia

Reactance

I am a regular reader of EVERY-DAY ELECTRONICS. There has been a slight error in the print of your April issue.

It is in the article *Demo Circuits* by Mike Hughes. The equation for inductive reactance is $X_L = 2\pi f L$ and that of capacitive

reactance is $X_C = \frac{1}{2\pi f C}$ but instead

you had the equation for capactive reactance below inductive reactance and that for inductive reactance below capacitive reactance.

This, I think is a bit misleading for beginners, as your magazine is primarily intended for beginners in electronics.

To conclude I would like to say that it is one of the most interesting informative magazines that I have come across. I appreciate the wonderful service and knowledge we derive from it.

Y. Bayat, London.

Somehow the two equations have been transposed. The equations are correct but appear under the wrong headings. We are sorry about this.

Electronics Club

I thought I would write and tell you about our school electronics club. I am in the third year at Kirkcaldy High School.

In the senior school there is an electronics club which meets every Monday, Tuesday and Thursday. The club supply us with resistors, capacitors, solder, soldering irons, p.c. board etc., for our projects. We have to pay for some components such as semiconductors, transformers and IC's which the club has not got in stock.

We read your magazine and enjoy building the projects you print, so we hope you will keep us supplied.

G. Wilson, Fife.

We will certainly keep the supply of constructional projects flowing—there are four in this issue.

What do you know?

CAPACITORS

- Calculate the total value of the following capacitors wired in series:—0·1μF, 0·02μF and 0·47μF.
- 2. Calculate the total value of the following capacitors wired in parallel: -0.001 µF, 0.05 µF and 0.0047 µF.
- 3. You have a "flat" type capacitor with coloured bands around it. The colours are brown, black, orange, black, red, this is reading from the top (away from the leads) to bottom. State the value of the capacitor, its tolerance and voltage.
- 4. Is it necessary to always use an exact value electrolytic e.g. if $8\mu F$ is quoted could a $10\mu F$ normally be used and if so why?

ANSWERS

4. Most electrolytic capacitors have a tolerance of -20% + 100%. Therefore the circuit must be able to cope with a large range of values and it is normally permissible to use a capacitor of slightly higher value.

 $C_t = \frac{1}{62 \cdot 13} = 0.016 \mu F$ 2. $C_t = 0.001 + 0.05 + 0.0047 = 0.0657 \mu F$.
3. The value is 10,000pF \pm 20% at 250V.

$$\frac{C^{1}}{1} = \frac{0 \cdot 1}{1} + \frac{0 \cdot 05}{1} + \frac{0 \cdot 71}{1} nE$$

ne largest selection

EX COMPUTER BOARDS

Packed with transistors, diodes, capacitors and resistors—COMPONENT VALUE \$1.50. 3 for ONLY 55p + p & p 30p

SPECIAL ONE. As above PLUS Power Transistors ONLY 55p each + p & p 15p STABILISED POWER MODULES Complete with circuit diagram 99p each + p & p 15p

PAXOLINE BOARDS 7½ × 9" approx. 4 for 30p + p & p 20p.

FIBRE-GLASS PRINTED **CIRCUIT BOARDS** 161 × 4" approx. 2 for 55p

DECON-DALO 33PC Marker Etch resistant printed circuit marker pen 90p each

VEROBOARDS

Packs containing approx., 50sq. ins. various sizes, all ·1 matric 55p

REPANCO CHOKES & COILS

RF Chokes CH1. 2-5mH 25p CH2. 5-0i CH3. 7-5mH 25p CH4. 10n CH5. 1-5mH 25p CH2. 5.0mH 25p CH4. 10mH 25r

COILS DRX1 Crystal set 31p DRR2 Dual range 45p

COIL FORMERS & CORES

NORMAN 1" Cores & Formers 7p 1" Cores & Formers 8p

SWITCHES

DP/DT Toggle 25p SP/ST Toggle 18p

FUSES

14" and 20mm. 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A QUICK-BLOW 4p ea. ANTI-SURGE 5p ea.

EARPHONES

Crystal 2.5mm plug 33p Crystal 3.5mm plug 33p 8 ohms 2.5mm plug 22p 8 ohms 3.5mm plug 22p

DYNAMIC MICROPHONES

B1223. 200 ohms plus on/off switch and 2.5mm and 3.5mm plugs £1.60

3-WAY STEREO HEAD-PHONE JUNCTION BOX H1012

2-WAY CROSSOVER **NETWORK**

K4007. 80 ohms Imp. Insertion loss 3dB £1.21

CAR STEREO SPEAKERS (Angled) £3.85 per pair.

BI-PAK

CATALOGUE AND LISTS Send S.A.E. and 10p.

INSTRUMENT CASES



5½'

90p £1.20

VISIT OUR COMPONENT SHOP

ALUMINIUM BOXES

BA1	51"	×	2‡"	×	11"	42
BA2	4"	×	4"	×	11"	41
BA3	4"	×	2‡″ 4″	×	14"	41
BA4	51"	×	4"	×	11"	47
BA5	4"	×	21"	×	2"	41
BA6	3"	×	2"	×	- 1"	34
BA7	7"	×	5"	×	21"	66
BA8	8"	×	6"	×	3″	84
BA9	6"	×	4"	×	2"	54

BIB HI-FI ACCESSORIES

De Luxe Groov-Kleen Model 42 £1 ·84

Chrome Finish Model 60 £1 50

SOCKETS

PS 39

PS 40

PS 41

PS 42

PS 44

PS 45 PS 46

PS 47

Ref. 36A. Record/Stylus Cleaning Kit 28p Ref. 43. Record Care Kit £2:35 Ref. 31. Cassette Head Cleaner 54n Ref. 32. Tape editing Kit £1.54

Model 9. Wire Stripper/Cutter 83p

Ref. P. Hi-Fi Cleaner 31p Ref. 32A. Stylus Balance £1.36 Ref. J. Tape Head Cleaning Kit 51p Ref. 34. Cassette Case £1.27 Ref. 56. Hi-Fi Stereo Hints & Tips 32p

PLUGS AND SOCKETS

Jack 2.5mm Switched

Jack 3.5mm Switched

Jack Stereo Switched

Jack 1" Switched

Phono Single

Phono Double

Co-Axial Surface Co-Axial Flush

0.06

0.10

0.10

0.09

0.10

0.17

0.26

0.06

0.10

0.09

PS 35 DIN 2 Pin (Speaker)

PS 36 DIN 3 Pin

PS 37 DIN 5 Pin 1809

PS 38 DIN 5 Pin 240°

ANTEX SOLDERING IRONS

X25. 25 watt £1.93
CCN 240. 15 watt £2·15
Model G. 18 watt £2.15
SK2. Soldering Kit £2.86
STANDS: SŢ1 £1.21. ST2 77p
SOLDER: 18SWG Multicore 7oz 82p
228WG 7oz 82p. 188WG 22ft 28p
22SWG Tube 22p

ANTEX BITS and ELEMENTS

Bits No.	
102 For model CN240 3/	32" 38p
104 For model CN240 3/1	.6" 38p
1100 For model CCN240 3	/32" 38p
1101 For model CCN240	3/8" 38p
1102 For model CCN240	." 38p
1020 For model G240 3/3	2" 38p
1021 For model G240 1/8	″ 38p
1022 For model G240 3/1	6" 38p
50 For model X25 3/32"	38p
51 For model X25 1/8"	38p
52 For model X25 3/16	38p
ELEMENTS	
ECN 240 £1.16 ECC	N 240 £1 ·32

ANTEX HEAT SINKS 10p

EG 940 41.16

V.A.T. included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders—please add extra for postage.

EX 25 £1.16

NEW COMPONENT PAK BARGAINS

Paci No.	Qty.	Description	Price
C1		-	prox. 0.55
C2	200	Capacitors mixed values appropriate count by weight	prox. 0.55
C3	50	Precision Resistors 1%, mixed values	$^{2\%}_{ extbf{0.55}}$
C4	75	th W Resistors mixed preferr values	ed 0.55
C5	5	Pieces assorted Ferrite Rods	0.55
C6	2	Tuning Gangs, MW/LW VHF	0.55
C7	1	Pack Wire 50 metres associours	rted 0.55
C 8	10	Reed Switches	0.55
C 9	3	Micro Switches	0.55
C10	15	Assorted Pots & Pre-Sets	0.55
C11	5	Jack Sockets 3 × 3.5m 2 × Standard Switch Type	0.55
C12	40	Paper Condensers preferred types mixed values	0.55
C13	20	Electrolytics Trans. types	0.55
C14	1	Pack assorted Hardware— Nuts/Bolts, Grommets etc.	0.55
C15	4	Mains Slide Switches	0.55
C16	20	Assorted Tag strips & Panels	0.55
C17	10	Assorted Control Knobs	0.55
C18	4	Rotary Wave Change Switches	0.55
C19	3	Relays 6-24V Operating	0.55
C20	4	Sheets Copper Laminate approx. 10" × 7"	0.55

	INLI	NE SOCKETS	
ı	PS 21	D.I.N. 2 Pin (Speaker)	0.13
	PS 22	D.I.N. 3 Pin	0.17
ı	PS 23	D.I.N. 5 Pin 180°	0.17
	PS 24	D.I.N. 5 Pin 240°	0.17
	PS 25	Jack 2.5mm Plastic	0.10
	PS 26	Jack 3.5mm Plastic	0.12
	PS 27	Jack †" Plastic	0.24
ı	PS 28	Jack 1" Screened	0.28
	PS 29	Jack Stereo Plastic	0.22
ı	PS 30	Jack Stereo Screened	0.32
ı	PS 31	Phono Screened	0.14
ı	PS 32	Car Aerial	0.15
	PS 33	Co-Axial	0.17

PLUGS

PS 1	D.I.N. 2 Pin (Speaker)	0.11
PS 2	D.I.N. 3 Pin	0.12
PS 3	D.I.N. 4 Pin	0.15
PS · 4	D.I.N. 5 Pin 180°	0.14
PS 5	D.I.N. 5 Pin 240°	0.15
PS 6	D.I.N. 6 Pin	0.15
PS 7	S.I.N. 7 Pin	0.15
PS 8	Jack 2.5mm Screened	0.10
PS 9	Jack 3.5mm Plastic	0.09
PS 10	Jack 3.5mm Screened	0.12
PS 11	Jack ‡" Plastic	0.13
PS 12	Jack 1" Screened	0.18
PS 13	Jack Stereo Screened	0.29
PS 14	Phono	0.08
PS 15	Car Aerial	0.15
PS 16	Co-Axial	0.10

C	٩B	LES	
CP	1	Single Lapped Screen	0.06
CP	2	Twin Common Screen	0.08
CP	3	Stereo Screened	0.08
CP	4	Four Core Common Screen	0.28
CP	5	Four Core Individually Screened	0.30
CP	6	Microphone Fully Braided Cable	0.10
CP	7	Three Core Mains Cable	0.07
CP	8	Twin Oval Mains Cable	0.06
CP	9	Speaker Cable	0.04
CP	10	Low Loss Co-Axial	0.10
_	_	DON	

CARBON

Log ar	nd Lin	
4·7K,	10K, 22K, 47K, 100K, 220K,	470K
1M, 21	M	
VC 1	Single less Switch	0.1
VC 2	Single D.P. Switch	0.2
VC 3	Tandem Less Switch	0.4
VC 4	1K Lin Less Switch	0.1
VC 5	100K Log anti-Log	0.4

HORIZONTAL CARBON PRESETS.

18 BALDOCK ST., WARE, Herts. (A10)

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Tel. 61593

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Tel. 61593

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Tel. 61593

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Tel. 61593

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping until 7 Fri.

Open Mon.—Thurs. 9.15–6 p.m. Sat. 9.15–5.30. Late Night Shopping u

WORLD SCOOP

IUMBO SEMICONDUCTOR PACK

Transistors - Germ. and Silicon Rectifiers -Diodes - Triacs - Thyristors - I.C's and Zeners ALL NEW AND CODED.

APPROX 100 PIECES

Offering the amateur a fantastic bargain Pak and an enormous saving—identification and data sheet in every Pak.

Only £2 p. & p. 20p

EX-COMPUTER BOARDS BY THE BOXFULL!!

20 Boards packed with Semiconductors and other Electronic Components. Each board approx. size 8" x 7". All known type no's and easily recognisable.

FANTASTIC VALUE AT £2.20 per BOX p. & p. 52p

SPECIAL PURCHASE

2N3055. Silicon Power Transistors NPN. Famous manufacturers out-of-spec devices free from open and short defects—every one able! 115w. T03. Metal Case.

OUR SPECIAL PRICE 8 for £1

LOW COST	CAPACITORS
·01UF 400v. 500UF 50v. Elect.	3p. eacl

RECORD STORAGE/ **CARRY CASES**

7" EP. 18%" x 7" x 8". (50 records) \$2.10 12" LP. 13%" x 7%" x 12%". (50 records) \$2.95

CASSETTE CASES Holds 12. 10" x 33" x 5". Lock & Handle.

8-TRACK CARTRIDGE CASES Holds 14. 13" x 5" x 6". Lock & Handle

£1.95 Holds 24. 13%" x 8" x 5%". Lock & Handle COLOURS: Red, Black and Tan—Please state preference.

REPANCO TRANSFORMERS

240v. Primary. Secondary voltages available from selected tappings 4v, 7v, 8v, 10v, 14v, 15v, 17v, 19v, 21v, 25v, 31v, 33v, 40, 50 and 25v-0-25v.

Type MT50/1 MT50/1 MT50/2	Amps. 1 2	Price £1.93 £2.42 £3.30	P & P 80p 35p 40p

CARTRIDGES

ACOS GP91-1SC. 200mV at 1.2cms/s	ec £1·16
ACOS GP93-1. 280mV at 1cm/sec	£1·65
ACOS GP96-1. 100mV at 1cm/sec	£2·65
TTC J-2005. Crystal/Hi Output	95p
TTC J-20 10C Crystal/Hi Output Con	npatible £1·10
TTC J-200 CS Stereo/Hi Output	£1-60
TTC J-2105 Ceramis/Med. Output	£1-64

CARBON FILM RESISTORS

The E12 Range of Carbon Film Resistors, 1/8th watt available in PAKS of 50 pieces, assorted into the following groups:— R1 50 Mixed 100 ohms-820 ohms 40p R2 50 Mixed 1K ohms-8-2K ohms 40p R3 50 Mixed 10K ohms-82K ohms 40p R4 50 Mixed 100K ohms-1 Meg. ohms 40p THESE ARE UNBEATABLE PRICES-LESS THAN 1p EACH INCL. V.A.T.

BI-PAK SUPERIOR QUALITY LOW - NOISE CASSETTES

-the lowest prices!

BI-PAK QUALITY COMES TO AUDIO!

AL10/AL20/AL30 AUDIO AMPLIFIER MODULES



The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S.

The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	Po = 3 WATTS f=1KHz	0.25%
LOAD IMPEDANCE		8 – 16 Ω
INPUT IMPEDANCE	f=1KHz	100 kΩ
FREQUENCY RESPONSE Œ 3dB	Po=2 WATTS	50 Hz - 25KH2
SENSITIVITY for RATED O/P	Vs=25V. Rl=8Ω f=1KHz	75mV. RMS
DIMENSIONS	_	3" × 21" × 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL80
Maximum Supply Voltage	25	30	30
Power output for 2% T.H.D. $(RL = 8\Omega f = 1 \text{ KHz})$	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.

AUDIO AMPLIFIER

	OLLO		
L 10.	3 watts	RMS	£2·19
L 20.	5 watts	RMS	£2.59
L 30.	10 watts	RMS	£3.01
	L 10. L 20.	L 20. 5 watts	L 10. 3 watts RMS L 20. 5 watts RMS

POWER SUPPLIES

PS 12. (Use with AL10 & AL20) SPM 80. (Use with also AL30 & AL50) 88p FRONT PANELS SP 12 with Knobs \$1.10

PRE-AMPLIFIERS

PA 12. (Use with AL10 & AL20) \$4.35 PA 100. (Use with AL30 & AL50) \$13.15

TRANSFORMERS

T461 (Use with AL10) £1.38 P & P 15p T538 (Use with AL20) £1.93 P & P 15p BMT80 (Use with AL30 & AL50) £2:15

PA 12. PRE-AMPLIFIER SPECIFICATION

The PA 12 pre-amplifier has been designed to match into match into most budget stereo systems. It is compatible with the 20Hz-50KHz(-3dB) AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with *Ceramic cartridges while the auxiliary input will suit most †Magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 152mm × 84mm × 35mm.

± 12dB at 60Hz
Treble control—
± 14dB at 14KHz
*Input 1. Impedance

*Input 1. Impedance
1 Meg. ohm
Sensitivity 300mV
†Input 2. Impedance
30 K ohms
Sensitivity 4mV

Look for our

SEMICONDUCTOR ADVERTISEMENTS in

Practical Wireless Wireless World Radio Constructor

ALL PRICES INCLUDE V.A.T.

The **STEREO 20**

The 'Stereo 20' amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm x 14 cm x 5.5 cm. This compact unit comes complete with on/off switch volume control, balance, bass and treble controls, Transformer, Power supply and Power amps. Attractively printed front panel and matching control knobs. The 'Stereo 20' has been designed to fit into most turntable plinths without interfering with the mechanism or, alternatively, into a separate cabinet. Output power 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. res. 25Hz-25kHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion. Bass control ± 12dB at 60Hz typically 0.25% at 1 watt. Treble con. ± 14dB at 14kHz.



NOW WE GIVE YOU 50w PEAK (25w R.M.S.) PLUS THERMAL PROTECTION! The NEW AL60 Hi-Fi Audio Amplifier FOR ONLY £3.95

- Max Heat Sink temp. 90°c. Frequency Response 20Hz to 100KHz
- 0·1% Distortion
 Distortion better than 1% at
- Supply voltage 10-35 volts
- Thermal Feedback
- Latest Design Improvements
- Load-3, 4, 8 or 16 ohms
- Signal to noise ratio 80dB
- Overall size 63mm imes 105mm imes13mm

Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.



STABILISED POWER **MODULE SPM80**

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1-5 amps at 35 volts. Size: 65mm × 105mm × 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disco Systems, Public Address Intercom Units, etc. Handbook available 10p PRICE £3.25

TRANSFORMER BMT80 £2.15 p. & p. 28p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates

Designed for use with the ALSO power ampliner system, this quanty made unit incorporates no less than eight sillicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.

Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.



SPECIFICATION

Scratch (Low Pass) Signal/Noise Ratio Input overload Supply Dimensions

8KHz better than -65dB

better than
+ 26dB
+ 35 volts at 20mA
+ 35 volts at 20mA
292mm × 82mm × 35mm
ONLY £13 · 15

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25.30 FREE p. & p.

Giro No. 388-7006 Please send all orders direct to warshouse and despatch department

P.O. BOX 6, WARE · HERTS
Postage and packing add 11p. Overseas add extra for airmail.

Minimum order 55p. Cash with order please. Guaranteed Satisfaction or Money Back



DOUBLE-SIDED WALL CHART

'How to build and use the P.E. Sound Bender'

Centred around a simple constructed "audio modulator" unit, the P.E. Sound Bender is not just a single sound effects unit, but your key to a host of exciting with-it sounds.

Just feed a music or speech signal to one input and a control signal to the other and you can have a tremolo, a frequency doubler, a ring modulator, or a voice-operated fader.

Also in the MAY ISSUE . . .

FIRST STEPS IN CIRCUIT DESIGN - 2

The second article in this new series for beginners deals with the "parameter jungle", input impedance and voltage gain equations.

PLUS

An Improved BATTERY CHARGER

This "fail-safe" design includes short-circuit, reverse-polarity, and overcharge protection – without adding drastically to the costs.

ELECTRONIC FLASH METER


Remove the chance element from flash photography with an accurate and simple-to-operate instrument which will cope with all normal and many abnormal exposure conditions for both black-and-white and colour photography.

ELECTRONICS

MAY ISSUE ON SALE MID APRIL* 25p

^{*} subject to the current national industrial situation at the time of going to press

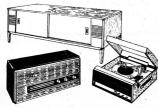The items below are from the March Supplement to our 1974 Catalogue. You can receive this Catalogue and the next 12 supplements by sending 66p.



Stereo Radiogram Cabinet, Long, Lon Feak veneered with sliding front and tapered eas. Speaker spaces each end. Size approx ftt. 2" × 15" × 15". Probably cost over £20 to make. Our Price £8:10 each. We can arrange lelivery within 200 miles if you can order

Bush Record Player. Bush Ref. No. SRP 64. Separate bass and treble controls help give thismusually good sound quality. A suitable amplifier, speaker unit converts this to full stereo. Cabiner size 74" × 18" × 18" deep. Finished in charcoal crey leather cloth. Fully transistorised with 8" > 5" speaker. Controls bass, on/off, freble and volume. Socket stereo. Makers recommended price £27.73. Our Price £17.72. A saving of over CS. Post and insurance £2.

CS. Post and insurance £2. Erres Table Radio, Dutch made. Three waveband-L.M. & S.) Nice size (16½" × 8½" × 5") wooden cabinet with high gloss finish. 6" × 4" speaker zives better than average tone—these radios are very well made from good quality components ond should not be confused with Hong Kong makes. They recently retailed at £18 each and were well worth it. The ones we have are brand new and working but have failed final inspection because either they will work only on mains or only on batteries, It is unlikely that the fault i-ery much however and we are arranging for a circuit diagram. Price £8-64 plus £1 post and insurance.

Electric Welder, Big transformer in metal caswith carrying handle and control switch, output brough very heavy duty terminals. Output offs 1:9-4-25 volts max, 117 amps.—normal nains input socket for optional foot switch 519-50 plus 22 carriage up to 200 miles. A further c! for each 100 miles extra.

24v 3 amp Mains Transformer. Upright mounting with fixing clamps, standard primary 240/200/195/160—23.50 plus 30p post and service.

Mains Transformer. (6.5v-0-6.5v at 500 mA and tv at 1 amp). Normal tapped primary. Upright mounting with fixing lugs. £1-00.

Mains Transformer, (18v-37v-39v-41v at 2 amper this would function at 18v-0-18v). Primary apped 110, 115, 127, 200, 220 and 240v selected by labelled plug. Primary screen and multi-apped. Upright mounting with fixing lugs 22v.

Midget Two Gangs. Tuning condenser as fitted to nany Japanese and Hong Kong radios—probabls 300pf each section with 4" spindle with terminal-less trimmers. Price 38p. With trimmers 50p

Ferrite Rods for aeriais, etc. The following type-tre in stock Dia. 2". 4" long 15p, 5" long 18p, Dia. 5/16", 5" long 20p, 6" long 25p, 8" long 30p, Dia. 3/8", 4" long 20p, 5" long 25p, 6" long 30p, 5" long 40p; Dia. 4", 6" long 35p; Ferrite Slal-3" long 4 2" x 1/8th"-20p.

Photo Resistor. Mullard type. This drops it resistance from approx. 250Kohms in dark to-mly approx. 200 ohms in bright light but it i-mly quite small, in fact less than 4" square with eads coming out of corners on one side. Price 22p

0-8 Ammeter, 2" square, full vision face for flust mounting—moving iron, ideal for charger 75p each.

MAINS TRANSISTOR POWER

Pack
Pesigned to operate transistor sets and amplifierdjustable output 6v., 9v., 12 volts for up to500mA (class B working). Takes the place of any
of the following batteries: PP1, PP3, PP4, PP6,
PP7, PP9 and others. Kit comprises: maintransformer rectifier, smoothing and load resistor,
madanasa and instructions. Real snip at only and instructions. Real snip £1.10, plus 20p postage.

TERMS:- Add 10% V.A.T. Send postage where quoted—other items post free if order for these items is £6.00, otherwise add 20p.

J.BULL(ELECTRICAL)LTD.

(Dept.EE) 7 Park Street, Croydon CRO 1YD. Callers to: 102/103 Tamworth Rd. Croydon

BEAT THE BUDGET AT ZIGGY'S 200

Multimeter AC-DC Type U-437 10kΩ/V 2·5% precision A—d.c. 0·1-1A—5 ranges V—d.c./a.c. 2·5 to 1,000V—

V—d.c./a.c. 6 f ranges. Ohms—100 to IMΩ—4 ranges. Frequency: 45-40kHz —2 ranges.

—2 ranges.
TAUT SUSPENSIONS
MOVEMENT
Complete with steel

case. ONLY £4-95 inc. VAT and postage

and postage.

SPECS. MULTIMETER
U4324. Sensitivity 20,000 OPV
d.c. Usually high current ranges
3 amps a.c./d.c. Voltages
AC3 to 900V d.c. 0-6 to 1200V.
Resistance 500 ohms—20-2002,000k D. Transmission level
-10 to +12dB. This high
quality instrument has diode
protection. Complete with
test leads, batteries, etc.
Price only £8 incl. VAT and
postage. postage.

ENAMELLED COPPER WIRE S.W.G. 16, 18, 20, 22, 24, 26, 202 reels, 26p. 28, 30, 32, 34, 36, 38, 40, 20z reels, 36p. Postage I-5, 10p, 6 plus, 15p.

Postage 1–5, 10p, 6 plus, 15p.

ANTEX SOLDERING IRON BITS
Chrome type for 15 watt models.
§in. Ain, §in. Ail 26p each. Postage 5p
MAINS TRANSFORMER
Eagle M76, 6–0–6, 100M/A, 95p plus 16p, P. & P.
M713, 12–0–12, 50M/A, 95p plus 10p, P. & P.
Eagle Type M728, 6–0–6, 250MA | Ail £1.43
M7150 12–0–12, 150M/A | P. & P.
R/S 13V 0.57 mp C.T. | £1.40
M7160 24–0–24, 100M/A | P. & P.
R/S 13V 0.53 mp C.T. | £1.40
Lamp £1.20 P. & P. 12p
1 Amp £1.20 P. & P. 12p
2 Amp £1.25 P. & P. 12p
4 Amp £1.95 P. & P. 20p
6 Amp £2.62 P. & P. 35p
POTENTIOMETERS

6 Amp £2-62 P. & P. 35p
POTENTIO METERS
log or lin less switch (and I kΩ lin) I-5 I2p
6-10 IIp each. I plus I0p each.
5kΩ 50kΩ 10kΩ 10kΩ
25kΩ 250kΩ 2mΩ
10g or lin with switch I-5 24p. 6-10 23p. II
plus 20p.
dual less switch I-5 39p. 5-10 37p. 10 plus
35p. Any mix for Quantity Prices. P. & P. 7p.

35p. Any mix for Quantity Prices. P. & P. 7p. QUALITY MONO SLIDER POTS FROM JAPAN RRS 10kΩ. RR6 100kΩ. RR7 500kΩ. Track Length: 30mm. Fixing Centre: 50mm. 34p each, P. & P. 5p. HS16 Heavy gauge tapered copper jaw heat sink clip on to the leads of heat sensitive components to ensure that they are not damaged when soldering or de-soldering. 50p each. P. & P. 5p.

MINI LOUDSPEAKERS 2½ in 8Ω 50p. 5p. P. & P. TP26G. 70mm 80 ohm replacement transistor radio loudspeaker. 70p. P. & P. 5p

Tadio Ioudspeaker. 70p. P. & P. 5p

TURNTABLE SERVICES

Headshells

Garrard SP25 Mk. I & II. Type M7

S.M.E. S2 Shell

G.77

Thorens TP50 for TD150

G.330

Thorens TP50 for TD160

G.330

Goldring PH7 for GLBS

Head Slides

Postage 5p per item

Garrard C1 for SL75, etc.

Garrard C2 for SP25 Mk III, SL95, etc.

B.S.R. for MP60, 310, 510, 610

Jockey Wheels

Garrard SP25 Type, etc.

McDonald MP60, etc.

Sop

STA/HC LP/LP 95p

NSW210 210 pieces, assorted nuts, screws and washers.

S5p. P. & P. 5p.

TRANSISTORS
BC107, 108, 109, all 9p each. Any six 50p
P. & P. 4p.

P. & P. 4p.
EAGLE LT700 TRANSFORMER
40p P. & P. 5p.
NEW MULLARD DATA BOOK 1973/74
30p. P. & P. 5p.

30p. P. & P. Dp.

FOR SPEEDY DELIVERY OF THESE
MINT CONDITION COMPONENTS
PLEASE SEND C.W.O. to ZIGGY'S 2001
ELECTRONICS CO. LTD., DEPT. E.E.,
34 MABELEY STREET, LONDON, E.9.

All prices include VAT, please add postage where indicated.

SINCLAIR CALCULATORS

Cambridge Kit £23-95 (£2-80) Cambridge Assembled £25-95 (£3-00) Executive Memory £39-95 (£4-40) New Sinclair Scientific £43-95 (£4-80)

FERRANTI ZN414

IC radio chip with data £1.20 (23p). Also available kit of other parts to complete a radio £2.39 (40p). Send sae for free leaflet.

SINCLAIR PROJECT 80

AFU £5·95 (80p) Z40 £4·65 (67p) Z60 £5·95 (80p) Q16 £6·70 (87p) PZ5 £4·28 (55p) PZ6 £6·95 (92p) PZ8 £6·95 (92p)



Decoder £6.45 (85p) Trans for PZ8 £2.95 (50p)
Tuner £9.95 (£1.20) Stereo 80 £9.95 (£1.20) Send sae for free leaflet on new quadraphonic adapter for use with Project 80 £9.95 (£1.20)

SUPERIC 12

6W rms power with 44 page booklet and printed circuit £2·10 (43p)



SWANLEY IC TOMORROW

The world's most powerful IC amplifier. Similar o the IC12 but rated at 10W rms power. Supplied with data but no printed circuit £2⋅60 (47p). 20% discount on 10 + quantities.

DELUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1-55 (26p). Stereo model with balance control £3-50 (46p).

IC12 POWER KIT

Supplies 28V 0.5 Amps £2.47 (50p)

LOUDSPEAKERS FOR THE IC12 5" 8 ohm £1.10 (27p), 5" x 8" 8 ohm £1.55 (37p).

PREAMP KITS FOR THE IC12

Type 1 for magnetic pickups, mics and tuners. Mono model £1·30 (24p). Stereo model £2·30 (34p) Type 2 for ceramic or crystal pickups. Mono 60p (17p). Stereo £1·20 (23p).

SEND SAE FOR FREE LEAFLET ON KITS

FLIMINATOR BARGAIN

The most versatile battery eliminator ever offered. Switched output of 3, 4½, 6, 7½, 9 and 12V at 500 mA £3·95 (70p)



Other eliminators stocked: 50mA:-6V £1·50 (30p). 9V £1·50 (30p). $7\frac{1}{2}V$ cassette type £2·25 (30p). Double 6+6V £2·50 (35p). 9+9V £2·50 (35p).

500mA:—Higher current deluxe models. 6, $7\frac{1}{2}$ or 9V (state which) £2.85 (50p).

S-DECS AND T-DECS

S-DEC £1.98 (31p) T-DEC £3.63 (47p) μ-DEC A £3.99 (51p) μ-DEC B £6.99 (81p)



IC carriers:—
16 dil:—plain 81p (15p). With socket £1·77 (25p).
10 TO5:—plain 78p (15p). With socket £1·68 (24p). Experiment guides:—A £1·50 (26p), B £1·77 (29p), C 90p (15p), D £2·40 (35p). E £4·20 (53p).

ZIPPY CABINETS

ZIPPY CABINETS
Attractive plastic instrument cases in 4 sizes. 80 x 50 x 30 mm 60p (25p). 115 x 65 x 40 mm 87p (30p). 155 x 90 x 50 mm £1 · 20 (35p). 210 x 125 x 70 mm £1 · 20 (45p)

ECONOMICAL QUADRAPHONICS

Complete self contained matrix guadraphonic synthesizer in attractive cabinet. Just feed output of ordinary stereo hi-fi into it and hook up to speakers to obtain the latest experience in sound Send sae for free leaflet.

SWANLEY ELECTRONICS PO BOX 68, SWANLEY, KENT BR8 8TQ.

Please add the sum shown in brackets after the price to cover the cost of post and VAT. Official credit orders from schools etc. welcome. No VAT charged on overseas orders.

Everyday Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p. extra. Semi-display—£6·00 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Department, "EVERYDAY ELECTRONICS," I.P.C. Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD.

EDUCATIONAL

GUILDS EXAMINATIONS. CITY Make sure you succeed with an ICS home study course for C & G Electrical Installations, Telecommunications Installations, Telecommunications, Technicians and Radio Amateurs. Free details from:—International Correspondence Schools, Dept. 73IP, Intertext House, London SW8 4UJ.

COLOUR TV SERVICING. Make the most of the current boom. Learn the technique of servicing Colour & Mono TV sets through new home study courses, approved by leading manufacturers. Also radio and audio courses. Free details from:—International Correspondence Schools, Dept. 731F2, Intertext House London SW8 4UJ.

TECHNICAL TRAINING. Get the qualifications you need to succeed. Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering & Programming. Also self build radio kits. Free details from:— International Correspondence Schools, Dept. 731F3, Intertext House, London SW8 4UJ. SW8 411.1.

RECEIVERS and COMPONENTS

COMPONENTS GALORE. Pack of 500 mixed components manufacturers sur-plus plus once used. Pack includes Resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1+10pp. and p. c.w.o. to CALEDONIAN COMPONENTS, Strathore Road, Thornton,

TUNBRIDGE WELLS, components from Teleservice, 108 Camden Road, Tunbridge Wells, Kent. Telephone

7LB ASSORTED COMPONENTS £1-65 c.p. 2LB ASSORTED COMPUTER PANELS

ZLB ASSONTED COMPUTER PANELS
£1:65 c.p.
3 ASS. M.C. METERS 2"-3" £1:15 (25p)
SILICON DIODES 650V 1½A, 35p (5p).
COMPUTER PANELS 5-BC108, Diodes 4-55p
(10p). LARGE PANELS, average 40 transistors, loads of hi-stabs, etc. 85p (25p).
COPPER CLAD PAX. PANELS 5½" x 5½"
6-45p c.p.

6-45p c.p.
VALUPAKS—from 25 to 75p, Send 10p for lists of these and panels etc. Refund on purchase.
J.W.B. RADIO
2 Barnfield Crescent, Sale, Cheshire M33 1NL Postage in brackets
Mail order only

SPECIAL PACK of components, 25 resistors, 10 diodes, 20 capacitors, all tested and guaranteed. Also contains 20 transistors, untested manufacturers rejects. Send 50p to Felectronics, 6 The Grassing, Carlisle.

SERVICE SHEETS

SERVICE SHEETS for Televisions, Radios, Transistors, Record Players, Tape Recorders, etc., from 5p with free Fault-Finding Guide. Over 10,000 models available. S.A.E. enquiries. Catalogue 20p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 429066.

MISCELLANEOUS

BATTERY ELIMINATOR KITS. Our well-known Mini Mains Pack Kits now complete with drilled insulated base 32 x 55mm. Fits into space of most large transistor batteries. Easy wiring instructions. Safe, silent mains transformer, silicon rects, smoothing capacitor, all top grade. For any ONE of these voltages (state which): 3V, 300mA max.; 6V, 180mA; 9V, 120mA; 18V. 60mA. 1-50 VAT included. By mail only, UK post 5p. Amatronix Ltd., 396 Selsdon Rd., South Croydon, Surrey CR2 0DE. CR2 ODE. rey

DESOLDERING BRAID direct from manufacturers. Removes components from printed panels in seconds. Noncorrosive. Hang-up cards containing 5 feet. 40p V.A.T. paid. Postage 5p any quantity. Ashleys, 91 Vale Road, Ash Vale, Surrey.

RADIO & TELEVISION AERIAL BOOS RADIO & TELEVISION AERIAL BOOS-TERS \$2.95p, five television valves 45p. 50p bargain transistor packs, bargain £1 resistor and capacitor packs. UHF-VHF televisions £7.50, carr. £1.50p. S.A.E. for 3 leaflets. ELECTRONIC MAIL ORDER (BURY) LTD., Bridge Street, Ramsbottom, Bury, Lancs.

STYLI. Finest quality for most Crystal and Magnetic Cartridges: Double-Diamond, Diamond/Sapphire, Double-Sapphire, Sapphire, at lowest prices. Quick Service. FREE LIST sent for S.A.E. FELSTEAD ELECTRONICS (EE) LONGLEY LANE, GATLEY, CHEADLE, CHESHIRE SK8 4EE.

WIRE


H.C. Copper, P.V.C. Insulated 24 A.W.G. (0.2 m.m.2) in P.V.C. Colours Black, Yellow, Blue or White. Reels 80zs £0.95; 11b £1.80; 21bs £3.50; 41bs £6.75 including VAT and postage larger Reels available C.W.O.

H. A. WAINWRIGHT & CO. LTD., 9A Farncombe Street, Farncombe, Godalming, Surrey. Tel: Godalming 23545.



delighted.
V.G.S. INTERNATIONAL (SGE10)
Pickworth. Sleaford, Lincolnshire.

LOUDSPEAKERS

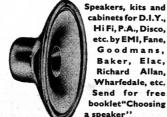

Wharfedale, etc. Send for free booklet"Choosing a speaker"

Goodmans.

Baker, Elac,

Richard Allan,

WILMSLOW AUDIO
Dept. H. Swan Works, Bank Square,
Wilmslow, Cheshire SK9 1HF
Tel. Wilmslow 29599

12 VOLT FLUORESCENT LIGHTS (As illustrated by Thorn A.E.I.)

Beat power cuts, be independent. Caravans, Tent, Emergency Lighting, etc. Works anywhere where 12V is available. Guaranteed for six months, READY TO USE at:-

£4 post inc. 12 ins 8watt

SALOP ELECTRONICS 23 Wyle Cop Shrewsbury, Shropshire.

Callers welcome for lists or Enquiries Large S.A.E.

Tel. Shrewsbury 53206

BEGINNERS, we exist for you. Instruction, components, constructional kits. Send S.A.E. to Electrolern, Lyburn Lodge, Nomansland, Wiltshire.

FIBRE OPTICS—OPTIKIT 103 contains 2 m. Crofon 1610, 64 Strand Light Conduit plus 5 metres each FP20, FP40, FP60 Plastic Monofibre (diameter 0·5, 1·0, 1·5 mm). Price £4·84 including booklet, pp., VAT. FIBRE OPTIC SUPPLIERS, (EE), P.O. Box 702, London W10 6SL.

2N5777 SILICON PHOTODARLING-2N5777 SILICON PHOTODARLING-TON AMPLIFIER sensitive light detector, much superior to CdS light cell. Price I off 55p, 5 of £2·53 inc. data, VAT, pp. FIBRE OPTIC SUPPLIERS, (EE), P.O. Box 702, London WI0 6SL.

RED LIGHT EMITTING DIODES MLED 500 in TO92 case, MV54 miniature (2 mm). Price (both types) 5 for £1·10 inc. data, VAT, pp. FIBRE OPTIC SUPPLIERS, (EE), P.O. Box 702, London WI0 6SL.

NEW PRODUCTS. Panel mounting holders for ORP12 L.D.Rs. in polished aluminium 25p. Control knobs 11/16 dia. in aluminium with colour coded ends 18p, state colour. Any turned part supplied. 7p for list. Post 10p. Electro-Mech Products, 7 Chantry Avenue Rideford. Devon. Avenue, Bideford, Devon.

71b BARGAIN PARCELS

Hundreds of new resistors, capacitors, pots, switches. Also crystals, computer panels & loads of odds & ends. Only £1.65 (40p)

VERSATILE POWER UNIT

Contains Mains Transformer, 2A Thermal Cut-Out and Bridge Rect. Will give 1-7-10:5V output with 2 extra capacitors (provided), Ideal for Nick-Cad Battery Charger, 5V TTL supply, Cassette or Radio, etc. Brand new with information 87p (20p).

3W TAPE AMPLIFIERS

Very sensitive 4 valve amplifier with tone & volume controls giving 3 watts into 3 ohms. Only £1.65 (40p); Also available in cabinet with 7 x 4* speaker and non-standard tape deck. Mains operated, fully tested. £3 (£1 up to 200 miles, £1.20 over) Suitable cassette £1 (30p). Spare head 30p.

FERRIC CHLORIDE

Anhydrous to mil-spec. 1lb 50p (20p) 3lb £1:20 (30p), 10lb £3:50 (60p). SURPLUS COMPONENTS: 500 asstd resistors £1 (20p); 300 capacitors all types £1 (30p); 25:10X crystals 75p (30p); 40 asstd. pols £1 (30p), VAT NOT INCLUDED—ADD 10%; TO TOTAL. Carr in brackets, small parts 4p. SAE List.

GREENWELD ELECTRONICS [EE1]

24 Goodhart Way, West Wickham, Kent, BR4 0ES. hops at 21 Deptford Broadway, SE8, el 01-692 2009 & 38 Lower Addiscombe Rd,

DON'T LOOK

unless you can resist the temptation to get these super

- ### Pocket-sized MAXI-VOLT Big finch Spark Generator (instant IS,000 volts!). Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz. (85g.) send £1⋅35 for your Maxi-Volt-could.
- Volt now!

 ★ Unique TRANSMITTER/RECEIVER Kic. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send
- to build. Get transmitting, Send 45-90 for yours now!

 ★ Psychedelic MINI-STROBE Kit. Take a pocket-sized lightning storm to Disco's and parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too.
 Send £2.20 now! (All prices include V.A.T., packing,

and postage.) Send remittance to:

BOFFIN PROJECTS, 4 CUNLIFFE ROAD, STONELEIGH, EWELL, SURREY

(Mail order U.K. only)
Or for more details, send 15p for lists, plus free design project sheet.

construction AIDS. Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards masters, negatives and boards, one-off or small numbers. Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warks.

INSTRUMENTAL

SUPER "FUZZ" UNIT KIT. CONNECTS BETWEEN GUITAR & AMPLIFIER. OPER-ATES FROM 9v BATTERY (not supplied). ALL COMPONENTS AND PRINTED CIRCUIT BOARD WITH FULL INSTRUCTIONS. KIT PRICE: £2.86 post paid.

CREATE "PHASE" EFFECT ON YOUR RECORDS, TAPES ETC., UNIQUE CIRCUITRY ENABLES YOU TO CREATE PHASE EFFECT AT THE TURN OF A KNOB. OPER-ATES FROM 9v BATTERY (not supplied) COMPLETE KIT OF COMPONENTS WITH PRINTED CIRCUIT BOARD & FULL INSTRUC-TIONS. KIT PRICE: £2-86 post paid.


MAIL ORDER ONLY.

S.A.E. ALL ENQUIRIES.

DABAR **ELECTRONIC PRODUCTS**

98a, LICHFIELD STREET. WALSALL, STAFFS. WS1 1UZ

Price ea

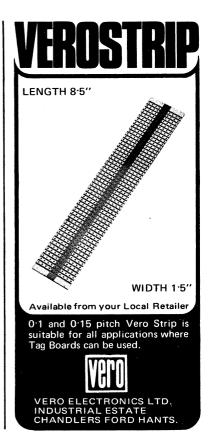



FROM

FAIRCHILD

			i i icc ca
μ Α 703	TO-78	RF-IF Amp	£0.94
μΑ706A	DIPP	2.5W Audio Amp	£2.14
μ Α706 Β	DIPP	5.0W Audio Amp	£2.39
μ Α720	DIP	AM Radio Cct	£1.20
μ Α732	DIP	FM Stereo Decoder	£1.14
μA739	DIP	Dual Low Noise Pre-Amp	£1.45
μ Α749	TO-78	Dual Audio Pre-Amp	£1.28
μA753	DIP	FM Gain Block	£1.19
CA3075	DIP	FM-IF Amp	£1.07

Complete circuit connection diagram and characteristics supplied free with each circuit type.

A FULL RANGE OF RADIO AND AUDIO INTEGRATED CIRCUITS GUARANTEED TO MANUFACTURER'S FULL SPECIFICATIONS.

Please send cash with order. Prices include VAT. P & P for U.K. 12p per order. Overseas add airmail charge.

Send this coupon and 4" x 9" stamped addressed envelope for comprehensive free price list
Please print
ADDRESS
ee .



89-91 Wardour St., London, W1V 3TF.

YATES ELECTRONICS (FLITWICK) LTD

DEPT. E.E., ELSTOW STORAGE DEPT. KEMPSTON HARDWICK, BEDFORD.

C.W.O. PLEASE. POST AND PACKING PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the components listed will be sent free on request. 10p stamp appreciated.

Callers Welcome Mon. to Sat. 9 a.m. 5 p.m.

PLEASE ADD 10% VAT

RESISTORS W lakra high stability carbon film—very low noise—capless construction. W Mullard CR25 carbon film—very small body size 7.5 x 2.5 mm. W 2% ELECTROSIL TR5. Values available E24 E12 E24 E12 E12 E12

DEVELOPMENT PACK 0.5 watt 5% lskra resistors 5 off each value $4.7\,\Omega$ to IM Ω . E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS Carbon track $5k\Omega$ to $2M\Omega$, log or linear (log $\frac{1}{2}W$, lin $\frac{1}{2}W$). Single, 12p. Dual gang (stereo), 40p. Single D.P. switch, 24p.

SKELETON PRESET POTENTIOMETERS Linear: 100, 250, 500 Ω and decades to $5M\,\Omega$. Horizontal or vertical P.C. mounting (0·1 matrix). Sub-miniature 0·1W, 5p each. Miniature 0·25W, 7p each.

TRANSISTORS									
AC107	15p	AFI26	20p	BF115	25p	OC42	12p	2N3707	12p
ACI26	12p	AF139	32p	BF173	20p	OC44	12p	2N3708	10p
ACI27	15p	AF178	32p	BF177	28p	OC45	12p	2N3709	Hp
ACI28	15p	AFI80	40p	BF178	32p	OC70	12p	2N3710	Hp
AC131	12p	AFI81	40p	BF179	32p	OC71	12p	2N3711	Hp
ACI32	12p	BC107	12p	BF180	32p	OC72	12p	2N3819	32p
AC176	15p	BC108	12p	BFI81	32p	OC81	12p	2N4062	12p
AC187	22p	BC109	12p	BF194	14p	OC82D	12p	2N4286	20p
ACI88	22p	BC147	12p	BF195	14p	2N2646	60p	2N4289	20p
ADI40	50p	BC148	12p	BF197	15p	2N2904	20p	40360	35p
AD149	45p	BC149	12p	BF200	32p	2N2926	10p	40361	35p
ADI6I	33p	BC157	14p	BFY50	20p	2N3054	58p	40362	40p
AD162	36p	BC158	14p	BFY51	20p	2N3055	60p	40408	40p
AF! 14	20p	BC159	14p	BFY52	20p	2N3702	13p	ZTX108	15p
AFI15	20p	BC187	22p	BU105	225p	2N3703	12p	ZTX300	15p
AFI16	20p	BD131	75p	OC26	45p	2N3704	13p	ZTX302	20p
AFI17	20p	BD132	75p	OC28	50p	2N3705	12p	ZTX500	15p
AFI18	38p	BD133	75p	OC35	50p	2N3706	Hp	ZXT503	20p

400mW 5	% 3·3V to 3	0V, 12p.		ades to $100k \Omega$, 45p.	
DIODES	- D			SIGNAL	
BY127	1250V	IA	I2p	OA85	7p
IN4001	50V	IA	7p	OA90	5p
IN4002	100V	IA	8p (OA91	5p
IN4004	400V	IA	8p	OA202	7p
IN4006	800V	IA	10p	IN4148	5p
IN4007	1000V	IA	10p	BAII4	86

SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.

DUAL GANG, IOK +.IOK etc. log. or lin. 60p. KNOB FOR ABOVE, 12p.

FRONT PANEL, 65p.

18 Gauge panel 12in x 4in with slots cut for use with slider pots. Grey or matt black finish complete with fixings for 4 pots.

BRUSHED ALUMINIUM PANELS

I WIRE WOLLNID BOTE 3W IN SE

12in × 6in, 25p 12 in × 2½in, 10p 9in × 2in, 7p

THYRISTORS
2N5060 50V 0·8A 65p
2N5064 200V 0·8A 80p
106F 50V 4A 55p
106D 400V 4A 80p

MULLARD POLYESTER CAPACITORS C296 SERIES
'-400V: 0·001μF, 0·0015μF, 0·0022μF, 0·0032μF, 0·0032μF, 0·0047μF, 2½p. 0·0068μF, 0·01μF,
0·015μF, 0·022μF, 0·033μF, 3p. 0·047μF, 0·068μF, 0·1μF, 2½p. 0·033μF, 11p. 0·47μF, 13p.
160V: 0·01μF, 0·015μF, 0·022μF, 0·033μF, 0·047μF, 0·068μF, 3p. 0·1μF, 3½p. 0·15μF,
4½p. 0·22μF, 5p. 0·33μF, 0·021μF, 7½p. 0·68μF, 11p. 1·0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SRIES
250V P.C. mounting: 0·01μF, 0·015μF, 0·022μF, 3p. 0·033μF, 0·047μF, 0·068μF, 3p. 0·047μF, 0·068μF, 13p. 1·2μF, 20p. 2·2μF, 24p.

MYLAR FILM CAPACITORS 100V
0·01μF, 0·002μF, 0·005μF, 0·01μF, 0·02μF, 100PF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS (µF/ν) 1/63, 1·5/63, 2·2/63, 3·3/63, 4·7/63, 6·8/40, 6·8/63, 10/25, 10/63, 15/16, 15/40, 15/63, 2·2/10, 2/2/5, 2/2/63, 33/6-3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6·3, 68/16, 100/4, 100/10, 100/25, 150/6·3, 150/16, 220/4, 220/6-3, 220/16, 330/4, 6p. 47/63, 100/40, 150/25, 220/25, 330/10, 47/06·3, 7p. 68/63, 150/40, 220/40, 330/16, 1000/4, 100/40, 168/06·3, 11p. 100/63, 150/63, 220/63, 1000/10, 12p. 470/25, 680/16, 1500/6·3, 13p. 470/40, 680/25, 1000/16, 1500/10, 2200/6·3, 18p. 330/63, 680/40, 1000/25, 1500/16, 2200/10, 3300/6·3, 4700/4, 21p.

SOLID	0·1μF 0·22μF 0·47μF 1·0μF	35V 35V 35V 35V 35V	2·2μF 4·7μF 6·8μF 10μF	35V 35V 35V 25V 25V	22µF 33µF 47µF 100µF	16V 10V 6·3V 3V	I2p
				THE PERSON NAMED IN		H WHITEHOUSE SWAN	APRILITATION OF THE PARTY OF

VEROBOARD 12 + x 32 22p 16p 22 + x 5 24p 24p 33 + x 35 24p 24p 33 + x 5 27p 27p 17 x 24 75p 374p 17 x 32 100p 78p 17 x 34 (plain) — 82p 17 x 32 (plain) — 42p 22 + x 5 (plain) — 12p 24 x 32 (plain) — 12p 27 x 32 (plain) — 12p 29 x 32 (plain) — 12p 29 x 52 (plain) — 12p 20 x 52 (plain)	JACK PLUGS AND SOCKETS Standard screened 28p 2.5mm insulated 12p Standard insulated 18p 3.5mm insulated 12p Standard socket 20p 2.5mm socket 11p Standard socket 30p 3.5mm socket 11p D.I.N. PLUGS AND SOCKETS 2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin Plug 12p. Socket 8p. 4 way screened cable, 25p/metre. BATTERY ELIMINATOR 15.5 \$1.50 pin 240°, 6 pin Plug 12p. Socket 8p. 4 way screened cable, 25p/metre.
---	--

LARGE (CAN) ELECTRO	LYTICS	
1600μF 64V 74p	2500μF 64V 80p	4500μF 16V 50 p
2500μF 40V 74p	2800µF 100V £3 · 20	4500µF 25V £1.6
2500μF 50V 58p	3200μF 16V 50p	5000µF 50V £1.10
HIGH VOLTAGE TUBU	LAR CAPACITORS-	,000 VOLT
0·01μF 10p	0·047μF 13p	0·22μF 20p
0·022μF 12p	0·1μF 13p	0·47μF 22p
POLYSTYRENE CAPACITOR TO 1,000 PF E12 Series		


SMOKE AND COMBUSTIBLE GAS DETECTOR-GDI

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI
The GDI is the world's first semiconductor that can convert a concentration of gas
or smoke into an electrical signal. The sensor decreases its electrical resistance when
it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide,
methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or
smoke. This decrease is usually large enough to be utilized without amplification.
Full details and circuits are supplied with each detector.
Detector GDI, £2. Kit of parts for detectors including GDI and P.C. board but
excluding case. Mains operated detector £5.20. 12 or 24V battery operated audible
alarm £7.30. As above for PP9 battery, £6.40.

PRINTED BOARD MARKER

Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high refilef.

 PARKERS SHEET METAL FOLDING MACHINES HEAVY VICE MODELS



No. 1. Capacity 18 gauge mild steel × 36in. wide ... £21.00 carr. free No. 2. Capacity 18 gauge mild steel × 24in. wide ... £15.00 carr. free No. 3. Capacity 16 gauge mild steel × 18in. wide ... £15.00 carr. free No. 3. Capacity 16 gauge mild steel × 18in. vide ... £15.00 carr. free Also new bench models. Capacities 36in. × 18 gauge £40.00 24 in. × 16 gauge £38.00. Carriage free. Add 10% VAT to total price of machine. End folding attachments for radio chassis, tray and box making. Steel angle 36" model, 40p per ft. Other models 30p. The two smaller models will form flanges. As supplied to Government Departments. Universities, Hospitals.

One year's guarantee. Money refunded if not satisfied. Send for details.

A. B. PARKER, Folding Machine Works, Upper George St., Heckmondwike, Yorks. Heckmondwike 403997 If you have difficulty in obtaining

RRYDAY ECTRON

Please place a regular order with your newsagent or send I year's subscription (£2.95) to:-

Subscription Department, Everyday Electronics Tower House, Southampton Street, London, WC2E 9QX

Over I50 ways to better future

This FREE 76 page book can put you on the road to success througha BIET Home Study Course, Choose your subject now!

Practical Radio & Electronics Certificate course includes a learn while you build 3 transistor radio kit. Everything you need to know

> about Radio & **Electronics** maintenance and repairs for a spare time income and a *career* for a better future.

HIGHER PAY A BETTER JOB **SECURITY**

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained thousands of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

Student D.I.B., YORKS.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. BEEI. Aldermaston Court, Reading RG7 4PF.

MECHANICAL Society of	Post to address bel DRAUGHTSMANSHIP Institute of	A.B.T. Clerk of Works
Engineers— A.M.S.E. (Mech.)	Engineering	Construction
Institute of	(A.M.I.E.D.)	SurveyorsInsti- tute—L.C.S.I. CITY & GUILDS
Engineers & Technicians	General Draughtsmanship□	
(A.M.I.E.) CITY & GUILDS	□ Elec. Draughts-	(all branches)
Gen. Mech. Eng.	manship Architectural	Heating & Vent. Inst. Clerk of
Maintenance Eng	□ Draughtsmanship□	Works
Welding Gen. Diesel Eng.	☐ Technical ☐ Drawing ☐	Site Surveying Health Engineer-
Sheet Metal Work	: D	ing Road Construc-
Eng. Inspection Eng. Metallurgy	RADIO & TELE-COMMUNICATIONS	tion
ELECTRICAL &	CITY & GUILDS, Radio, TV/	Quantities, Estimates
ELECTRONIC	Radio, TV/	Hydraulics
Society of	Electronics CITY & GUILDS	Structural Eng.
Engineers— A.M.S.E. (Elec.) CITY & GUILDS	□ Telecoms. □ Gen. Radio & TV	
CITY & GUILDS Gen. Electrical	Eng.	GENERAL Agricultural Eng
Engineering	□ Radio Amateurs □ Exam □	Council of Eng.
Electrical Installations	Radio Servicing	Farm Science
Electrical Maths	TV Servicing Colour TV	Plactice
Computer Electronics		G
Electronic Eng.	AUTOMOBILE & AERONAUTICAL	Supplementary courses for Nat.
Practical Radio & Electronics	Institute of the	Certificates.
(with kit)	□ MotorIndustry □	
MANAGEMENT &	A.M.I.I. MAA/IMI CITY & GUILDS	i
PRODUCTION Institute of Cost		G.C.E.
& Management	Gen. Auto Eng.	
Acctnts. Computer	Auto Diesel Eng.	=0 (01 0 (11
Programming	☐ Garage M'ment. ☐	
Works M'ment. Work Study	neering Certs.	
Gen. Production	Gen. Aero Eng.	
Eng. Estimating &	CONSTRUCTIONAL	
Planning Storekeeping	□ Society of □ Engineers—	Coaching for many
Management	A.M.S.E. (Civ.)	exams, including
Skills Quality Control	☐ Institute of Build- ☐ ing—L.I.O.B. ☐	C & G
POS"	TODAY	FOR A
3.1 本声 3	ER TOMC	
لللحنا		
To B.I.E.T.,	Dept. BEE1	QN
	Court, Reading R	G7 4PF BEE1
NAME Block Capitals Plea	: A	
ADDRESS		

Accredited by C.A.C.C. Member of A.B.C.C. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Published approximately the third Friday of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C. 44AD. Printed in England by Index Printers Ltd., Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/Sia) Ltd. South Africa—Central News Agency Ltd. Publisher's Subscription Rate (including postage): For one year to any part of the world £2-95. Everyday Electronics is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Henry'

DON'T RELY ON YOUR MEMORY BUY NOW AT BARGAIN PRICES

Hi Fi and Transistors - Up to date Brochures on request

You pay less VAT with Henry's **Low Prices**

BUILD THE

Now built and used by thousands f satisfied customers. Features

20 + 20 WATT IC STEREO AMPLIFIER

As featured by Practical Wireless 1972

Now built and used by thousands of satisfied customers. Features slim design overall size in cabinet 15½" x 2½" x 6½". 6-IC's, 10 transistors, stabilisers Gardners low field transformer. Fibre Glass PC Panel, complete chassis work. Now available built and tested as well as in kit form. HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES — DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION. PACILITIES. Onjoffs witch indicator, headphones socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector; Mag. P.U., Radio Tuner, Aux. Can be altered for Mic. Tape. Tape-head, etc.

Constructional details Ref. No. 21
30p. Distributed by Henry's throughout UK. FREE—Teak cabinet with complete kit. Kit

Kit price £28-50 (+VAT+50p carr/packing)

or built and tested £35-00 (+ VAT + 50p carr/packing) as illustrated.

EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT **SPEAKERS**

DISCO MINI A complete portable disco, fitted mixer/preamp, 2 decks all facilities. As above but with Slider Controls 4118-50 100 wattamplifier for above 59-LS 100 wattamixer/amplifier with slider controls 100 mattamixer/amplifier 449-50 R50-50 watt mixer/amplifier 475-50 DISCO AMP 100 wattamixer/amplifier 473-00 Northcourt: £37 · 50 £45 · 00

DISCO AMP 100 watt mixer/amplifier in Northcourt:
400 40 watt mixer/amp
800 80 watt mixer/amp
DISCO MIXER/PREAMPLIFIERS
(OP for up to 6-100 watt amplifiers)
SDLI (sider controls)
SDLI (sider controls)
DISCO YOX (slider controls) the £49 · 50 £58 · 50 complete disco preamp
DJ100 100 watt power amplifier for £49 · 50 DJ30L Mk II 3 channel 3kw sound to

£41 · 25 DJ30L Mk III slider controls
DJ DISC LITE as 30L-2 plus variable speed flashes
DIMAMATIC I kW adjustable speed

speed flashes
DIMAMATIC I kW adjustable speed
auto dimmer
Carlsboro Reverberation Unit
Disco anti-feedback microphone
Colt 150 watt liquid wheel projector
150 watt QI liquid wheel projector
150 watt QI liquid wheel projector
Spare Effects and liquid cassettes large
ange of patterns
6 inch Liquid wheels
Various cassettes
Mini spot bank fired 3 lamps
Auto Trilite (mini w flashers)
Bubblemaker www.nguid
Licy Speakers/Lighting
Licy Argest range of Disco Lighting.
FREQUEST.
AKG / RESLO / DJ / CARLSBRO / EAGLE
MICS., STANDS, MIXERS, CABINETS.
CHASSIS AND COMPLETE SPEAKER
TYSTEMS, MEGAPHONES, TURN-TABLES, PUBLIC ADDRESS
COM-PONENTS.



All prices carr. paid (UK) (VAT EXTRA) Barclaycard/Access call, write or phone your order 01-723-6963—easy terms for callers.

EXCLUSIVE DECCA KELLY

12 watt speaker Tweeter systems. 8" Bass/Midrobe and Melinexs/Midrobe and Melinex Domed HF radiator plus crossover £12-50 per pair of systems (carr./packg. 40p) or built into veneered cabinets, size 18 × 12 × 64" £19 50 pair (carr. £1).

HI-FI TAPE EQUIPMENT

U.K.'s largest range with discounts and demonstrations for callers. Latest stock lists on request (Ref. No. 17). Phone 01-402-4736 for Barclay/Access Card. Direct orders and latest prices

TRANSISTORS/SEMI-CONDUCTORS

U.K.'s largest range for every application. Small quantity discounts. Also Trade, Export and Industrial enquiries invited. Latest stock list (Ref. No. 36) including valves on request.

ELECTRONICS SUPPLIES

Specialists in electronics for more than 30 years. Trade and industry supplies—every type of component and equipment.





Henry's

SJA (S

NEW SINCLAIR PROJECT 80

Stereo PreAmplifier
Audio Filter Unit
Z40 15 Watt Amplifier
Z60 25 Watt Amplifier
Z50 25 Watt Amplifier
Z50 Mod (S Tab) | or 2 Z40
Z56 Mod (S Tab) | or 2 Z60
TRANSFORMER FOR PZ8 £11.95 £6.95 £5.45 £6.95 £4.98 £7.98 £7.98 NEW FM TUNER STEREO DECODER

All items post paid.

BUILD THE NEW HENELEG STEREO FM TUNER

A completely new high stability stereo FM tuner. Features variable capacity diode tuning, stabiliser power supply, IC Decoder, high gain low noise. If stages. LED indicators. Tuning meter, AFC, easy to construct and use. Mains operated. Slim modern design with fibre glass PC, teak cabinet, etc. Available as a kit to build or ready built. Overall size 8° x 2½° x 6½°. Produced to give high performance with a realistic price. (Parts list and constructional details Ref. No. S 30p). Henry's are sole distributors UK and Europe.

KIT PRICE £21.00 (+ VAT) or built and tested £24.95 (+ VAT)

LIVING SOUND LOW NOISE TOP QUALITY CASSETTES MADE BY EMI TAPES LTD. TO INTERNATIONAL STANDARDS ESPECIALLY FOR HENRY'S. ALL POST PAID LESS THAN ½ REC. PRICES COMPLETE WITH LIBRARY CASES

C 60 £1·10 £1·98 £20·00 £25 for £7·40 £1·98 £20·00 £1.40 £1.40 £1.40 £1.40 £1.40 £1.40 £1.40 £1.45 £1.

LEARN A LANGUAGE—complete with phrase book. German — French — Spanish — Italian £1.36 per course. £5 for any 4.

LOW COST HI-FI SPEAKERS

SPECIAL OFFERS
EMI 13" x 8"-full range speakers (post 20) peach or 30p pair)
*150TC—8 ohms Twin Cone 10 watt 62-20 each or £4-00 pair.
*450 10 watt C/o Twin Tweeters 3, 8 or 15 ohms £3-85 each
EW 15 watt 8 ohms C/o Tweeter £5-25
350 20 watt C/o Tweeters 8 or 15 ohms £7-80 each
*Polished wood cabinet £4-80

Polished wood cabinet £4.80 post 35p.



KEF KK2 KEF KK3



£4 · 75 £6 · 30 £8 · 50 £8 · 40

£3 · 75 £7 · 20 £8 · 50 £13 · 75

£2 · 10 £3 · 35 £4 · 80 £5 · 50 £5 · 52 £2 · 70 £3 · 10

HENRY'S CATALOGUE

and raw

£24·50 pair £35·95 pair £18·30 pair £32·95 pair £51·50 pair £55·00 pair £78·00 pair **BUILD YOURSELF A POCKET CALCULATOR**

A complete kit, packaged in a polystyrene container and taking about 3 hours to assemble—thats the Sinclair Cambridge pocket calculator from Henry's. Some of the many features include interface chip, thick-film resistor pack, printed circuit board, electronic components pack. Size 44" long x 2" wide x \(\frac{1}{2}\)'' deep.
Free of charge with the kit for the more advanced technologist is a 32-page booklet explaining how to calculate Logs. Tangents. Sines etc.

£24-95 Also available assembled ready to use. £27-20 + VAT. + VAT.



10% VAT to be added to all orders. Export supplied. Prices and descriptions correct at time of proof. Subject to change without notice. E&O E. Like a permanent job at Henry's? Experienced and trainee salesmen required. Tel. 01-402 8791.

See page 251 of this magazine



EDGWARE ROAD. LONDON W2

404.406 Electronic Components and Equipment 01-402 8381
309 PA – Disco – Lighting High Power Sound 01-723 6963
303 Bargains Store (Callers only)
Home and Car Entertainment Centres. London and branches now open.
120 Shaftesbury Avenue, London W1 01-437 9692
104 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7402
190-194 Station Road, Harrow, Middlesse 01-863 7788/9
354-356 Edgware Road, London W2 01-402 5854/4736

All mail to 303 Edgware Road, London W2 1BW All stores open 9 am to 6 pm six days a week Hi-Fi - Tape Equipment